 


---

## 2. Boolean Logic & Basic Gates

### 2.1 Boolean Logic

- Logic is the realm of human reasoning that allows you to determine whether or not a particular statement is **TRUE** or **FALSE** depending on the truth of other pertinent conditions.
- Logic based on true/false states lends itself very well to digital states which, as we now know, are also based on two states.
- By way of example, consider the logic statement '*the light is on*' if '*the bulb is not burned out*' and if '*the light switch is on*'.
- More explicitly, we can say that '*the light is on*' is **TRUE** if '*the bulb is not burned out*' is **TRUE** and if '*the light switch is on*' is **TRUE**.
- We can express this in tabular form to allow us to see the 'big picture' more clearly, as follows:




<i>the bulb is not burned out</i>	<i>the light switch is on</i>	<i>the light is on</i>
TRUE	FALSE	$\Rightarrow$ <b>FALSE</b>
FALSE	TRUE	$\Rightarrow$ <b>FALSE</b>
FALSE	FALSE	$\Rightarrow$ <b>FALSE</b>
TRUE	TRUE	$\Rightarrow$ <b>TRUE</b>

- Using a binary representation of '1' and '0', this table looks like:

<i>the bulb is not burned out</i>	<i>the light switch is on</i>	<i>the light is on</i>
1	0	<b>1</b>
0	1	<b>0</b>
0	0	<b>0</b>
1	1	<b>1</b>

- The above tabular form is known as a **truth table**, in which all possible combinations of the inputs are listed.
- The English logician and mathematician, George Boole, developed a mathematical system for such logic, allowing problems in logic to be solved in an algebraic way.
- This branch of mathematics is known as **Boolean Algebra** and is applied in the design and analysis of digital systems.

 

---

## 2.2 Basic Logic Gates

- Digital logic circuits contain several basic logic components, referred to as **gates**. These gates carry out important logical operations and form the fundamental building blocks of digital systems.
- We are now going to study a selection of these important gates.
- Each gate will be examined in terms of its symbol, its Boolean algebraic expression and operator and its truth table.
- Note, in the following section of the notes, **A, B, C**, etc... are used to **denote logical inputs** while **f** denotes a **logical output**.


### *The NOT gate ...*

- The **NOT** gate (or the **Inverter**) simply inverts the input. Hence, if the input is a logic '1' then the output will be a logic '0' and vice versa.


- The truth table for the inverter is:

A	f

- The symbol for the gate is:

 

 - The Boolean expression for the NOT gate is:  $f = \overline{A}$  (or  $A'$ )
- An example application using a bank of inverters is to produce the 1's complement of an 8-bit binary number, as illustrated below:




---

### *The AND gate ...*


- The **AND** gate performs logical *multiplication*.
- For a 2-input AND gate, the output is only HIGH if both inputs are HIGH, otherwise the output is LOW.
- This principle extends to an  $n$ -input gate. In other words, for an  $n$ -input AND gate, the output is HIGH if **ALL**  $n$  inputs are HIGH, otherwise it is LOW.
- The truth table for the 2-input AND gate is:

A	B	f

 - *Note – as there are 2 inputs, there are 4 possible combinations to be covered in the truth table. Recall that for  $n$ -inputs there are  $2^n$  possible combinations.*
- The symbol for the gate is:



 - The Boolean expression for a 2-input AND gate is:  $f = AB$  (or  $A.B$ )
- The Boolean expression for a 3-input AND gate is:  $f = ABC$
- And so on for a higher number of inputs ...
- An example seat belt alarm application using an AND gate is shown below:




---

### The OR gate ...


- The **OR** gate performs logical *addition*.
- For a 2-input OR gate, the output is HIGH if any of the inputs are HIGH. The output is only LOW if both inputs are LOW.
- For an  $n$ -input OR gate, the output is HIGH if **ANY** of the  $n$  inputs are HIGH, otherwise it is LOW.
- The truth table for the 2-input OR gate is:

A	B	f

- The symbol for the gate is:

 

 - The Boolean expression for a 2-input OR gate is:  $f = A + B$
- The Boolean expression for a 3-input OR gate is:  $f = A + B + C$
- And so on for a higher number of inputs ...
- An example intruder alarm application using an OR gate is shown below:



---


### *The NAND gate ...*

- The **NAND** gate stems from NOT–AND. It implies an AND function followed by an inverter.
- For a 2-input NAND gate, the output is only LOW if both inputs are HIGH, otherwise the output is HIGH.
- In general, we can say that for an  $n$ -input NAND gate, the output is LOW if **ALL**  $n$  inputs are HIGH, otherwise it is HIGH.


- Thus, the truth table for the NAND gate is:

A	B	f

- The symbol for the gate is:

 

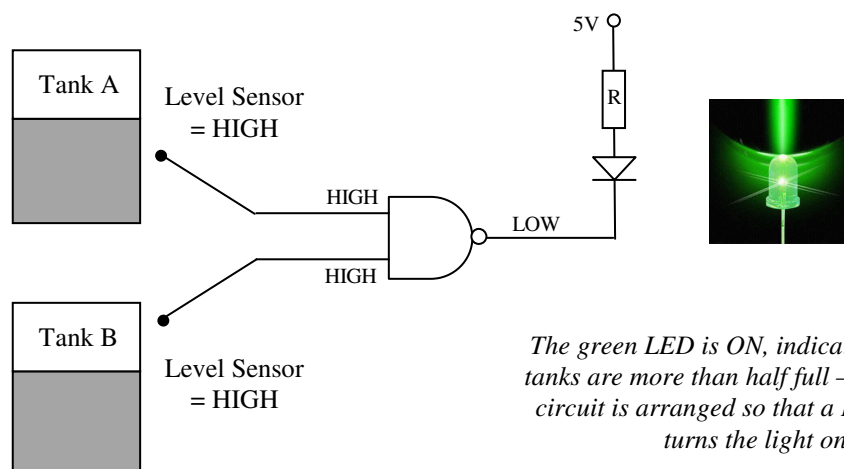- The Boolean expression for a 2-input NAND gate is:  $f = \overline{AB}$  (or  $\overline{A.B}$ )
- The Boolean expression for a 3-input NAND gate is:  $f = \overline{ABC}$
- And so on for a higher number of inputs ...
- An example fluid level monitoring application using a NAND gate is shown below:



*The green LED is ON, indicating that both tanks are more than half full – note how the circuit is arranged so that a LOW voltage turns the light on.*


---

### *The NOR gate ...*


- The **NOR** gate stems from NOT–OR. It implies an OR function followed by an inverter.
- For a 2-input NOR gate, the output is LOW if any of the inputs are HIGH otherwise it is HIGH.
- In general, we can say that for an  $n$ -input NOR gate, the output is LOW if **ANY** of the  $n$  inputs are HIGH, otherwise it is HIGH.
- Thus, the truth table for the NOR gate is:

A	B	f

- The symbol for the gate is:

 

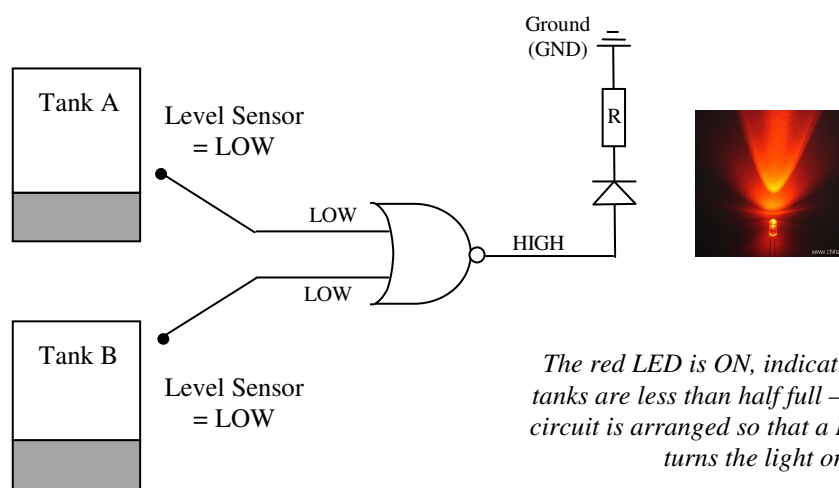- The Boolean expression for a 2-input NOR gate is:  $f = \overline{A + B}$
- The Boolean expression for a 3-input NOR gate is:  $f = \overline{A + B + C}$
- And so on for a higher number of inputs ...
- An example low fluid level warning system using a NOR gate is shown below:



*The red LED is ON, indicating that both tanks are less than half full – note how the circuit is arranged so that a HIGH voltage turns the light on.*


---

### *The XOR gate ...*


- The **XOR (Exclusive – OR)** gate is a combination of the previous gates. However, it is an important gate in many applications and, as such, has its own symbol.
- For a 2-input XOR gate, the output is HIGH if both inputs are different and the output is LOW if both inputs are the same.
- Thus, the truth table for the XOR gate is:

A	B	f

- The symbol for the gate is:

 

- The Boolean expression for the XOR gate is:  $f = A \oplus B \quad (= \bar{A}B + A\bar{B})$
- The XOR operation is a binary operation and is therefore defined for two inputs only.
- However, it is nevertheless common in electronic design to use the XOR operation on 3 or more signals.
- For 3 (or more) inputs  $A \oplus B \oplus C = 1$  only if the number of 1's in the input combination is odd.
- Since XOR gates are only designed for 2 inputs, the 3-input XOR function is implemented by using two 2-input XOR gates as follows:

 

- On closer inspection of the truth table, we can see that the XOR gate acts like a 2-bit adder:


$$\begin{array}{ll} 0 + 0 = 0 \\ 0 + 1 = 1 \\ 1 + 0 = 1 \\ 1 + 1 = 0 \quad \dots \text{the carry of '1' is lost} \end{array}$$

### The XNOR gate ...

- The final gate that we are going to look at is the **XNOR (Exclusive – NOR)** gate.
- For a 2-input XNOR gate, the output is LOW if both inputs are different and the output is HIGH if both inputs are the same.
- Thus, the truth table for the XNOR gate is:

A	B	f



- The symbol for the gate is:

 

- The Boolean expression for a 2-input OR gate is:  $f = \overline{A} \oplus B$  ( $= AB + \overline{A}\overline{B}$ )
- On closer inspection of the truth table, we can see that the XNOR gate acts like a 2-bit comparator, i.e. when both bits are the same, the output is HIGH but when the bits are different the output is LOW.
  
### Integrated Circuits (ICs) ...

- From a laboratory viewpoint, you will notice that logic gates are provided on integrated circuits (ICs), where a single IC can contain multiple gates.
- For example, a **quad 2-input OR** integrate circuit contains  $4 \times 2$ -input OR gates, as illustrated below. Hence, this IC provides you with 4 OR gates on one chip.



- In labs, make sure that you are using the appropriate ICs for your circuits and make sure to connect them correctly!*
- Detailed information on integrated circuit technologies (such as CMOS and TTL) will be covered in other modules.*




## 2.3 Preliminary Definitions

- A **canonical truth table** is a table in which **all** possible combinations are listed.
- For example, the canonical truth table of the AND gate:

A	B	f
0	0	0
0	1	0
1	0	0
1	1	1

 - Other possibilities exist – for example, the AND gate can be view as an **enable** gate and therefore, we can express its operation in tabular form as follows:



- A **variable** is a symbol used to represent a logical quantity. As we have seen, a single variable can have a value of 1 or 0.
- The **complement** is the inverse of a variable and is denoted by a bar over the variable. For example, the complement of variable A is  $\bar{A}$ .
- A **literal** is a variable or its complement.
- A **canonical product term** is a product expression containing all literals e.g. ABC for a 3 variable function.
- A **canonical sum term** is a sum expression containing all literals e.g.  $A + B + C$  for a 3 variable function.
- A **canonical expression** is a logical expression made up of canonical terms.
- There are two standard forms used, namely the **sum-of-products** (SOP) and the **product-of-sums** (POS). For example:

$$f_{(x,y,z)} = xy\bar{z} + xyz + \bar{x}yz \quad \text{Sum of products (SOP)}$$

$$f_{(x,y,z)} = (x + \bar{y} + z)(\bar{x} + y + z) \quad \text{Product of sums (POS)}$$

*Note, how each term is in canonical form!*

- 
- The canonical form can often be simplified or minimised to reduce the number of logic gates required to implement a particular Boolean function.
  - For example a **simplified or minimised Boolean function** might look like:

$$f_{(x,y,z)} = x + x\bar{y}z + y\bar{z} \quad \text{Sum of products (SOP)}$$

$$f_{(x,y,z)} = (x + \bar{y})(y + \bar{z}) \quad \text{Product of sums (POS)}$$

- The main goal in digital system design is to obtain a minimised expression for a digital function since this generally leads to a more cost-effective design, i.e. fewer gates are required.
- There exist a few different techniques for carrying out Boolean minimisation. We are now going to look in detail at two such techniques, namely Boolean Algebra and Karnaugh Maps.