

别担心，好好复习，咱们尽可能地去拿下所有可以拿下的分数就好，不要急，也不要懊悔什么，按自己的节奏来读书就好！明确自己的赛道，便无怨无悔。加油吧！！！！



加油！！！！

**SEMESTER 1**  
**2020-21**

**EE204FZ**  
**Analogue Electronics 1**

Dr. L. Tarachand, Prof. R. Farrell, Dr. J. Harkin

Time allowed: 2 hours

Answer question ONE and any TWO other questions  
Q1 is worth 34 marks. All others are worth 33 marks each.

**Instructions**

	<b>Yes</b>	<b>No</b>
Log Books Allowed	<input type="checkbox"/>	<b>X</b>
Formula Tables Allowed*	<b>X</b>	<input type="checkbox"/>
Other Allowed ( <i>enter details</i> )	<b>X</b>	<input type="checkbox"/>

**General**

- Formula Tables Allowed: Attached to the back of the exam paper
- Other Allowed: Non-programmable calculator

### QUESTION 1 (34-marks)

(a) Choose the correct answer. Each question carries equal 1 mark. (10-marks)

- (1) When **PN junction** is in forward bias, by increasing the battery voltage
- (A) circuit resistance increases
  - (B) current through PN junction increases**
  - (C) current through PN junction decreases
  - (D) none of the above
- (2) A **PN junction** is said to be forward-biased when
- (A) N-side is connected directly to the p-side
  - (B) junction is earthed
  - (C) the positive terminal of the battery is connected to P-side and the negative side to the N-side**
  - (D) the positive terminal of the battery is connected to N-side and the negative side to the P-side
- (3) **MOSFET** uses the electric field of
- (A) gate capacitance to control the channel current.
  - (B) barrier potential of p-n junction to control the channel current.
  - (C) both (A) and (B)
  - (D) none of these**
- (4)** The extremely high input impedance of a **MOSFET** is primarily due to the
- (A) absence of its channel
  - (B) negative gate-source voltage
  - (C) depletion of electric current carriers
  - (D) extremely small leakage electric current of its gate capacitor**
- (5) The **ratio** of output current change against an input voltage change is called:
- (A) Trans-conductance**
  - (B) Siemens
  - (C) Resistivity
  - (D) Gain
- (6) For which region of operation is a **MOSFET** represented by its **small signal model**?
- (A) Triode
  - (B) Saturation**
  - (C) Cut-off
  - (D) Independent of the region

PP<sub>1</sub>E—forward

- (7) In a small signal equivalent model of an FET, what does  $g_m V_{GS}$  stand for?  
 (A) A pure resistor  
 (B) Voltage controlled current source  
 (C) Current controlled current source  
 (D) Voltage controlled voltage source
- (8) A noninverting closed-loop op-amp circuit generally has a gain factor:  
 (A) less than one  
 (B) greater than one  
 (C) of zero  
 (D) equal to one
- (9) Op-amps used as high- and low-pass filter circuits employ which configuration?  
 (A) Noninverting  
 (B) Comparator  
 (C) Open-loop  
 (D) Inverting
- (10) An ideal operational amplifier has  
 (A) infinite output impedance  
 (B) zero input impedance  
 (C) infinite bandwidth  
 (D) All of the above
- (b) Describe the three regions of operation of a MOSFET. (3-marks)
- (c) Define channel length modulation parameter ( $\lambda$ ). Discuss, how the voltage-current characteristics of MOSFET are affected by  $\lambda$  value. (3-marks)
- (d) Differentiate between BJT and FET in terms of their structure, characteristics and applications. (4-marks)

unipolar bipolar

Triode region: current is proportion to  $V_{ds}$

Active region: current will not increase dramatically and  $V_{gs}$  determine current

Cutoff region: there is no current in the channel

- (e) For the MOSFET in figure 1(e), determine the region of operation. The threshold voltage of MOSFET is  $V_{TP} = -0.4$  V. (3-marks)

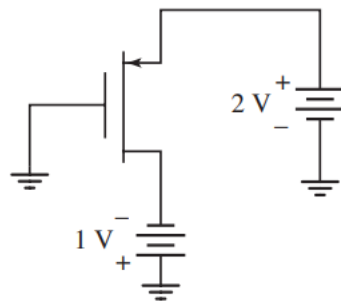


Figure 1(e)

- (f) When analyzing an ideal operational amplifier, what assumptions are made? List them down. (3-marks)

- (g) With the help of a diagram, define what is the slew rate of an operational amplifier? (4-marks)

- (h) The op-amp in the circuit shown in figure 1(h) is ideal except it has a finite open-loop gain. If  $A_{od} = 104$  and  $v_O = -2$  V, determine  $v_I$ . (4-marks)

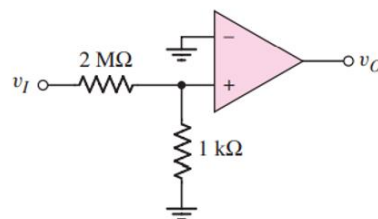


Figure 1(h)

## QUESTION 2 (33-marks)

- (a) Describe what does it mean “the channel is pinched off” in MOSFET? (3-marks)
- (b) Consider the circuit in figure 2(b). Assume that  $V_{TN} = 1\text{ V}$ ,  $K_n = 1.5\text{ mA/V}^2$ , and  $\lambda = 0$ . Sketch  $I_D$  versus  $V_{DS}$  for  $0 \leq V_{DS} \leq 5\text{ V}$ . Label and add numerical values on each the axis. Calculate and indicate  $V_{DS}(\text{Sat})$  on the plot. Clearly indicate the saturation and Ohmic regions and the saturation current in the diagram. (4-marks)

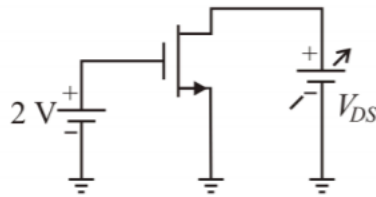


Figure 2(b)

- (c) The transistor characteristics  $i_D$  versus  $v_{DS}$  for an NMOS device are shown in figure 2(c).
- Is this an enhancement-mode or depletion-mode device? (1-marks)
  - Determine the values for  $K_n$  and  $V_{TN}$ . (3-marks)
  - Determine  $i_{D(\text{sat})}$  for  $v_{GS} = 3.5\text{ V}$  and  $v_{GS} = 4.5\text{ V}$ . (2-marks)

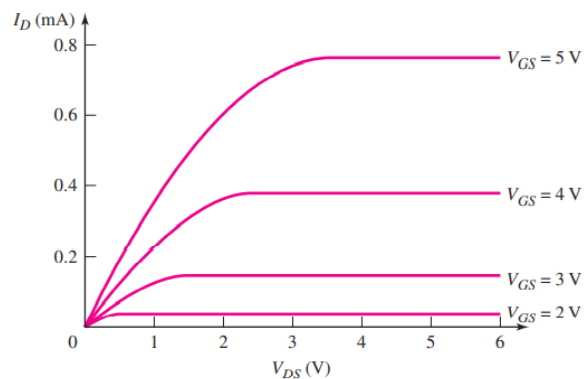


Figure 2(c)

- (d) CMOS transistors are used for a logic gate as shown in figure 2(d). Identify the type of logic gate, draw the logic symbol and write truth table for the logic function. (3-marks)

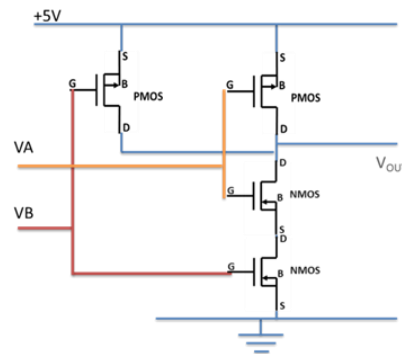


Figure 2(d)

- (e) An NMOS device has parameters  $V_{TN} = 0.8 \text{ V}$ ,  $L = 0.8 \mu\text{m}$ , and  $k'_n = 120 \mu\text{A/V}^2$ . When the transistor is biased in the saturation region with  $V_{GS} = 1.4 \text{ V}$ , the drain current is  $I_D = 0.6 \text{ mA}$ .

- What is the channel width  $W$ ? (3-marks)
- Determine the drain current when  $V_{DS} = 0.4 \text{ V}$ . (2-marks)
- What value of  $V_{DS}$  puts the device at the edge of saturation? (2-marks)

- (f) Describe the operation of a transmission gate? Draw its symbol and discuss its applications. (4-marks)

- (g) The transistor in the circuit in figure 2(g) is used to turn the LED on and off. The transistor parameters are  $V_{TN} = 0.6 \text{ V}$ ,  $k'_n = 80 \mu\text{A/V}^2$ , and  $\lambda = 0$ . The diode cut-in voltage is  $V_V = 1.6 \text{ V}$ . Design  $R_D$  and the transistor width-to-length ratio such that  $I_D = 12 \text{ mA}$  for  $V_I = 5 \text{ V}$  and  $V_{DS} = 0.15 \text{ V}$ . (6-marks)

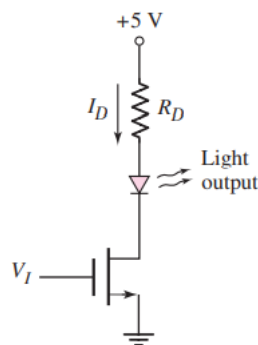


Figure 2(g)

### QUESTION 3 (33-marks)

- (a) Define biasing and why is it important for a MOSFET amplifier? List down different ways of biasing.  
(5-marks)
- (b) Explain the impact of the **Miller Effect** on the importance of the gate-drain capacitance for a MOSFET amplifier?  
(3-marks)
- (c) What does the term “clipping” refer to and how should you select your biasing values such that you would minimise the risk of it occurring?  
(3-marks)
- (d) Draw the small signal equivalent circuit model for a MOSFET, label clearly model components and pin names.  
(3-marks)
- (e) For the NMOS common-source amplifier in figure 3(e), the transistor parameters are:  $V_{TN} = 0.8 \text{ V}$ ,  $K_n = 1 \text{ mA/V}^2$ , and  $\lambda = 0$ . The circuit parameters are  $V_{DD} = 5 \text{ V}$ ,  $R_S = 1 \text{ k}\Omega$ ,  $R_D = 4 \text{ k}\Omega$ ,  $R_1 = 225 \text{ k}\Omega$ , and  $R_2 = 175 \text{ k}\Omega$ .
- (i) Calculate the quiescent values  $I_{DQ}$  and  $V_{DSQ}$ .  
(4-marks)
- (ii) Determine the small-signal voltage gain for  $R_L = \infty$ .  
(3-marks)
- (iii) Determine the value of  $R_L$  that will reduce the small-signal voltage gain to 75 percent of the value found in part (ii).  
(3-marks)

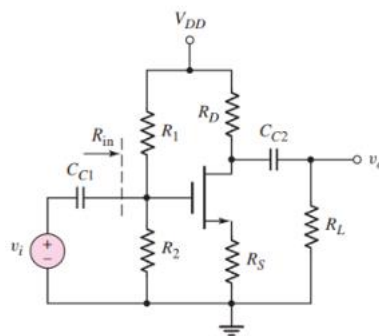


Figure 3(e)

- (f) What is the function of decoupling capacitors in amplifier circuits? Discuss what size of capacitor is best for high frequency signals. (3-marks)
- (g) Consider the source-follower circuit in figure 3(g). The small-signal parameters of the transistor are  $g_m = 2 \text{ mA/V}$  and  $r_o = 25 \text{ k}\Omega$ .
- (i) Determine the open-circuit ( $R_L = \infty$ ) voltage gain and output resistance. (3-marks)
- (ii) If  $R_L = 2 \text{ k}\Omega$  and the small-signal transistor parameters remain constant, determine the voltage gain. (3-marks)

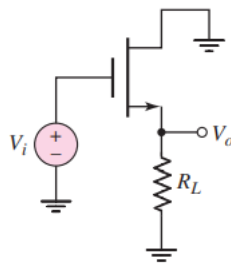


Figure 3(g)



Infinite input  
Zero output  
Infinite bandwidth

(b)  
The gain is Big enough  
The input impedance is high enough  
The output impedance is low enough

**QUESTION 4** (33-marks)

- (a) List down the characteristics of ideal and practical operational amplifiers (Op-Amp). (4-marks)
- (b) What are the design factors must be considered when designing Op-Amp? (3-marks)
- (c) Using the op-amp circuit in figure 4(c), explain the concept of 'virtual earth'. (3-marks)

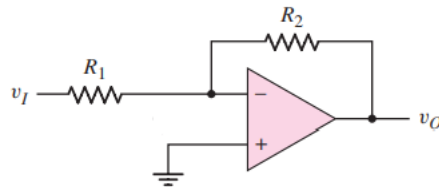


Figure 4(c)

- (d) Consider the ideal noninverting Op-Amp circuit in figure 4(d).
- (i) Derive the expression for  $v_O$  as a function of  $v_{I1}$  and  $v_{I2}$ . (4-marks)
- (iii) Find  $v_O$  for  $v_{I1} = 0.2$  V and  $v_{I2} = 0.3$  V. (2-marks)
- (iii) Find  $v_O$  for  $v_{I1} = +0.25$  V and  $v_{I2} = -0.40$  V. (2-marks)

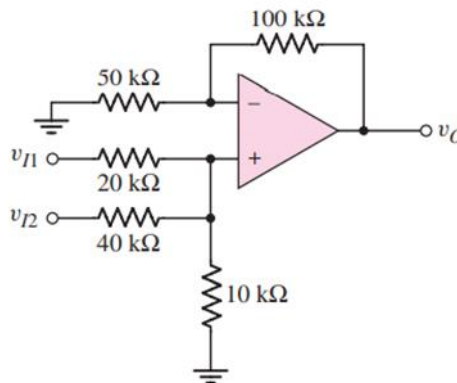


Figure 4(d)

- (e) Explain why low output impedance in an Op-Amp is important? (3-marks)

(f) The circuit in figure 4(f) is a first-order low-pass active filter.

(i) Show that the voltage transfer function is given by:

(4-marks)

$$A_v = -\frac{R_2}{R_1} \cdot \frac{1}{(1+j\omega R_2 C_2)}$$

(ii) What is the voltage gain at dc( $\omega = 0$ )?

(2-marks)

(iii) At what frequency is the magnitude of the voltage gain a factor of  $\sqrt{2}$  less than the dc value? (This is the  $-3$  dB frequency.)

(2-marks)

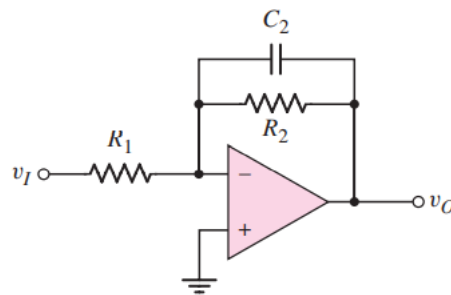


Figure 4(f)

(g) Design the low-pass active filter in figure 4(f) such that the input resistance is  $20\text{ k}\Omega$ , the low-frequency gain is  $-15$ , and the  $-3$  dB frequency is  $5\text{ kHz}$ .

(4-marks)

### Key MOSFET Equations

$$I_{D\ (Linear)} = \frac{W}{L} \mu_n C_{ox} \left( (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right)$$

$$I_{D(sat)} = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_T)^2$$

$$g_m = \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_T) = \sqrt{2 \frac{W}{L} \mu_n C_{ox} (I_{D(SAT)})}$$