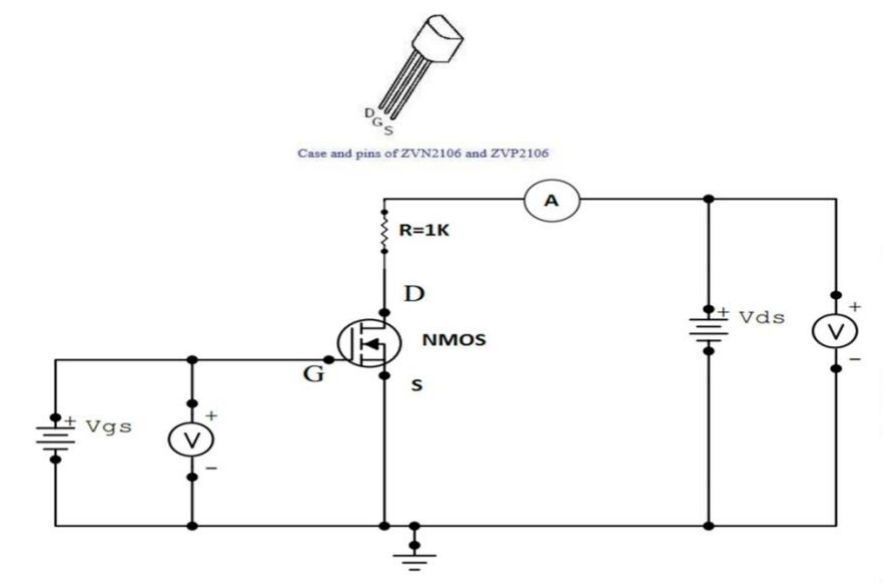


Lab1 Characteristics of the FET Transistor




Part.1

Brief introduction: This module requires me to measure the current situation at different Vds and Vgs.

1、

	Vds=0V	Vds=1V	Vds=2V	Vds=3V	Vds=4V	Vds=5V
Vgs=0V	infinite	infinite	infinite	infinite	infinite	infinite
Vgs=0.5V	infinite	infinite	infinite	infinite	infinite	infinite
Vgs=1.0V	infinite	infinite	infinite	infinite	infinite	infinite
Vgs=1.5V	infinite	infinite	infinite	infinite	infinite	infinite
Vgs=2.0V	infinite	0.8	1.1	1.1	1.1	1.2
Vgs=3.0V	infinite	0.8	1.7	2.6	3.5	4.4
Vgs=5.0V	0	0.9	1.8	2.6	3.5	4.4


Figure.01

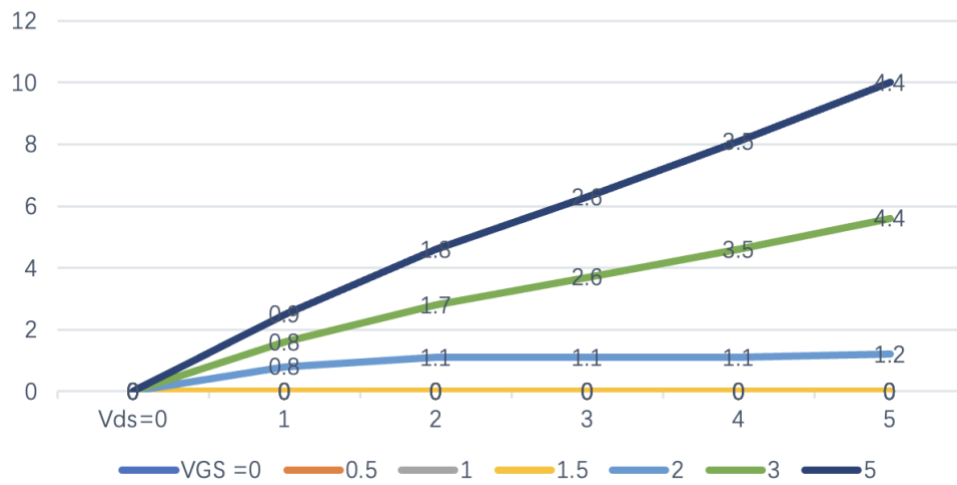

2、

$R = V_{ds}/I_d$	$V_{ds}=0$	$V_{ds}=1$	$V_{ds}=2$	$V_{ds}=3$	$V_{ds}=4$	$V_{ds}=5$
$V_{GS} = 2$	0Ω	1.25	1.81	2.73	3.64	4.17
$V_{GS} = 3$	0Ω	1.25	1.18	1.15	1.14	1.13
$V_{GS} = 5$	0Ω	1.11	1.11	1.15	1.14	1.13

$R = V_{ds}/I_d$

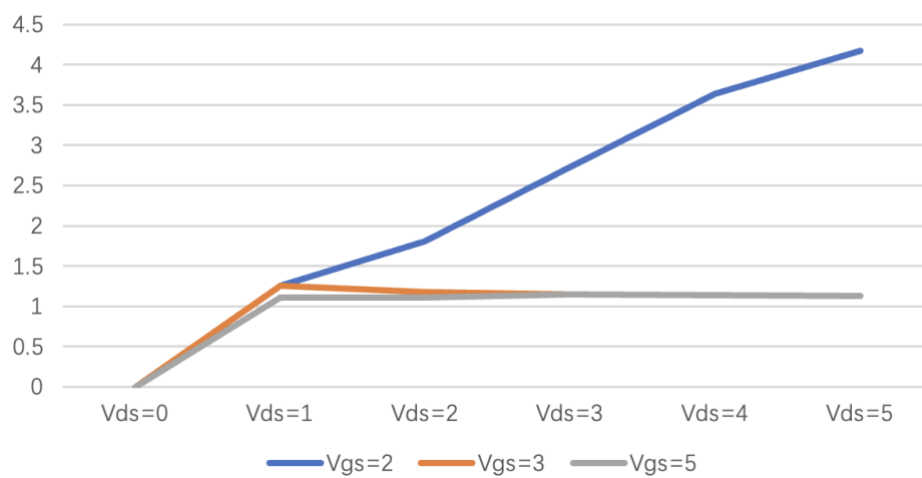


3、

$$V_{th} = 1.78V$$

Comment: In this module, I measured the resistance at different voltages by stepping 1.0 at each step. When the voltage was greater than the threshold value of 1.78, the current began to appear. Besides, I find that when $V_{gs}=2$, there will be a constant current zone.

Part2.

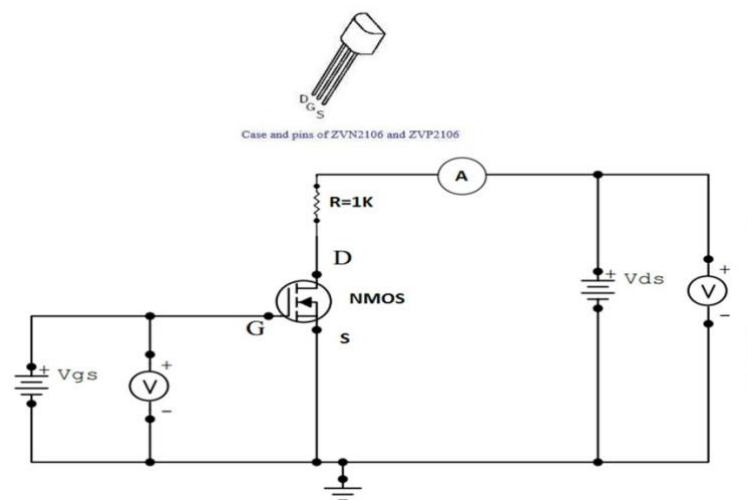

1、

When $V_{gs}=3$,


$V_{ds}(V)$	0.1	0.2	0.3	4	5	6	7	8	9	1.0
-------------	-----	-----	-----	---	---	---	---	---	---	-----

$I_D(\text{mA})$	0.09	0.15	0.22	0.30	0.40	0.50	0.60	0.70	0.78	0.85
------------------	------	------	------	------	------	------	------	------	------	------


$V_{DS}(\text{V})$	3.0	3.1	3.2	3.3	3.4	3.5	3.6	3.7	3.8	3.9	4.0
$I_D(\text{mA})$	2.6	2.72	2.75	2.8	2.9	3.0	3.1	3.2	3.3	3.4	3.5

2、

	$V_{DS}=0$	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8	0.9	1	/
$V_{GS}=3$	I_D	0.09	0.15	0.22	0.3	0.4	0.5	0.6	0.7	0.78	0.85	/
$V_{GS}=3$	$R=\Delta V_{DS}/\Delta I_D$	1667	1429	1250	1000	1000	1000	1000	1250	1429	/	/
$V_{GS}=3$	$R=V_{DS}/I_D$	1111	1333	1363	1333	1250	1200	1167	1143	1153	1142	/
	$V_{DS}=0$	3.0	3.1	3.2	3.3	3.4	3.5	3.6	3.7	3.8	3.9	4.0
$V_{GS}=3$	I_D	2.6	2.67	2.74	2.8	2.9	3	3.1	3.2	3.3	3.4	3.5
$V_{GS}=3$	$R=\Delta V_{DS}/\Delta I_D$	1420	1430	1490	1000	1000	1000	1000	1000	1000	1000	1430
$V_{GS}=3$	$R=V_{DS}/I_D$	1153	1161	1167	1178	1172	1167	1161	1156	1151	1147	1142

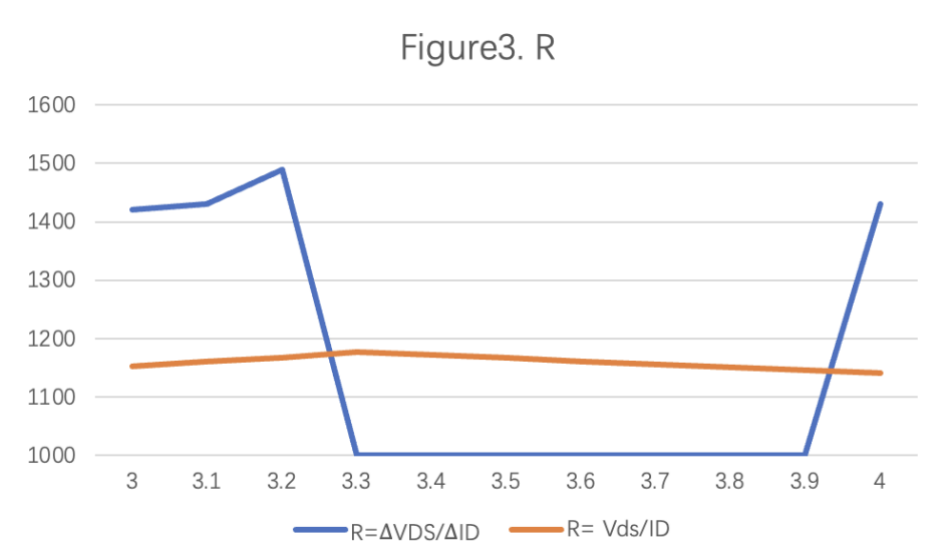

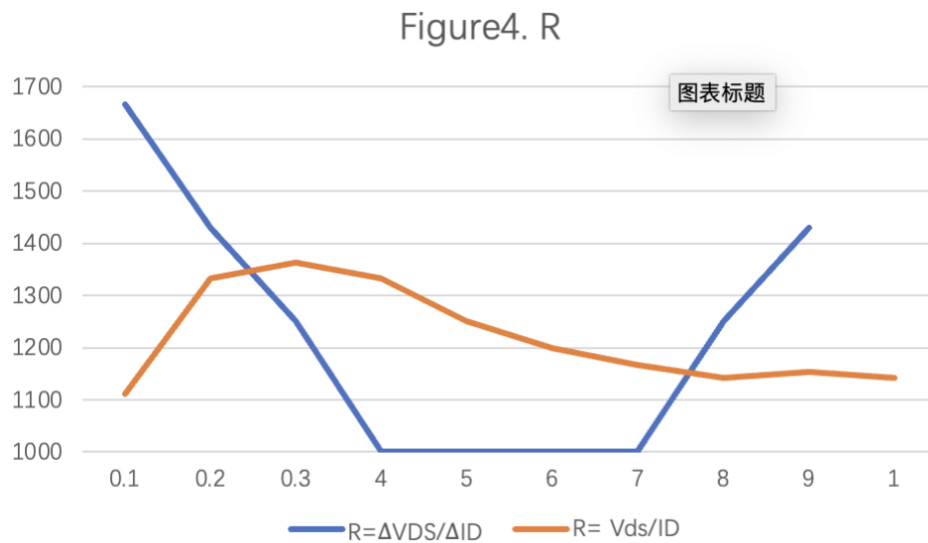This is the line chart of the V_{DS} from 3 to 4, step by 0.1



This is the line chart of the V_{ds} from 0 to 1, step by 0.1

Comment: In the second module, I measured the change of the resistance from 0 to 1 and from 3 to 4 with the method of 0.1 per step. I found that the resistance calculated by using the potential difference was different from the resistance calculated by dividing the total voltage drop by the total flow current.

Lab1 Summary:

In this experiment, I first completed the circuit connection, and then used the ammeter and voltmeter to measure the data I needed, and then made the calculation.

Through this experiment, I had a deeper understanding of the three regions of FET. During the experiment, I found that certain errors may occur in data reading and calculation, and wrong circuit connection may lead to short circuit, which requires my further attention.

Conclusion: When $V_{gs} < V_{th}$, cut-off area. When $V_{gs} > V_{th}$ and $V_{ds} < V_{GS} - V_{TH}$, the variable resistance region. When $V_{gs} > V_{th}$ and $V_{ds} > V_{GS} - V_{TH}$, the saturated region (constant current region).

That's all, thank you!

832002117 20122161 Hanlin Cai