


EE204FZ  
Lecture 6  
Models & Biasing  
Supplementary Information

Zhu DIAO


Email: [zhu.diao@mu.ie](mailto:zhu.diao@mu.ie)

# Typical Biasing Schemes for MOSFETs


Fixed biasing

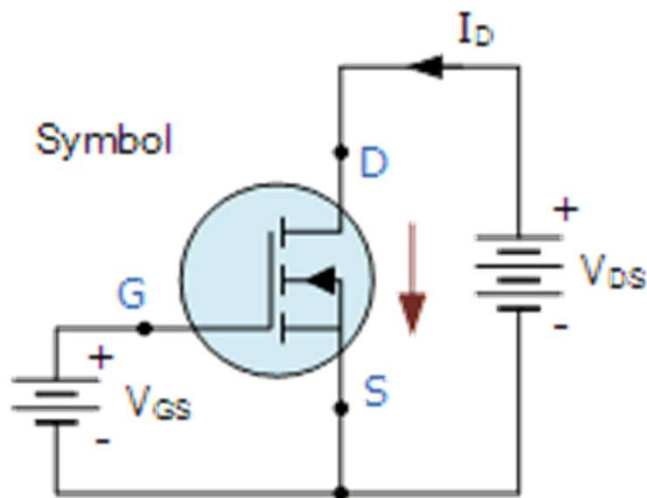

Voltage-divider biasing

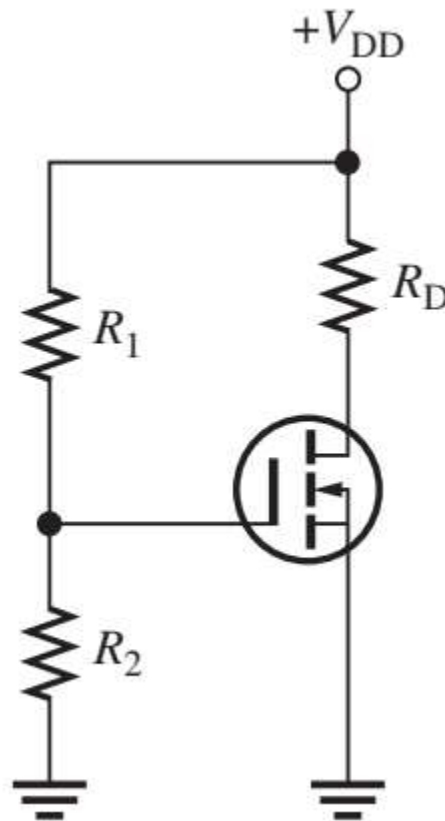

Drain-feedback biasing

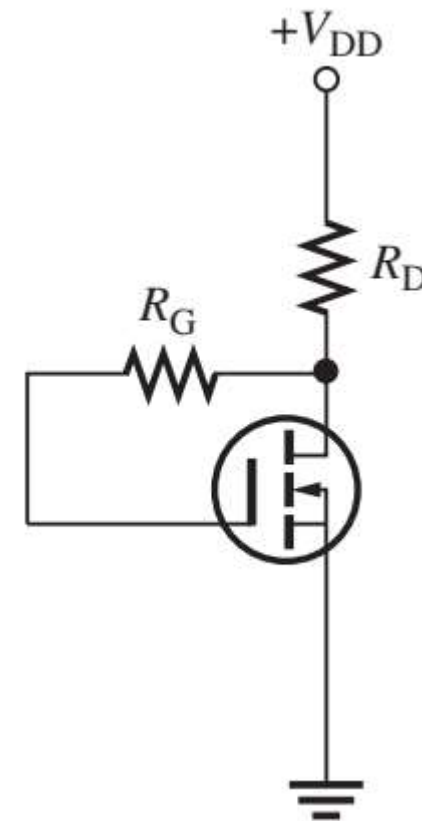

# Small Signal?

- Capacitors can be used to decouple the DC bias.

