


## Tutorial Sheet 5 – Sequential Logic & Flipflops

1. It is shown in the notes how the operation of a synchronous SR flipflop can be expressed using a state diagram. In a similar manner, use a state diagram to express the operation of each of the D, JK and T flipflops.

JK-ff

T	JK	Q	Q(1)
0	0 0	0	0
0	0 1	0	1
0	1 0	1	0
0	1 1	1	1
1	0 0	0	0
1	0 1	0	1
1	1 0	1	0
1	1 1	1	1


	J	K
stay at 0	0	X
"	X	0
go to 0	X	1
"	1	X

 

2. Derive the next state equation for the D and T flipflops.

T-ff  $\Rightarrow$  JK


T	J	K	Q	Q(1)
0			0	0
1			0	1
0			1	0
1			1	1

 






$$Q(1) = T\bar{Q} + \bar{T}Q$$

 3. Illustrate how the SR flipflop can be modified to obtain a D, JK and T flipflop respectively.





skip, find solution in the note / recorded lecture



    
 
4. Complete the following timing diagrams given that the devices in question are positive edge-triggered flipflops. Assume that the output starts in a LOW state.



   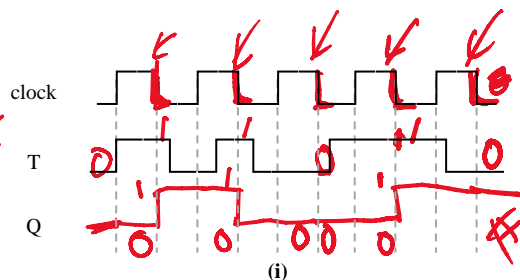5. Repeat Q4, given that the devices in question are negative edge-triggered flipflops.



  6. Repeat Q4 for parts (iii) and (iv), given that the devices are latches and that the clock signal is now an enable signal in each case.



#  
note

7. It is shown in the notes how a single D flipflop can be used to obtain the *divide-by-2* function. Draw out a circuit diagram, using D flipflops, to obtain a *divide-by-8* function. Provide a timing diagram (i.e. input and output waveforms) to illustrate the actual operation of your circuit.

