

---


### 3. Boolean Minimisation Using Boolean Algebra

- Boolean algebra provides a concise way to express the operation of a logic circuit formed by the combination of logic gates so that the output can be determined for various combinations of the input values.
- Before we consider how to use Boolean algebra to minimise a logic circuit, let us first consider how to analyse a circuit.


 
#### 3.1 Boolean Analysis of Logic Circuits

- Consider the following circuit with inputs A, B, C and D and output f. Intermediate variables X and Y have been added for convenience.



- We can obtain a Boolean expression for this circuit as follows. Writing out an expression for each of the gate outputs f, Y and X, we get:

$$f = DY$$


$$Y = C + X$$

$$X = AB$$

- Combining these three expressions, we obtain the following Boolean expression relating the output f to the inputs A, B, C and D:

$$f = D(C + AB)$$

 - **Ex. 3.1** Obtain a Boolean expression for the following circuit:



- 
- 
- Once we have obtained a Boolean expression for a logic circuit, it is possible to construct a truth table from this expression.
  - To do this, we can take every combination of the inputs and determine the corresponding output using the Boolean expression. For example, consider the expression:

$$f = D (C + AB)$$

- Taking the combination of ABCD = 0000, we can determine f as follows:

$$AB = 0.0 = 0 \quad (\text{i.e. } 0 \text{ AND } 0 = 0)$$

$$C + AB = 0 + 0 = 0 \quad (\text{i.e. } 0 \text{ OR } 0 = 0)$$

$$f = D (C + AB) = 0.0 = \mathbf{0}$$

- We can repeat this for all 16 combinations of ABCD. Note that we can also determine this output directly from the logical circuit.
- Alternatively, and a quicker method, is to use the Boolean expression to simply find the values of the variables that make the expression equal to 1.
- Thus, for  $f = D (C + AB) = 1$  we can deduce that:

$$D = 1 \text{ and } C + AB = 1$$

*(both inputs in an AND gate = 1 if the output = 1)*

- Now for  $C + AB = 1$ :

$$C = 1 \text{ and / or } AB = 1$$

*(refer to the truth table of the OR gate)*

- And for  $AB = 1$ :

$$A = 1 \text{ and } B = 1$$

- So, overall, we can state that:

$$f = D (C + AB) = 1 \quad \text{when:}$$

$$\mathbf{D = 1 \text{ and } C = 1 \text{ regardless of A and B}}$$

and

$$\mathbf{D = 1 \text{ and } A = 1 \text{ and } B = 1 \text{ regardless of C}}$$

All other combinations result in  $f = 0$ .

- Hence, we can complete the truth table as follows:


A	B	C	D	$f = D(C + AB)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

- Exercise – determine the truth table for the circuit in Ex 3.1.*
- We are now going to look at the laws, rules and theorems of Boolean algebra that can be used to simplify general Boolean expressions.
 
## 3.2 Boolean Algebra – Rules and Theorems

- The following Boolean rules and theorems are useful:

$$\begin{array}{ll}
 \left. \begin{array}{l} A + 0 = A \\ A + 1 = 1 \\ A + \bar{A} = 1 \\ A + A = A \end{array} \right\} & \text{properties of the OR gate} \\
 \\
 \left. \begin{array}{l} A \cdot 0 = 0 \\ A \cdot 1 = A \\ A \cdot \bar{A} = 0 \\ A \cdot A = A \end{array} \right\} & \text{properties of the AND gate} \\
 \\
 \left. \begin{array}{l} \bar{\bar{A}} = A \end{array} \right\} & \text{property of the NOT gate} \\
 \\
 \begin{array}{l} A + AB = A \\ A(\bar{A} + B) = A \\ A + \bar{A}B = A + B \end{array}
 \end{array}$$



- The commutative, associative and distributed laws can also be applied as follows:

$$\left. \begin{array}{l} A + B = B + A \\ A.B = B.A \end{array} \right\} \textbf{Commutative} - \text{order of variables does not matter when using the AND and OR operations}$$

$$\left. \begin{array}{l} A (BC) = (AB) C \\ A + (B + C) = (A + B) + C \end{array} \right\} \textbf{Associative} - \text{the result of applying an operation over 3 variables is not affected by the order taken}$$


$$\left. \begin{array}{l} A (B + C) = AB + AC \\ (A + B)(A + C) = A + BC \end{array} \right\} \textbf{Distributive} - \text{certain operations can be combined in different ways to give the same result, as shown}$$

- Finally, and most importantly, we have **De Morgan's theorems**, as follows:

$$\overline{A + B} = \overline{A} . \overline{B}$$

$$\overline{A.B} = \overline{A} + \overline{B}$$

 - The first theorem states that complement of a sum of variables is equal to the product of the complement of the variables.
- The second theorem states that complement of a product of variables is equal to the sum of the complement of the variables.
- These theorems extend to any number of variables.
- Visually, we can illustrate these theorems as follows:



- We will examine these theorems in more detail when we look at NAND and NOR implementation.
- All the aforementioned rules and theorems can be used to minimise Boolean expressions.

---

*Aside – some proofs ...*

- Show that  $A + AB = A$
- Show that  $A(A + B) = A$
- Show that  $A + \overline{A}B = A + B$
- Show that  $(A + B)(A + C) = A + BC$

### 3.3 Boolean Algebra – Minimisation

- In this section we will use the various rules, laws and theorems of Boolean algebra to simplify and minimise general Boolean expressions.
- It is important to minimise Boolean functions as this often leads to a reduction in the number of gates and/or inputs required.
- For example, consider the following function:

$$f = AB + A(B + C) + B(B + C)$$

- As it stands, this requires 5 gates – *can you work out what gates these are?*



Clarify



Simplify




Implement

- We can minimise this function as follows:

$$\begin{aligned}
 & AB + A(B + C) + B(B + C) \\
 &= AB + AB + AC + BB + BC && \text{(distribution)} \\
 &= AB + AC + B + BC && (X + X = X; \quad X.X = X) \\
 &= B(A + 1 + C) + AC && \text{(note } X = X.1) \\
 &= B + AC && (X + 1 = 1)
 \end{aligned}$$

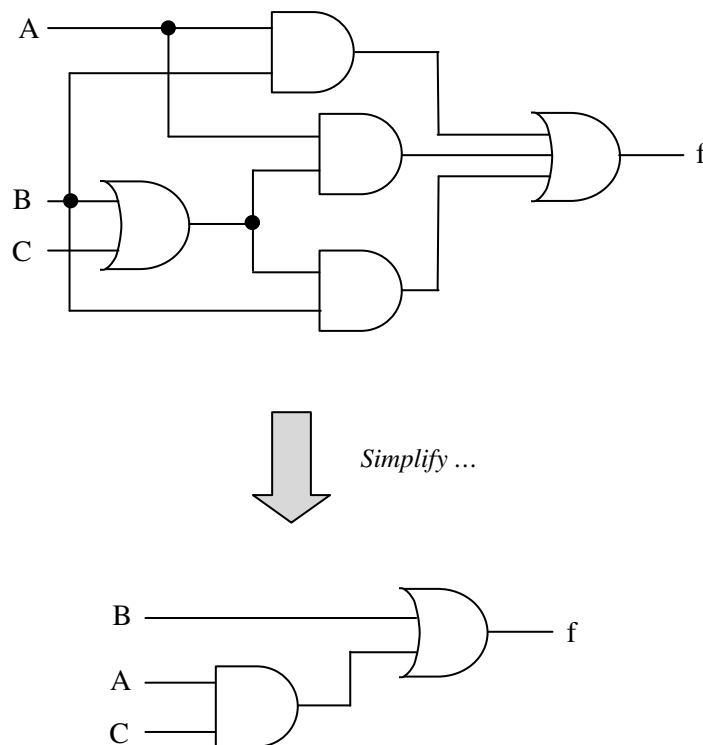- Now, this simplified expression,  $f = B + AC$ , only requires 2 gates.
- Visually, we can illustrate the obvious reduction in gates by looking at the circuit before and after simplification:



- Clearly there is a reduction in gates (from 5 to 2). However, it is also worth noting that we now only need to use 2-input gates, whereas the first circuit required a 3-input OR gate.
- In general, we multiply out and collect common terms, as we do when simplifying ordinary algebraic expressions.
- In some cases, we need to add in additional terms (without changing the function) in order to make the minimisation process easier.



- 
- **Ex. 3.2** Minimise the following logic function:

$$f_{(A,B,C)} = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

Can we reduce this further?

We know that  $X + YZ = (X + Y)(X + Z)$ . Hence:

- Here is an *alternative solution* to the same problem:

- *Note:* In this instance, adding an extra term resulted in a much easier solution.

- **Ex. 3.3** Minimise the following logic function:

$$f_{(X,Y,Z)} = XY + \bar{X}Z + YZ$$

- 
- *Ex. 3.4 Write out the Boolean function represented by the following truth table and hence obtain a minimal Boolean expression:*

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Two key limitations of the Boolean algebraic approach are:
  - (i) procedures are difficult to apply systematically and
  - (ii) it is difficult to determine the optimum solution.
- The task is greatly simplified by visualising the Boolean functions using **Karnaugh Maps**.