

Analogue Electronics 1 (EE204FZ)

Tutorial 2

Q1. Circle the correct answer.

1. A certain depletion-type MOSFET is biased at $V_{GS} = 0$ V. Its datasheet specifies $I_{DSS} = 20$ mA and the value of the drain current _____.

- A. 0 A
- B. cannot be determined
- C. 20 mA
- D. very high

2. The effective channel length of an n-channel MOSFET in saturation decreases with an increase in _____.

- A. drain voltage
- B. gate voltage
- C. source voltage
- D. body voltage

3. The main advantage of CMOS is its _____.

- A. high power rating
- B. lower power consumption
- C. small signal operation
- D. switching capability

4. Which of the following statements on using MOSFETs as resistors is NOT true? _____.

- A. Device resistance can be voltage controlled
- B. In the triode region ($V_{GS} > V_T$ and V_{DS} is small), MOSFETs can be used as adjustable resistors with high resistance values

Low

- C. MOSFET resistors usually have smaller footprints than other on-chip resistors
- D. MOSFET resistors can be very precise

5. When an input signal reduces the channel size of a MOSFET, the process is called _____.

- A. gate charging
- B. enhancement
- C. substrate connecting
- D. depletion

Q2. Answer the following questions.

1. How would you create a small and voltage controllable resistor using a MOSFET? State the two advantages of this device.

2. Figure Q2 shows a circuit implementation of an inverter using MOSFETs. Explain its operation. In your explanation, explain why the use of MOSFETs can lead to a very power efficient implementation for logic gates.

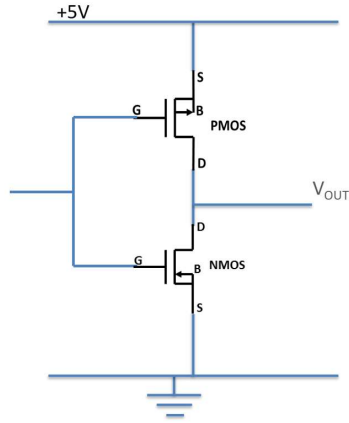


Fig. Q2

Q3. Determine in which mode (depletion, enhancement or neither) each depletion-type MOSFET in Fig Q3 is biased. Explain your reason briefly.

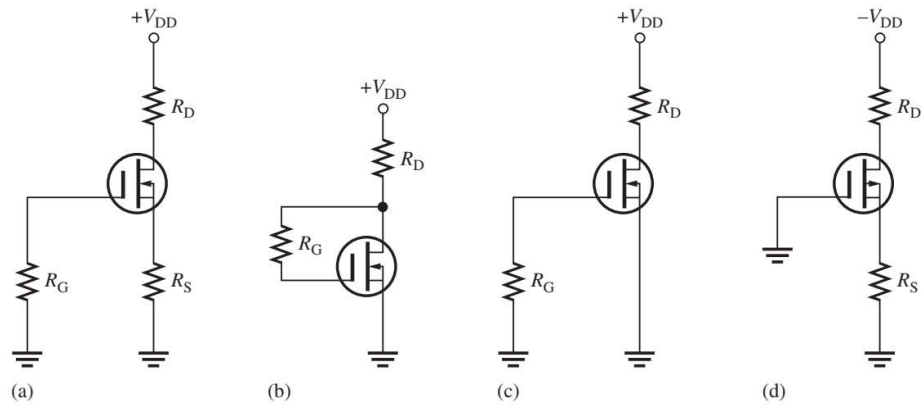


Fig Q3

Q4. An enhancement-type PMOS transistor in Fig Q4 has $\mu_p C_{ox}(W/L) = 80 \mu A/V^2$, $|V_T| = 1.5 V$ and $|\lambda| = 0.02 V^{-1}$. The gate is connected to ground and the source to $+5 V$. Find the drain current for $V_D = +4 V, +1.5 V, 0 V$, and $-5 V$.

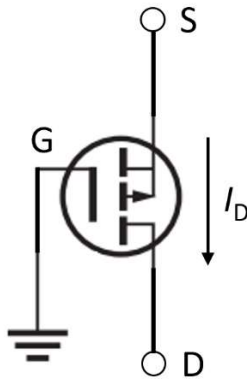


Fig Q4

Q5. The MOSFET circuit shown in Fig Q5 uses a MOSFET with $\mu_n C_{ox}(W/L) = 250 \mu\text{A}/\text{V}^2$, $V_T = 0.5 \text{ V}$. For $R = 100 \text{ ohm}$ and $V_{DD} = +5 \text{ V}$, solve MOSFET's device current and drain voltage, and indicate whether the device is operating in the saturation region or the triode region.

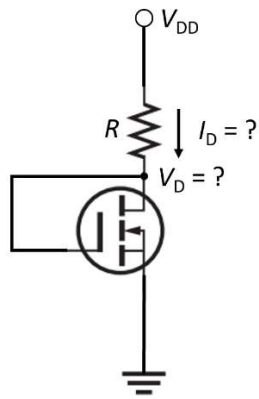


Fig Q5