

Tutorial Sheet 2 – Boolean Algebra & Minimisation

1. Express each of the following Boolean expressions in a minimal Sum of Product (SOP) form. Draw out the resulting logic circuit in each case.

(i) $A(B + C)$ (ii) $A + (BC)(C + \overline{D})$ (iii) $(AB)(\overline{B + C})(D + E)$

2. Show that the following expressions are equivalent:

(i) $X + \overline{X}YZ = X + YZ$


(ii) $(P + Q)(P + R) = P + QR$

(iii) $\overline{C}E + E(A + \overline{B}) + C = C + E$


(iv) $AB + B(B + \overline{C}) + \overline{B}C = B + C$

3. Obtain a Boolean expression for each of the following circuits and simplify where possible. Express your final answer as in SOP form.


(i)

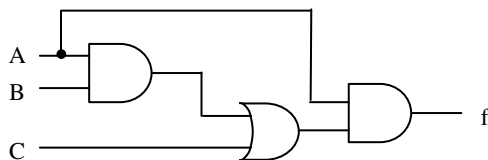


(ii)

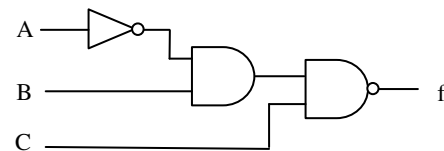

(iii)

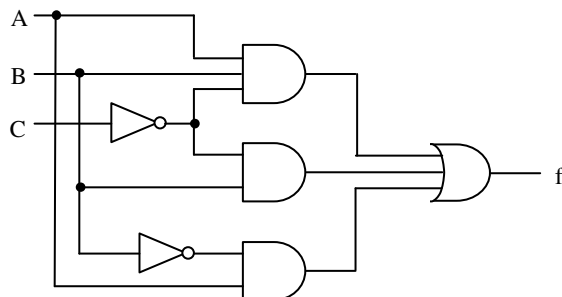

(iv)

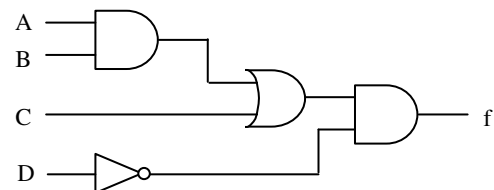

4. Obtain a minimal SOP Boolean expression for each of the following truth tables:

(i)

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(ii)

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

5. Simplify the following expressions using Boolean algebra:

(i) $WXYZ (WXYZ + W\bar{X}YZ + \bar{W}XYZ + WX\bar{Y}Z)$

(ii) $AB + AB\bar{C}D + AB\bar{D}\bar{E} + AB\bar{C}\bar{E} + \bar{C}DE$

(iii) $uvw + \bar{y}\bar{x}\bar{v} + xzu + \bar{y}wu\bar{x} + uz$

ANSWERS

1. (i) $AB + AC$ (ii) $A + BC$ (iii) $ABCD + ABCE$

3. (i) $AB + AC$ (ii) $A + \bar{B} + \bar{C}$ (iii) $A\bar{B} + B\bar{C}$ (iv) $AB\bar{D} + CD$

4. (i) $\bar{A} + B$ (ii) \bar{C}

5. (i) 0 (ii) $AB + \bar{C}DE$ (iii) $uvw + \bar{y}\bar{x}\bar{v} + uz$