

Name: Hanlin Cai

Student Num: 832002117 Or 20122161

Q1

D C B D A

Q2

(1)

Based on the majority charge carriers, the MOSFETs can be divided into NMOS and PMOS. NMOS use N-type material and PMOS use P-type material as channel.

The characteristics of NMOS, V_{gs} greater than a certain value will be turned on, suitable for the source grounding situation (low-end drive). The characteristics of PMOS, V_{gs} less than a certain value will be turned on, suitable for the source of VCC (high-end drive).


(2)

Pinch off regions (when $V_{GS} > V_T$): there is no current through the c

Linear Region (when $0 < V_{DS} < V_{GS} - V_T$): Its properties are similar to Ohm's law. The current is approximatively linearly dependent on V_{DS} .

Saturation region (When $V_{DS} > V_{GS} - V_T$): no more current should ideally flow. In practice, the current will approximate a steady constant current.

Q3

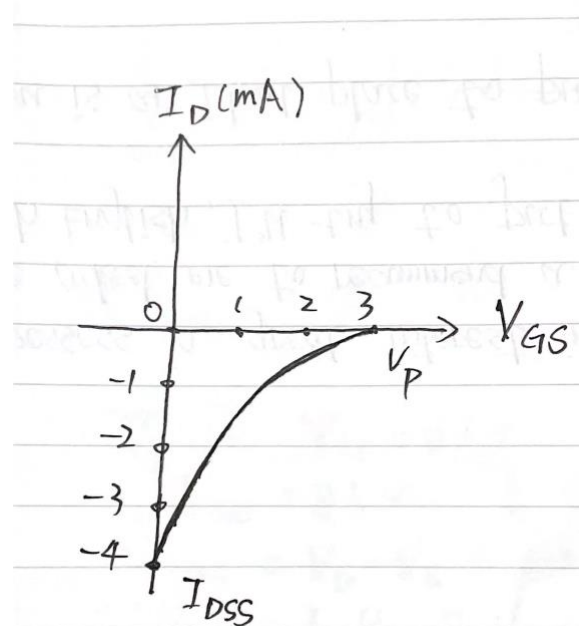

Q4

Q4. sol.

$$I_D = K (V_{GS} - V_{GS(th)})^2 \quad (1)$$

$$I_D = 3 \text{ mA} \quad V_{GS} = 4 \text{ V} \quad V_{GS(th)} = 2 \text{ V}$$

$$\text{So } K = 7.5 \times 10^{-4}$$

$$V_G = 10 \text{ V} \cdot \frac{4 \text{ k}\Omega}{14 \text{ k}\Omega} \approx 3.2 \text{ V}$$

$$\therefore V_{GS1} = 3.2 \text{ V} \quad (2)$$

$$I_{D1} = K (V_{GS1} - V_{GS(th)})^2 \quad (3)$$

$$\therefore I_{D1} = 1.1 \text{ mA}$$

$$\therefore V_{DD} - I_{D1} R_D = V_{D1} \quad (4)$$

$$\therefore V_{D1} = 8.9 \text{ V}$$

$$V_{DS} = V_{D1} - V_S \quad (5)$$

$$\text{So } V_{GS} = 3.2 \text{ V}$$

$$V_{DS} = 8.9 \text{ V}$$

Q5

Q5. sol

$$V_S = 0 \quad V_G = 8.5 \text{ V} \quad (1)$$

$$\therefore V_{GS} = 8.5 \text{ V} \quad V_D = 8.5 \text{ V} \quad (2)$$

$$\therefore V_{DS} = V_D - V_S = 8.5 \text{ V}$$

$$\therefore V_{DD} - I_D R_D = V_D$$

$$\therefore I_D = 1.4 \text{ mA}$$

$$\text{So } V_{DS} = 8.5 \text{ V}$$

$$I_D = 1.4 \text{ mA}$$