

## 5. Implementation Using NAND / NOR Gates

### 5.1 Universal Gates


- NAND and NOR gates are often referred to as **universal gates** as they can produce the NOT, AND, OR, NAND and NOR operations.
- In order to understand how the NOT, AND and OR gates can be obtained, we need to compare their truth tables with those of the NAND and NOR gates.
- Recall that the truth tables of the NAND, NOR, AND and OR gates are as follows:



A	B	f	A	B	f	A	B	f	A	B	f
0	0	1	0	0	1	0	0	0	0	0	0
0	1	1	0	1	0	0	1	0	0	1	1
1	0	1	1	0	0	1	0	0	1	0	1
1	1	0	1	1	0	1	1	1	1	1	1
NAND			NOR			AND			OR		

 
#### NOT gate using NAND ...

- Examining the NAND truth table, it is clear that when both inputs are the same, the output is the complement of the inputs.
- Also, when one input is a logic '1' or HIGH, the output is then the complement of the other input.
- Thus, 2 possible NAND gate configurations can be used to generate a NOT gate as follows:


 
#### NOT gate using NOR ...


- By a similar analogy to above, there are also 2 possible NOR gate configurations can be used to generate a NOT gate as follows:



---

 
### AND gate using NAND ...

- Obtaining an AND gate using NAND is straightforward as we simply invert the output of the NAND gate, as follows:



 
### AND gate using NOR...

- By comparing the AND truth table and the NOR truth table we can derive the following NOR gate implementation for an AND operation:



 
### OR gate using NOR ...

- Obtaining an OR gate using NOR is straightforward as we simply invert the output of the NOR gate, as follows:


 
### OR gate using NAND ...

- By comparing the OR truth table and the NAND truth table we can derive the following NAND gate implementation for the OR operation:




## 5.2 Implementing Logic using NAND / NOR gates

- In practice, the NAND and NOR gates are regarded as the natural primitive gates of integrated circuit technology, used to implement the simplest and fastest electronic circuits.
- Furthermore, as we have just seen, NAND and NOR gates are ‘universal gates’ and can be used to implement any other gate or any Boolean expression.
- As such, these gates are the mostly widely used gates in the implementation of actual logic circuits.
- In general, when we carry out logic minimisation (using either Boolean algebra or Karnaugh Maps), we express the final solution in sum-of-products (SOP) form.
- This consists of a collection of AND, OR and NOT gates.
- We now want to implement such expressions using either NAND gates only or NOR gates only.
- De Morgan’s theorems is used to achieve the conversion between AND and OR and NAND and NOR. This is best illustrated using examples.
- Consider the implementation of the following function using a quad 2 input NAND Integrated Circuit (IC) (i.e. the IC contains four 2-input NAND gates):

$$f_{(A,B,C)} = \bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}C + ABC$$

 - Firstly, we need to minimise the function. This was done previously in *Ex. 4.2*, but we will provide the solution here again for the sake of convenience:



Hence:  $f = A + BC$

- This is an AND-OR solution. Now, we want to convert this to a NAND only solution.
- Using De Morgan’s theorem, we know that:

$$\overline{X + Y} = \bar{X} \cdot \bar{Y} \quad \text{or} \quad X + Y = \overline{\bar{X} \cdot \bar{Y}}$$



- 
- Hence:

$$f = A + BC = \overline{\overline{A} \cdot \overline{BC}}$$

- This is now a NAND-NAND solution and can be implemented as follows:

- Note that we have 3 NAND gates in total (the given IC had 4 available).
- Also note that one of the NAND gates is used to implement the NOT gate.
- Now, consider the implementation of the **same function** using a quad 2 input **NOR** Integrated Circuit (IC) (i.e. the IC contains four 2-input NOR gates):
- This time, we want a NOR only solution.
- Using De Morgan's theorem, we know that:

$$\overline{X \cdot Y} = \overline{X} + \overline{Y} \quad \text{or} \quad X \cdot Y = \overline{\overline{X} + \overline{Y}}$$

- Thus:


$$f = A + BC = A + \overline{\overline{B} + \overline{C}}$$

- This is currently a NOR-OR format.
- As we have seen already, the OR can be implemented using a NOR gate followed by an inverter, i.e.:

$$X + Y = \overline{\overline{X} + \overline{Y}}$$


- Hence, the NOR-NOR solution is:  $f = A + \overline{\overline{\overline{B} + \overline{C}}}$
- This particular solution requires a total of 5 NOR gates for implementation purposes (the IC only contains 4 NOR gates!).
- However, this is **not a minimal** NOR solution.

 - Let's revisit the Karnaugh Map, **group the zeros instead** and see what we get:



- This gives:  $\bar{f} = \bar{A}\bar{B} + \bar{A}\bar{C}$
- Using De Morgan's rule, we get:  $\bar{f} = \overline{(A + B)} + \overline{(A + C)}$
- Inverting both sides:  $f = \overline{\overline{(A + B)} + \overline{(A + C)}}$
- Once again, we have a NOR-NOR solution, but this time we only require 3 gates as follows:

- In general, if we are looking for a NAND gate solution then we group the 1's in a Karnaugh Map.
- In general, if we are looking for a NOR gate solution then we group the 0's, as we have already seen.
- However, this does not ensure a minimal solution in either case.
- If we require a **minimal solution** (either NAND or NOR), we need to **examine grouping both the 1's and the 0's in a Karnaugh Map** to see which one leads to the best solution.
- The next exercise will illustrate this concept.


 


- *Ex. 5.1 Obtain a minimal NAND and a minimal NOR implementation for the following function:*

$$f_{(A,B,C,D,E)} = \sum(0, 1, 2, 4, 5, 8, 10, 12, 16, 17, 18, 20, 21, 24, 26, 28)$$



*given that the complemented input variables (i) are available and (ii) are NOT available.*

*Grouping 1's ...*

  

This gives:

*Grouping 0's ...*

  

This gives:

---

*NAND solutions:*

#1:

Applying De Morgan's gives:

This requires 4 NAND gates for (i) and requires 8 NAND gates for (ii).

#2:

Applying De Morgan's gives:

This requires 5 NAND gates for (i) and also requires 5 NAND gates for (ii).

Hence the **minimal NAND solution for (i)** is:

And the **minimal NAND solution for (ii)** is:

*NOR solutions:*

#1:

Applying De Morgan's gives:

We now need to convert from OR to NOR:

This requires 5 NOR gates for (i) and also requires 5 NOR gates for (ii).

#2:

Applying De Morgan's gives:

This requires 4 NOR gates for (i) and requires 8 NOR gates for (ii)

Hence the **minimal NOR solution for (i)** is:


And the **minimal NOR solution for (ii)** is:

- **Ex. 5.2** The output of a circuit containing 4 inputs is high when any three of the inputs are high, otherwise the output is low.
  - Derive a minimal sum-of products function for this circuit.
  - Implement this function using no more than 5 NAND gates. Draw out your final circuit.

 (i) We could fill out a truth table and then transfer this to a Karnaugh Map to obtain the solution.

Alternatively we can write down all valid combinations as follows:

Put this expression into a Karnaugh Map and simplify as follows:



Hence:

(ii) We are not required to get a minimal solution in this case. Hence, we should group the 1's first for a NAND solution. If this doesn't meet the criteria, then and only then do we consider grouping the 0's in the Karnaugh Map.

Grouping 1's gives us:

Applying De Morgan's:

This requires 5 NAND gates which satisfies the given criteria.

The final circuit is:

