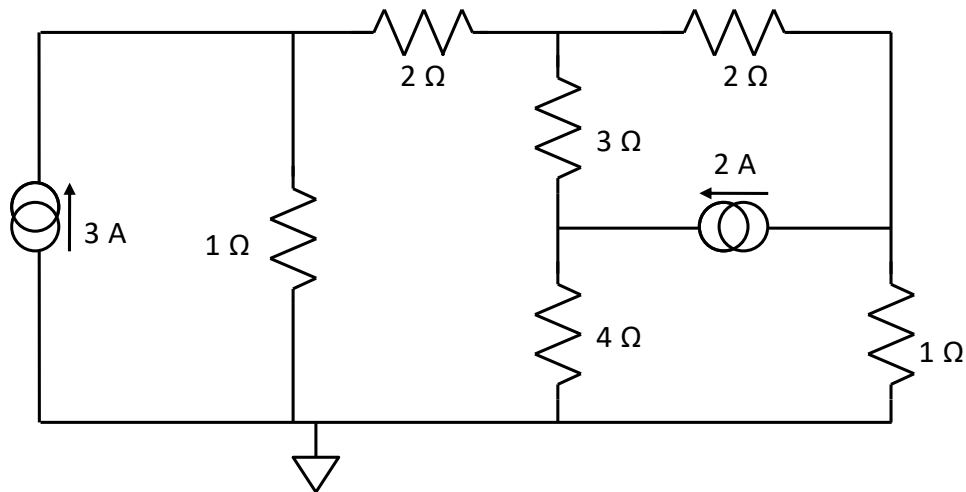



Electronics Engineering Fundamentals Tutorial Sheet - 3

Solving More Complex Circuits

Question A: Using an appropriate technique, generate the equations that will provide the currents flowing in each part of this circuit. **NOTE: No marks will be given for solving the resulting simultaneous equations, so stop at that point.** However, all steps in your derivation of these equations must be clearly identified and explained or marks will be deducted.



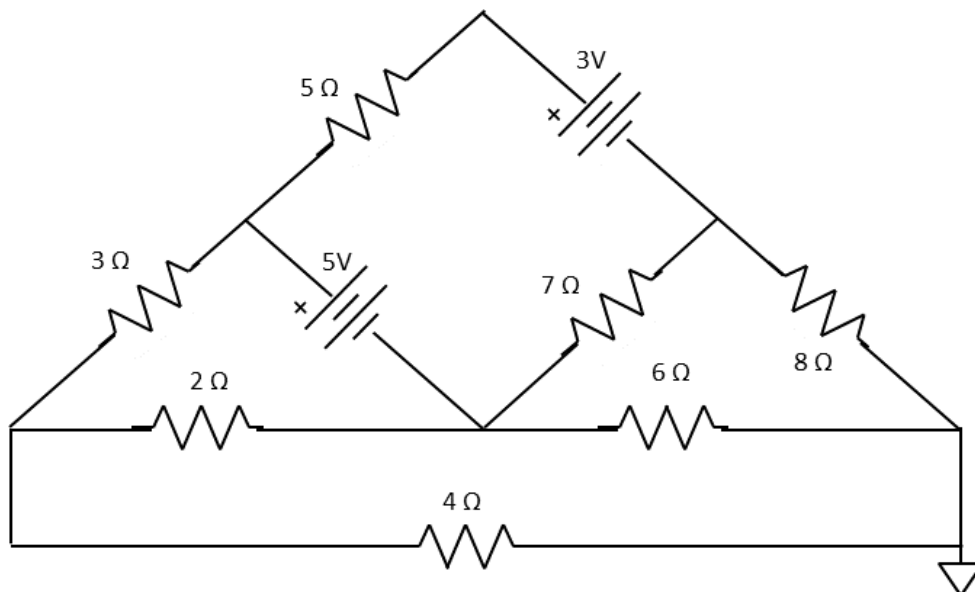
Question B: Using an appropriate technique, generate the equations that will provide the currents flowing in each part of this circuit. **NOTE: No marks will be given for solving the resulting simultaneous equations, so stop at that point.** However all steps in your derivation of these equations must be clearly identified and explained or marks will be deducted.



Electronics Engineering Fundamentals

Tutorial Sheet - 3

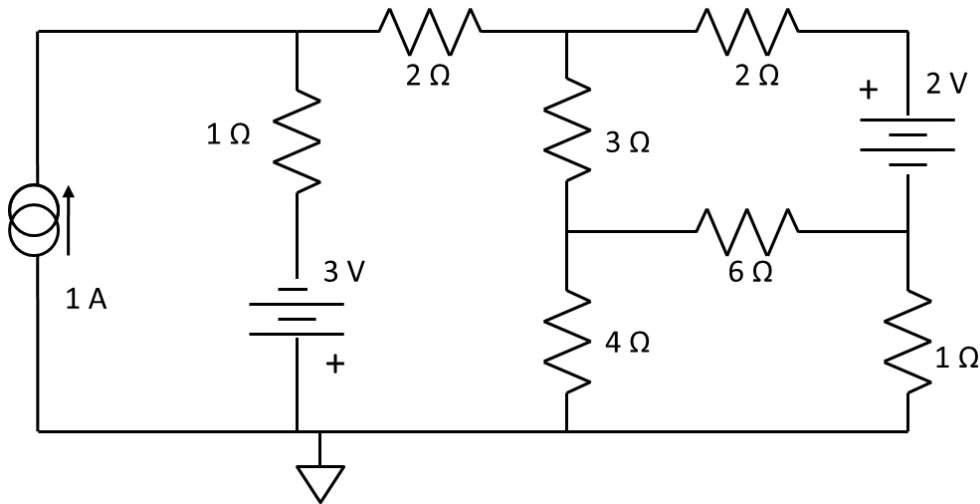Question C: Using an appropriate technique, generate the equations that will provide the currents flowing in each part of this circuit. **NOTE: No marks will be given for solving the resulting simultaneous equations, so stop at that point.** However all steps in your derivation of these equations must be clearly identified and explained or marks will be deducted.



Question D: Using an appropriate technique, generate the equations that will provide the currents flowing in each part of this circuit. **NOTE: No marks will be given for solving the resulting simultaneous equations, so stop at that point.** However, all steps in your derivation of these equations must be clearly identified and explained or marks will be deducted.

