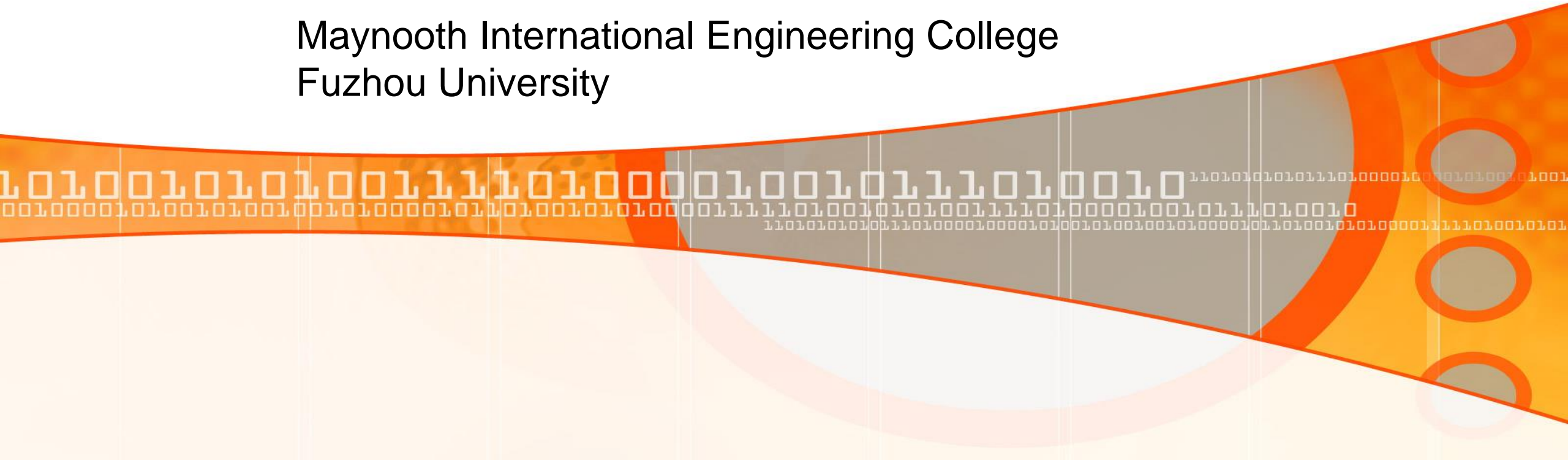


EE103 Digital Systems 1

Wong Chin Hong







106

Maynooth International Engineering College
Fuzhou University



EE103 - Learning Outcomes

At the end of this module, you will be able to:

1. Conduct basic arithmetic with binary numbers. ✓
 2. Perform Boolean algebra. ✓ 
 3. Minimise logic using Karnaugh Maps. ✓
 4. Implement a logic circuit using only NAND / NOR gates. ✓
-
5. Describe the operation of basic flip-flops. ✓
 6. Design a synchronous counter. ✓ 
 7. Distinguish between different programmable logic devices.
- 
- 
- 
- 

EE103 - Assessment Method

Assessment Type	Percentage	Week
Lab	10%	16 & 17
Tests	20%	17 18
Final Exam	70%	
100%		

x 2

Thursday.

Textbook:


- Mano, M. Morris, Digital design, (2nd ed.), Prentice-Hall, 1991.

EE103 - Assessment Method

2021 WEEKLY PLANNER – Indicative

EE103FZ Digital Systems 1

	Lecture / Tutorial		Lab
	Mon/Tue	Thu	
Week 14	Chapter 6	Chapter 6	
Week 15	Chapter 6	Chapter 7	
Week 16			Lab 3
Week 17			Lab 4
Week 18	Chapter 7	Chapter 8	
Week 19	Chapter 8	Test 2	
Week 20	Chapter 9	Chapter 9	
Week 21	Final Exam		

 

2021 WEEKLY PLANNER – Indicative

EE103FZ Digital Systems 1

	Lecture / Tutorial		Lab
	Mon/Tue	Thu	
Week 14	Chapter 6	Chapter 6	
Week 15	Chapter 6	Chapter 7	
Week 16	Chapter 7	Chapter 8	Lab 3
Week 17	Chapter 8	Test 2	Lab 4
Week 18	Chapter 9	Chapter 9	
Week 19	Final Exam		
Week 20			



EE103 - Module Detail

- 22 – lectures, tutorials (13 completed)
- (2 x 1 hr) Class tests (1 completed)
- 12 hours of laboratories (4 x 3hr) ... to start later in the semester (2 completed)
- 70% for final exam, 10% for labs & 20% for class tests.

EE103 – Some Advice

- Be punctual to class.
- Participate in class discussion.
- Pay attention when the lecturer is talking in front.
- No playing hand phone during class.

EE103 – Some Advice


- Check your emails, Teams announcement and chat regularly
- Check Moodle (EE103 module)
- Ask plenty of questions – *before, during and after class!*
- Study hard, but have fun also 😊

So ...

Let's begin ...

So far ... !

 
- We've introduced the concept of Karnaugh Maps and used these to minimise logic ...
- We've looked at implementing logic circuits using NAND only or NOR only gates ...



NOW, we are going to introduce Sequential Logic and look at Flipflops ...


Sequential Logic

- **Combinational logic** is where the output of a digital circuit is produced by combining the inputs in a manner defined by the logic.
- Until now, all our circuits have been based on combinational logic only.
- However many digital systems contain sequential logic.
- **Sequential logic** is where the **output** of a digital circuit **depends on both the inputs and also on the previous output state** of the circuit.
- Such a system is described as *having memory* because it can remember its output state.

 

Sequential Logic

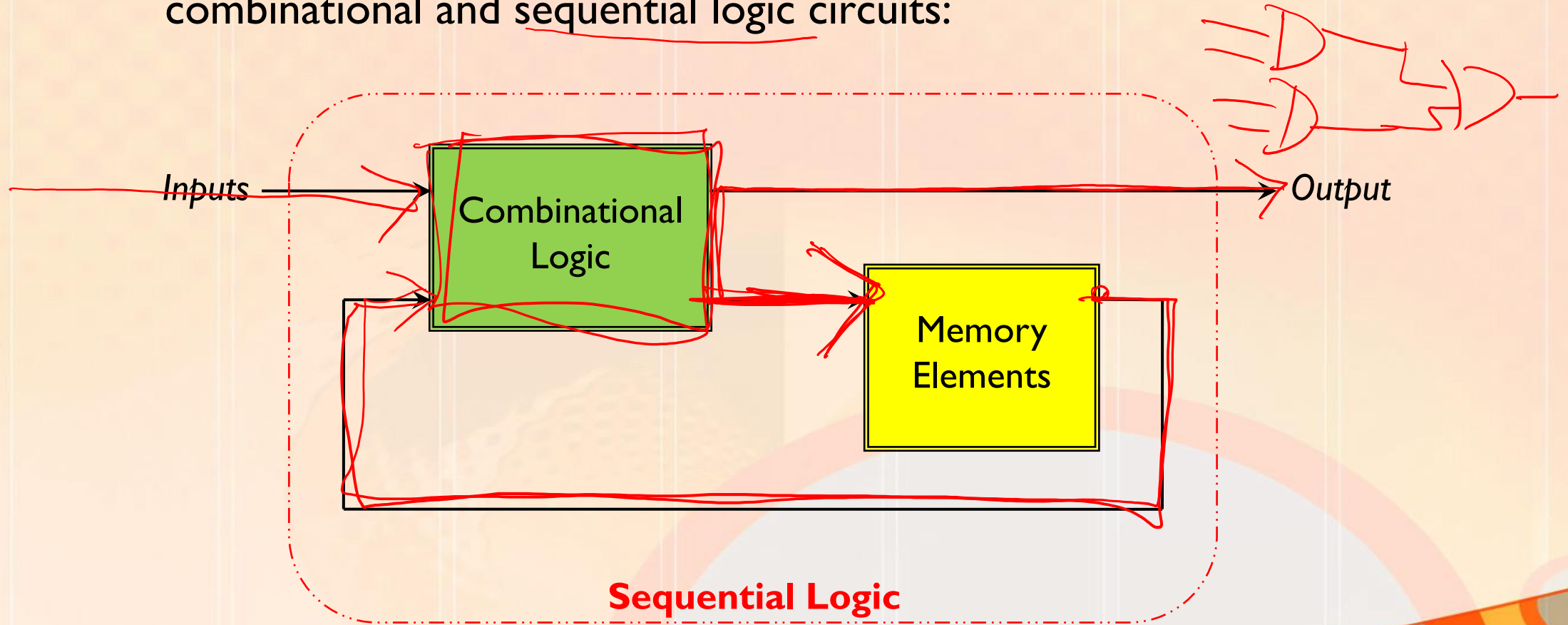- The following diagram illustrates the fundamental difference between combinational and sequential logic circuits:



Sequential Logic

- Sequential systems are categorised in two ways, namely synchronous and asynchronous.
- A **synchronous** sequential circuit is where its behaviour depends on knowledge of the inputs **at a discrete instant of time**, usually determined by a **clock**.

- An **asynchronous** sequential circuit is where its behaviour can be affected by changes in the input signals at **any instant of time**.

- One of the most basic but fundamental sequential circuit is the flip-flop, which is a bistable device, i.e. it settles in one of two possible states (typically SET and RESET).

0/1 set \rightarrow 1
0/1 \rightarrow 0

0 \rightarrow 0
1 \rightarrow 0
0 \rightarrow 1
1 \rightarrow 1

always
and output

Sequential Logic



- We are now going to look at four common types of flipflops, namely SR, D, JK and T.



Asynchronous SR Flipflop

- The following circuit represents a NAND implementation of an asynchronous SR flipflop:

X CLK

  


Asynchronous SR Flipflop

- The circuit has two inputs S and R and two outputs Q and \overline{Q} . Note how the outputs are both fed back to act as inputs to the NAND gates.
- Recall, once again, the truth table of the NAND gate as follows:

A	B	f
0	0	1
0	1	1
1	0	1
1	1	0

A	f	
0	1	Disabled
1	\overline{B}	Enabled

 

Asynchronous SR Flipflop

- We can work out the next output $Q(\tau)$ of the SR circuit for all combinations of the inputs S, R and **Q** (the previous output).
- This is similar to the truth table approach for combinational logic circuits, but we now refer to the table as a **state table**.
- Let's examine the circuit in relation to each combination of inputs in turn ...

tau

NAND


*current
Q*

*next
Q(τ)*

output

Asynchronous SR Flipflop

- Let **S = 0** and **R = 0** ...

 


$Q \neq \bar{Q}$
1 \rightarrow 0
0 \rightarrow 1
1 \times 1
0 \times 0

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0


Asynchronous SR Flipflop

- Let $S = 0$ and $R = 1$...

 

Asynchronous SR Flipflop

- Let $S = 1$ and $R = 0$...

 


0	0	1
0	1	1
1	0	1
1	1	0

Q(t)

Asynchronous SR Flipflop


- Let $\underline{S = 1}$ and $\underline{R = 1} \dots$

Set $Q \Rightarrow 0/1$

 

0	0	1
0	1	1
1	0	1
1	1	0

 - Thus, by taking each combination of the inputs, and working through the circuit, as we have done, we can derive the following **state table**:



- stay
- stay

Asynchronous SR Flipflop

- Thus, by taking each combination of the inputs, and working through the circuit, as we have done, we can derive the following **state table**:

S	R	Q	Q(τ)
0	0	0	-
0	0	1	-
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Handwritten annotations:

- Red curly braces on the right group rows:
 - Rows 1-2: Undefined
 - Rows 3-4: Q is Set to 1
 - Rows 5-6: Q is Reset to 0
 - Rows 7-8: Q stay
- Blue boxes around the next state values in the Q(τ) column: 1, 1, 0, 0, 0, 0, 0, 1.
- Blue circles around the current state values in the Q column for rows 3, 4, 5, and 6.
- Blue arrows pointing from Q to Q(τ) in the last two rows (rows 7 and 8).

Synchronous SR Flipflop

- As it stands, the previous design will react to change in the input **at any instant** of time, i.e. it is asynchronous.


X Time X CLK

- A synchronous version of the flipflop (i.e. one controlled by a clock) can be achieved through the addition of two NAND gates as follows:

✓ Time ✓ CLK



Synchronous SR Flipflop

 


Synchronous SR Flipflop

- Now, let us examine the operation of this circuit ...



Synchronous SR Flipflop

- If $S = 0$ and $R = 0 \dots$

 
$$\begin{array}{cc|c} & A & B \\ \hline 0 & 0 & \\ 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{array}$$

sync

SR	Q	Q(t)	SR	Q	Q(t)
0 0	0	0	1 0	0	1
	1	1		1	1
0 1	0	0	1 1	0	1
	1	0		1	1

Synchronous SR Flipflop

- Hence, we can derive the following **state table** for the **synchronous SR flipflop**:

Handwritten: Async

Handwritten: Sync

S	R	Q	Q(τ)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

Q

Q is Reset to 0

Q is Set to 1

Undefined

Synchronous SR Flipflop

- For convenience, we can also obtain a **concise form of the state table** as follows:

S	R	Q	Q(τ)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-



S	R	Q(τ)
0	0	Q
0	1	0
1	0	1
1	1	-

undefined.


undefined

Synchronous SR Flipflop

- The flipflop is SET by $S = 1, R = 0$ and is RESET by $S = 0, R = 1$ and hence the name SR flipflop.
- Note that the output values are only set when the clock is enabled, i.e. $\text{CLK} = 1$.
- When the clock is disabled (i.e. $\text{CLK} = 0$), the S_C and R_C are set to 1, thereby maintaining the previous output values. Any change in S and R will therefore not affect the output. *ignore*
- The circuit is now synchronous.

Synchronous SR Flipflop

 - The **standard symbol** for the flipflop is:



Synchronous SR Flipflop

- An alternative means for expressing the behaviour of the flipflop is in terms of a **requirements table**.



- This particular table is useful when we consider the design of counters later in this module.

$$Q \rightarrow Q(\tau)$$

- The requirements table basically defines the possible transitions between states. As we have only 2 possible states (or outputs), we thus have 4 possible transitions as follows:

GO from 0 to 1

GO from 1 to 0

STAY at 0

STAY at 1

Synchronous SR Flipflop

- By carefully analysing the state table, we can derive the following requirements table for the SR flipflop, where X represents don't care terms:

S	R	Q	Q(τ)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-



Operation	S	R
Stay at 0	0	X
Stay at 1	X	0
Go to 0	0	1
Go to 1	1	0