

The basic circuit analysis theorems



Introduction

Two important definitions:

Loop is any simple closed path in a circuit.

Mesh is a loop that doesn't have a closed path in its interior.

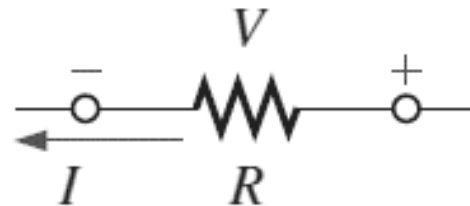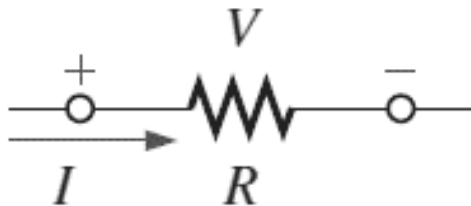And a reminder that the direction of current through a resistor will define the polarity of the voltage drop across the resistor:



MULTI-LOOP CIRCUIT ANALYSIS

Mesh/Loop Analysis

This is the systematic application of Kirchoff's Voltage Law

Step 1 Identify all loops (don't forget the outer loop)

Step 2 Identify what you want to learn

Step 3 Apply circuit simplification techniques to those parts of the circuits you do not care about

Step 4 Transform all current sources into their **equivalent voltage source form**

Step 5 Draw directions for the current in each loop. Label these currents (this is arbitrary as long as you stick with it).

Step 6 For each resistor in the loop, draw a +/- to indicate voltage drops. **Resistors always go + to- with current flow**, while batteries have their own signs.

Step 7 Express the voltage drops in terms of the loop current(s)


Step 8 Declare whether drops are positive or negative

Note that for ANY and ALL loops, **the algebraic sum of voltages must equal zero.**

This produces a set of simultaneous equations for each node. Solve the simultaneous equations (in any manner).

Multi-Loop Circuit Analysis

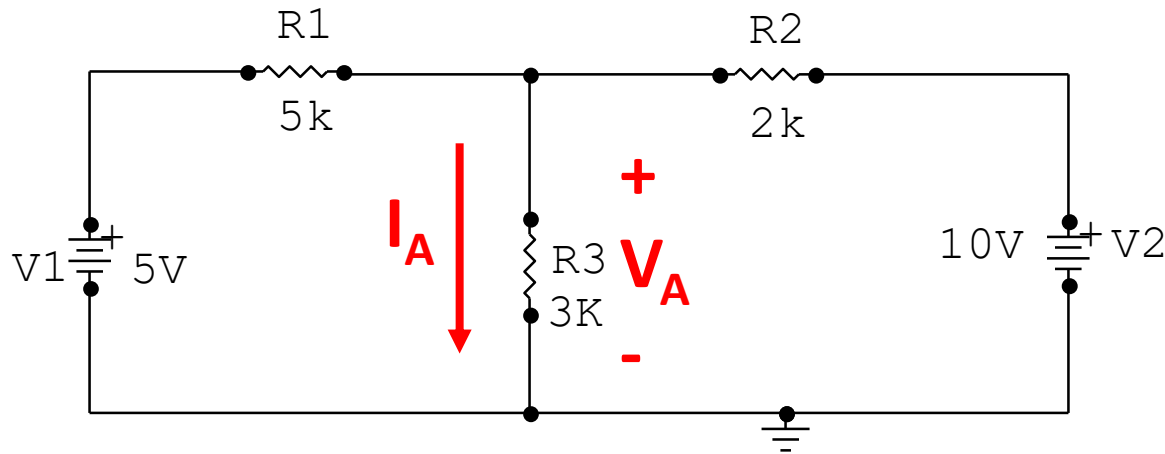Calculate the current I_A and the voltage (across R_3) V_A in the circuit below:



Ohms Law:

$$V=IR$$


Kirchoff's Current Law:

current is preserved at a node

Kirchoff's Voltage Law:

voltage in a loop sums to zero

Mesh Analysis - Example

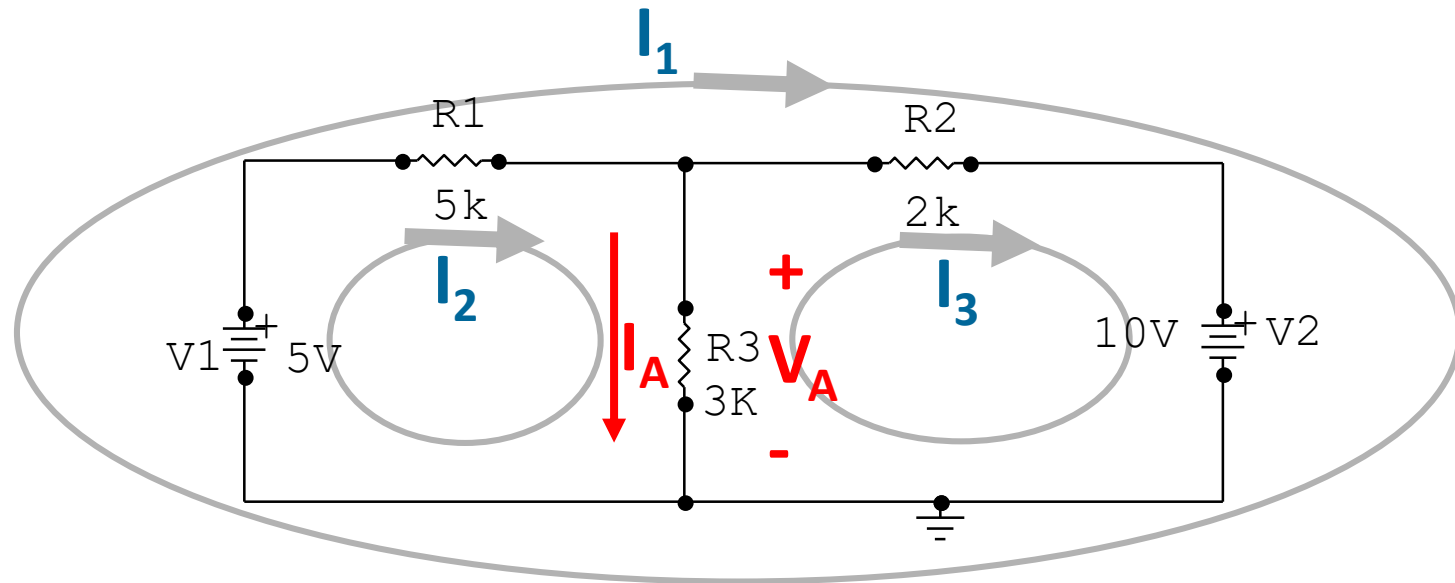

Step 1 Identify all loops: two inner loops, and one outer loop.


Step 2 Identify what you want to learn (I_A , V_A)

Step 3 Apply circuit simplification techniques to those parts of the circuits you do not care about

Step 4 Transform current sources into voltage sources: none

Step 5 Draw current directions


Mesh Analysis - Example

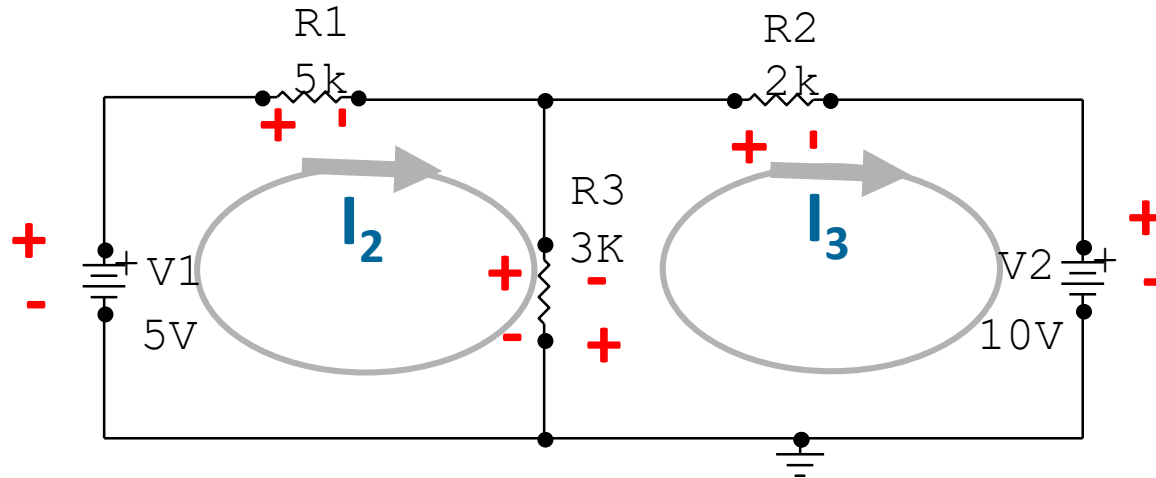

Step 6 Indicate Voltage Drops

- you only need to do the minimum set of loops provided that all elements are included in the loops you do select (I'll pick the two inner ones).
- nothing goes wrong if you do them all.. Just a little more work.

Mesh Analysis – Example

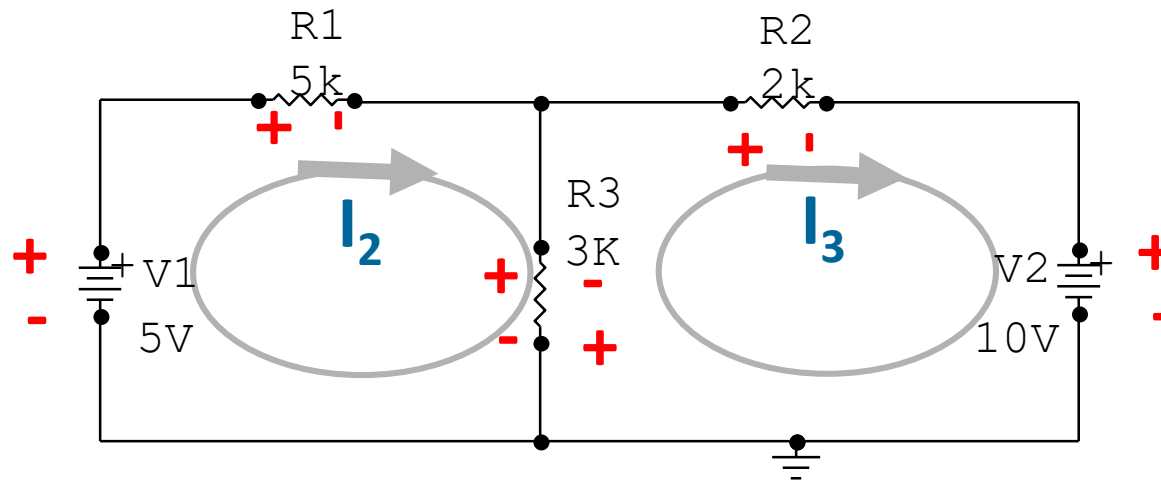

Step 7 Express the voltage drops in terms of the loop current(s).
Declare whether a drop is positive or negative

If I pick voltage drops as positive:

$$\text{Loop 2: } -V_1 + I_2 R_1 + (I_2 - I_3) R_3 = 0$$

$$\text{Loop 3: } +V_2 + I_3 R_2 + (I_3 - I_2) R_3 = 0$$


If I pick voltage drops as negative:

$$\text{Loop 2: } V_1 - I_2 R_1 - (I_2 - I_3) R_3 = 0$$

$$\text{Loop 3: } -V_2 - I_3 R_2 - (I_3 - I_2) R_3 = 0$$

Currents rotating in opposite directions in the same device... then we use the difference of the two currents for use in the device.

Mesh Analysis – Example

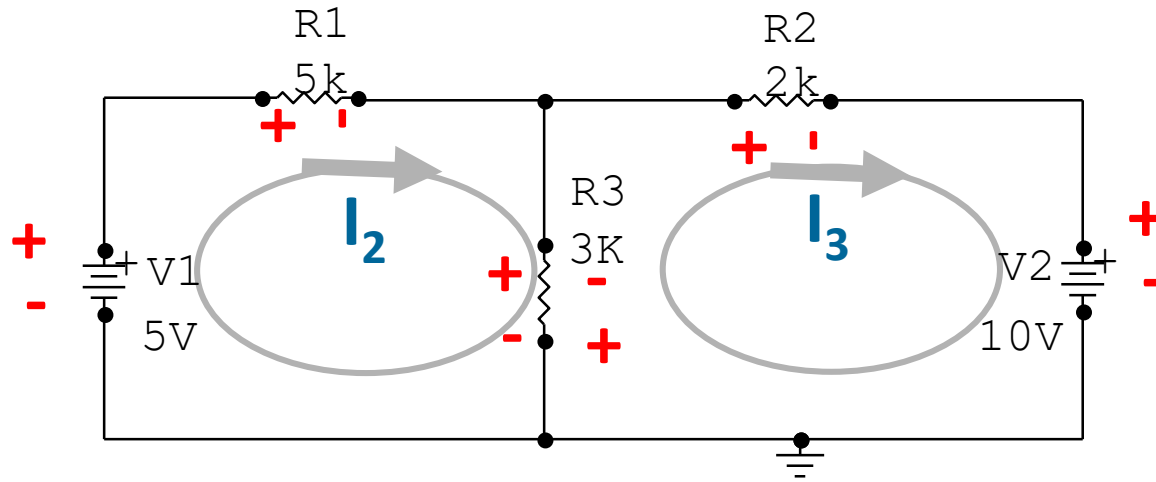

$$I_2 R_1 - (I_3 - I_2) R_3 = +V_1$$

$$+I_3 R_2 + (I_3 - I_2) R_3 = -V_2$$

Mesh Analysis – Example

Lets just use simultaneous equations (plug in numbers)

$$\begin{aligned}I_2 5000 - (I_3 - I_2) 3000 &= +5 \\+I_3 2000 + (I_3 - I_2) 3000 &= -10 \\8I_2 - 3I_3 &= +0.005 \\-3I_2 + 5I_3 &= -0.010\end{aligned}$$

Scale and cancel one variable, then get the other

$$\begin{aligned}8I_2 - 3I_3 &= +0.005 \\-3\left(\frac{3}{5}\right)I_2 + 5\left(\frac{3}{5}\right)I_3 &= -0.010\left(\frac{3}{5}\right) \\ \text{adding} & \\ \left(8 - \frac{9}{5}\right)I_2 - 00 &= +0.005 - 0.010\left(\frac{3}{5}\right) \\ I_2 &= -0.001\left(\frac{5}{31}\right) \\ I_3 &= -(0.0005 - 8I_2)/3\end{aligned}$$

**watch your
signs**

Mesh Analysis – Example

Now calculate the voltage and current through R3


Current through R3 from top-to-bottom is $(I_2 - I_3)$ as drawn on chart

$$I_2 - I_3 = (-0.161m) - (-2.097m) = +1.936mA$$

Voltage is current by resistance, direction is + at top, due to current direction

$$\begin{aligned} V &= IR = 3000 * 1.936mA \\ &= 5.808V \end{aligned}$$

Mesh Analysis – Example

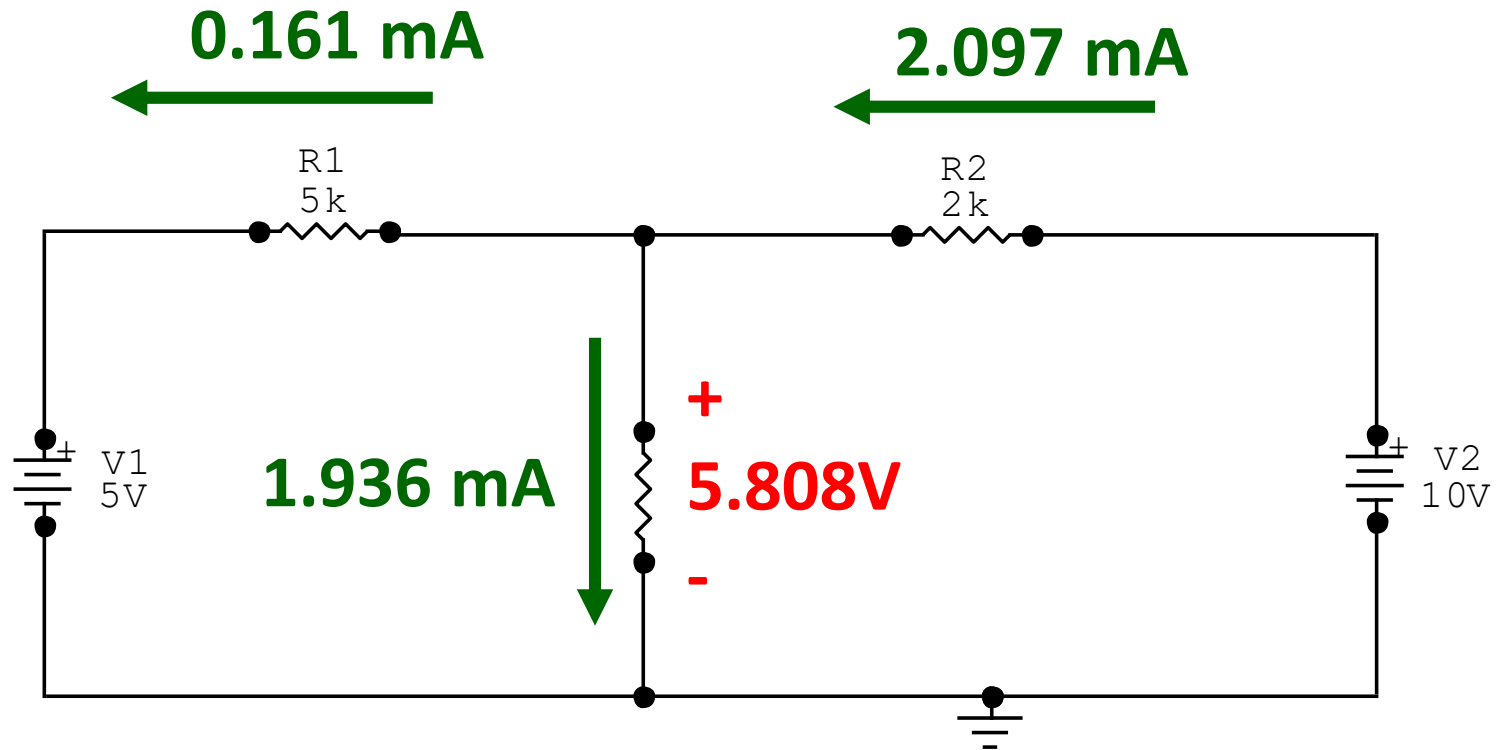

NODE ANALYSIS

Node Analysis

This is the systematic application of Kirchoff's Current Law

Step 1 Identify all nodes (greater than 2 paths). Note that the ground node is a valid node but you'll see that you only need to look at $n-1$ nodes to solve the circuit... so note but ignore ground.

Step 2 Identify what you want to learn.

Step 3 Apply circuit simplification techniques to those parts of the circuits you do not care about.

Step 4 Transform all voltage sources into their **equivalent Current Source form**.

Step 5 Draw directions for the currents in each branch (direction doesn't matter at this stage, but current sources have their own directions).

Step 6 For each branch, identify the magnitude of the current in terms of the voltage drop across that branch.


Step 7 Pick a direction (in or out) as positive (it doesn't matter which but be consistent).

Step 8 Note that at ANY and ALL nodes, **the algebraic sum of currents must equal zero**. This produces a set of simultaneous equations for each node.

Step 9 Solve the simultaneous equations (in any manner).


Node Analysis - Example

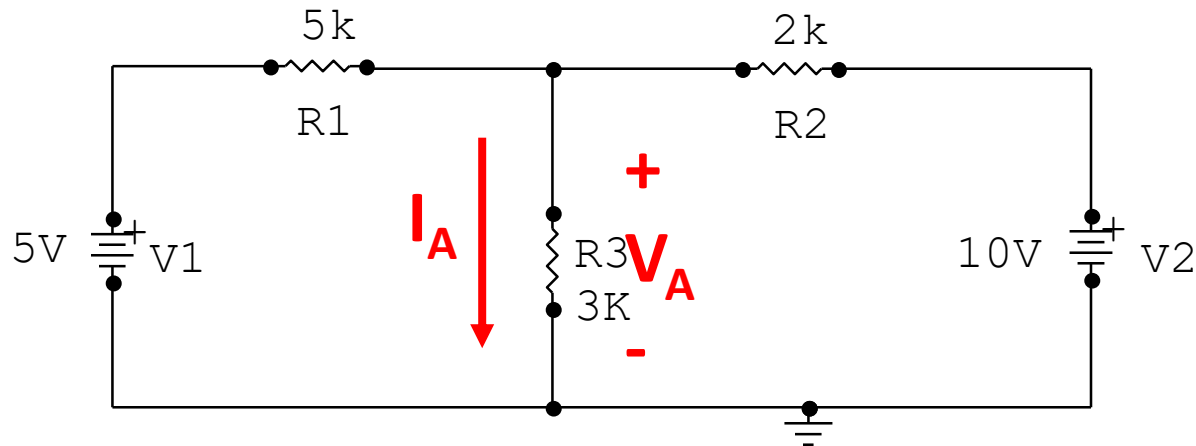Calculate the current I_A and the voltage (across R_3) V_A in the circuit below



Node Analysis - Example

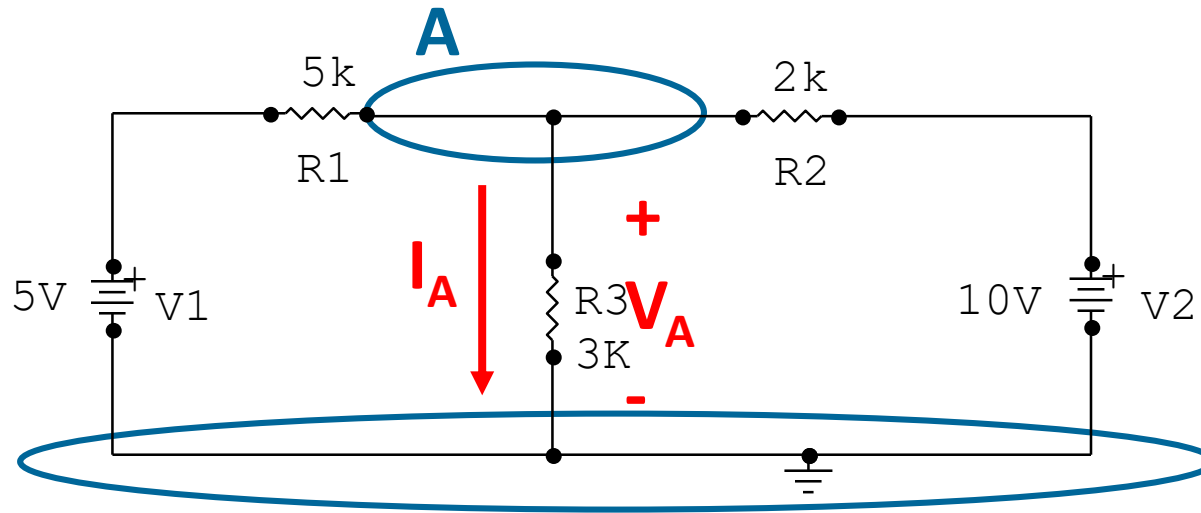Calculate the current I_A and the voltage (across R_3) V_A in the circuit below



Step 1 Identify all nodes:


- The 2-path nodes are trivial cases and can be ignored.
- The ground node is relevant but we don't tend to need to use it.
- That just leaves node A.

Node Analysis – Example (E3)

Step 2 Identify what you want to learn: I_A and V_A

Step 3 & Step 4 Apply circuit simplification techniques:

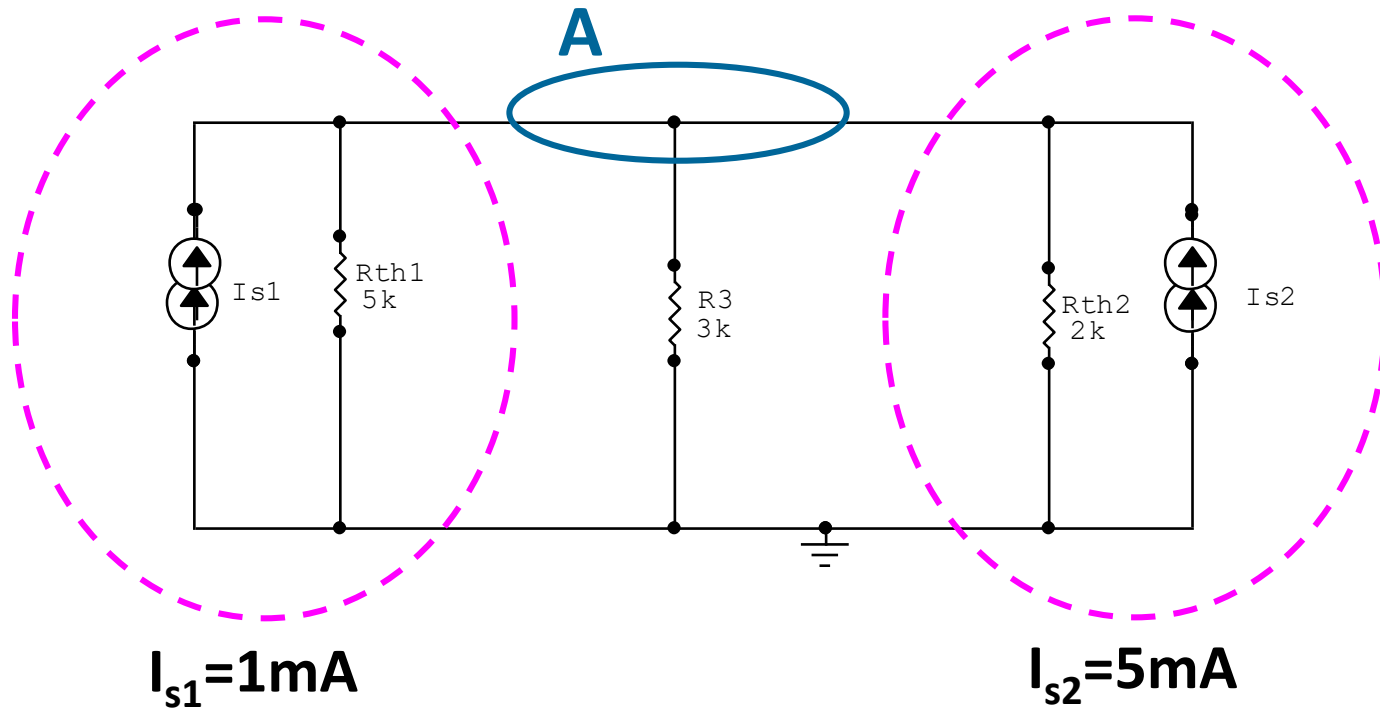
- we need to convert the voltage sources to current sources.
- keep the resistors the same, and $I_S = V_S/R_S$.



Node Analysis – Example (E5)

Step 5 Draw current directions in each branch

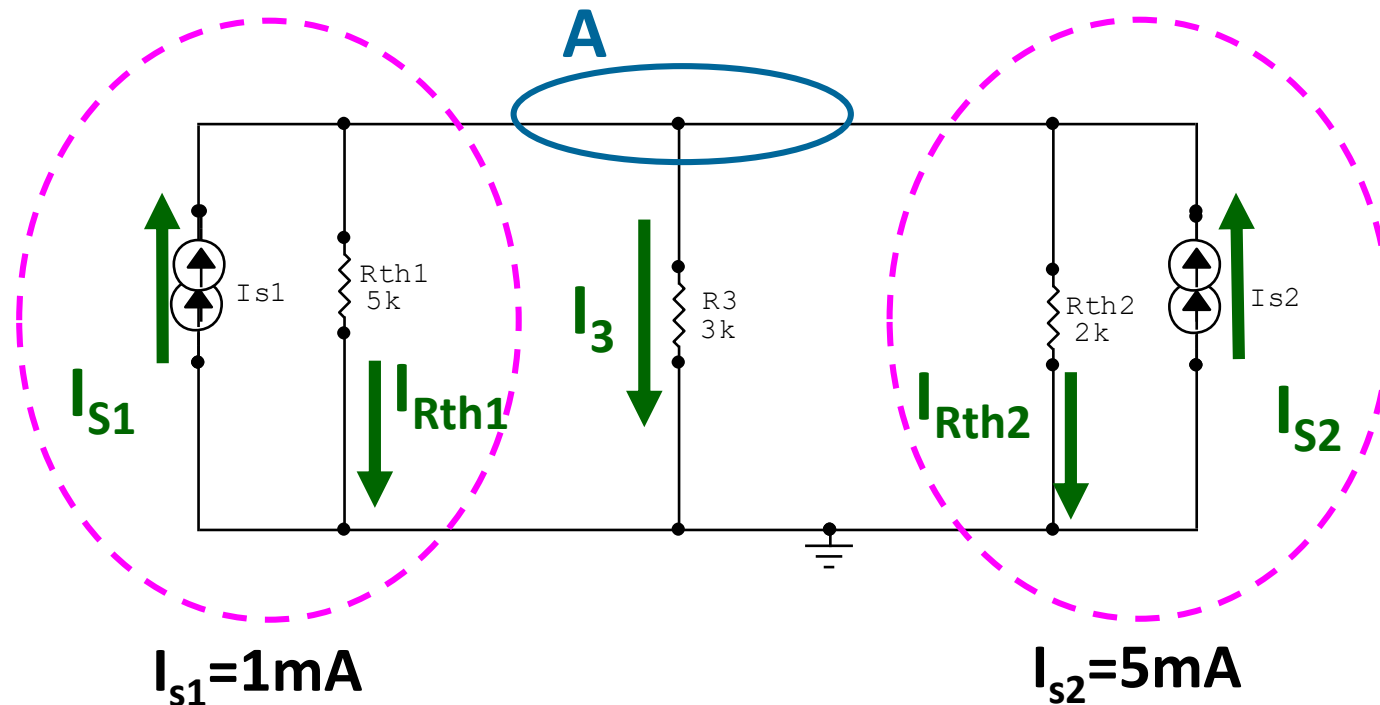- the direction does not matter as long as you stay consistent
- for me, I choose either **all** currents in or out of the node (this time out)
- it helps if you do try to use common sense ☺
- it is important to be careful with your labels!!



Node Analysis - Example (E6)

Step 6 Express all currents in terms of voltages or constants (worry about signs later)


$$I_{S1} = 1\text{mA}$$

$$I_{S2} = 5\text{mA}$$

$$I_3 = V_A / R_3 = V_A / 3000$$

$$I_{RTH1} = V_A / R_{th1} = V_A / 5000$$
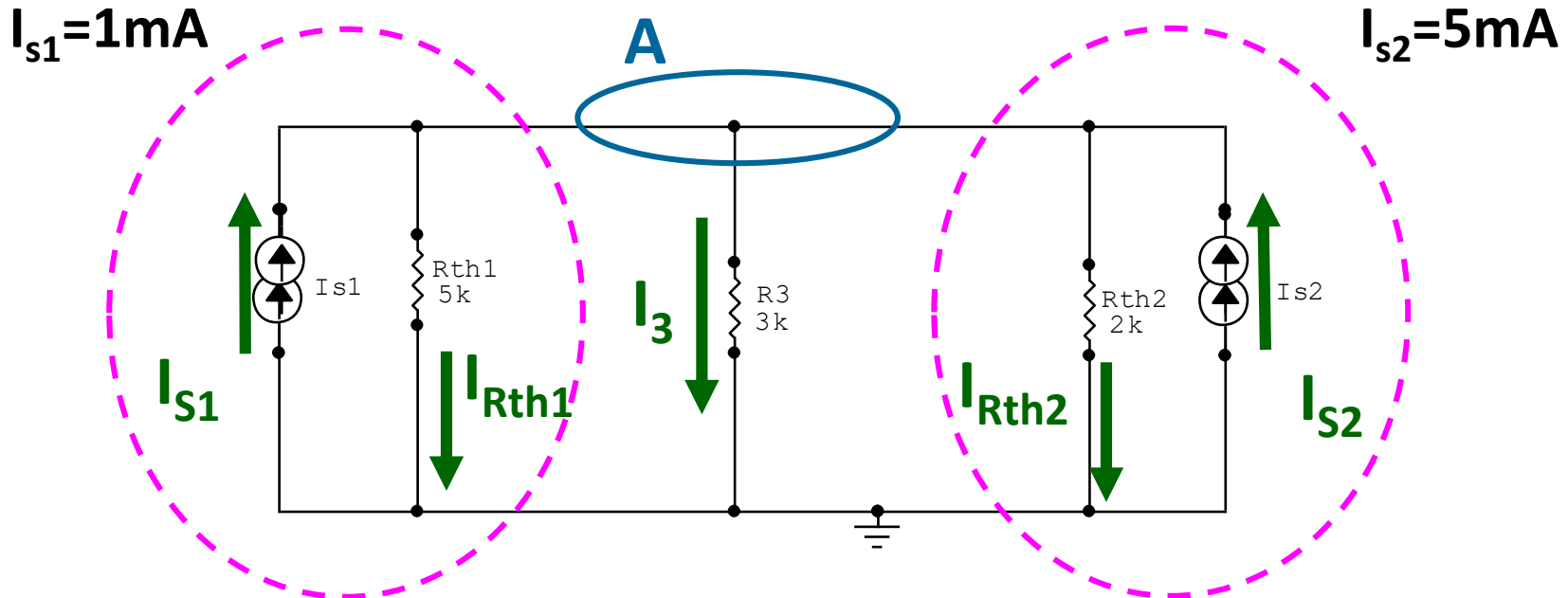
$$I_{RTH2} = V_A / R_{th2} = V_A / 2000$$



Node Analysis - Example (E7)


Step 7 Pick a sign for a direction (it doesn't matter which)

I picked **OUT** as being positive

Step 8 State Kirchhoff's Current Law for all Nodes (there's still only 1 + ground)

$$\begin{aligned} -I_{S1} + I_{RTH1} - I_{S2} + I_{RTH2} + I_{R3} &= 0 \\ (-1m) + (V_A/5000) + (-5m) + (V_A/2000) + (V_A/3000) &= 0 \end{aligned}$$

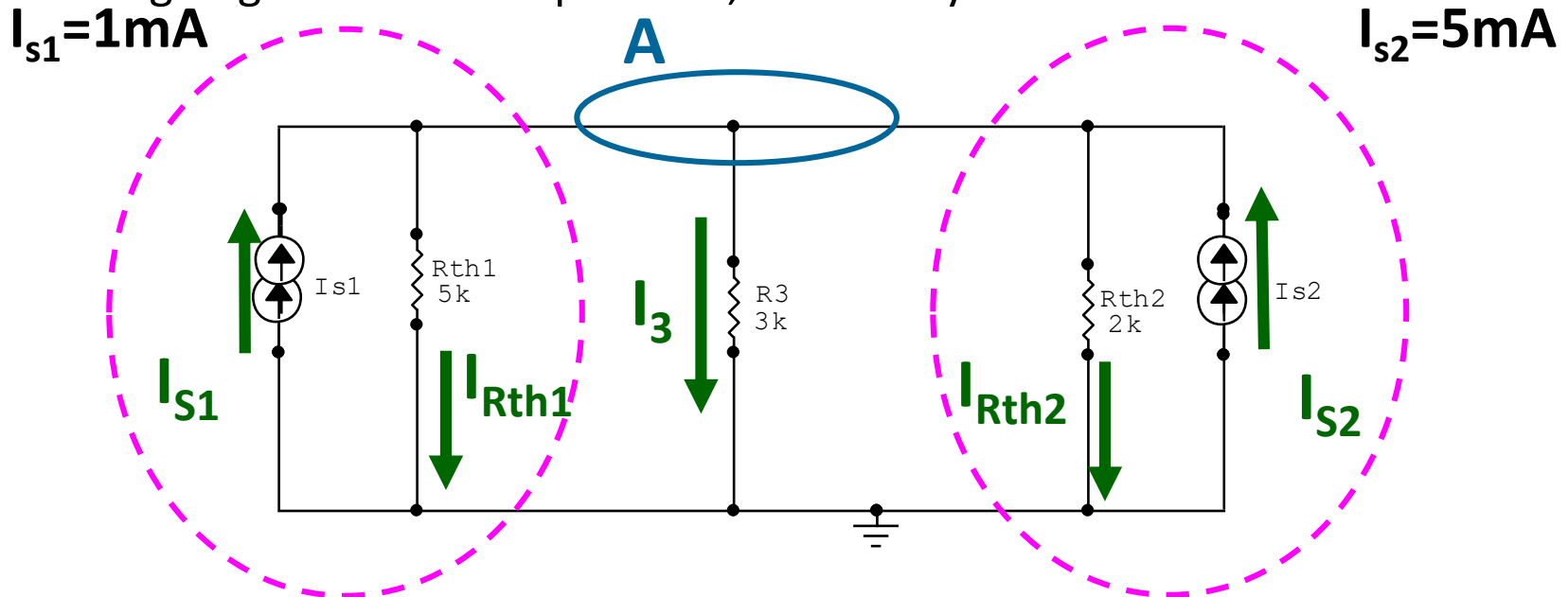This going to be a trivial problem, as it's only one node.



Node Analysis - Example (E8)


Step 9 Solve for V_A and then I_3

$$(V_A / 5) + (V_A / 2) + (V_A / 3) = 6$$

$$V_A (0.2 + 0.5 + 0.333) = 6$$

$$V_A = 5.808 \text{ Volts}$$

$$I_A = 1.936 \text{ Amperes}$$

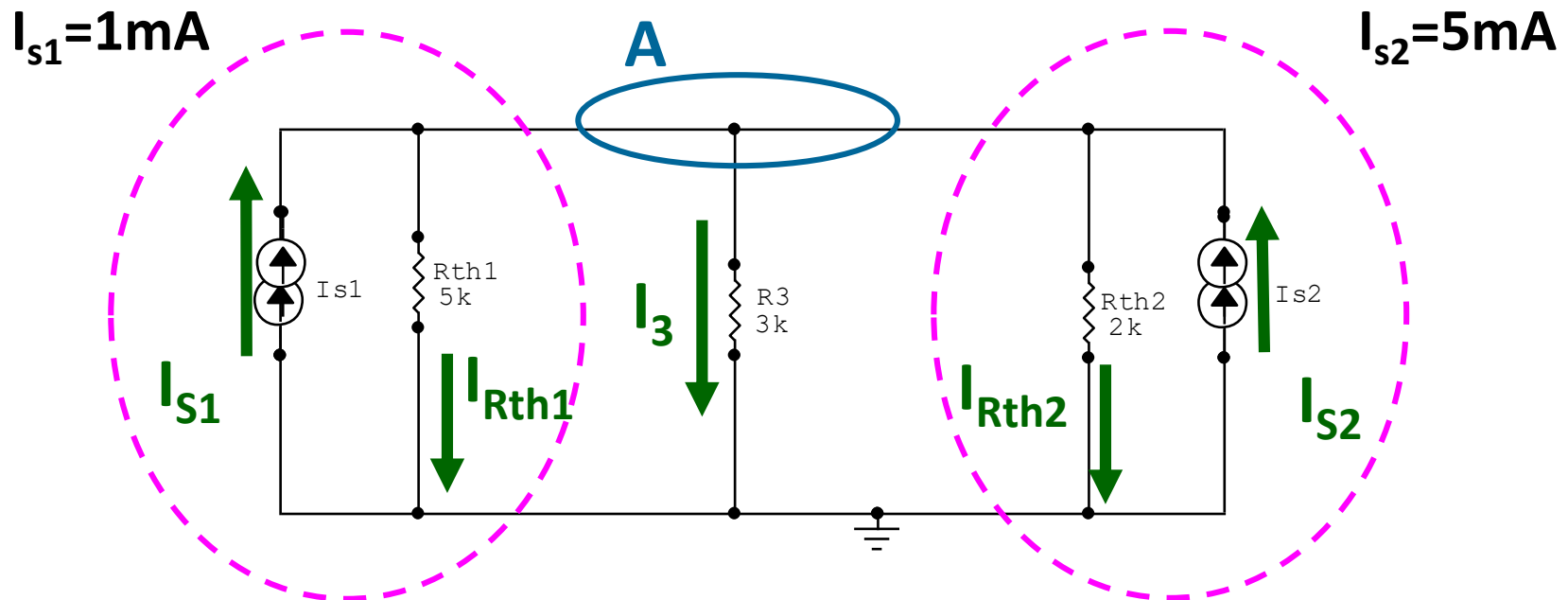

Observations

Mesh or Loop Analysis: you end up solving for currents, even though we start with voltages.

Node Analysis: you end up solving for voltages, even though we start with currents.

Which one to use?

- **Complexity** is based on the number of nodes/loops you have in the final circuit. The one with the least is the easiest.
- You may have no choice depending on your current and voltage sources.