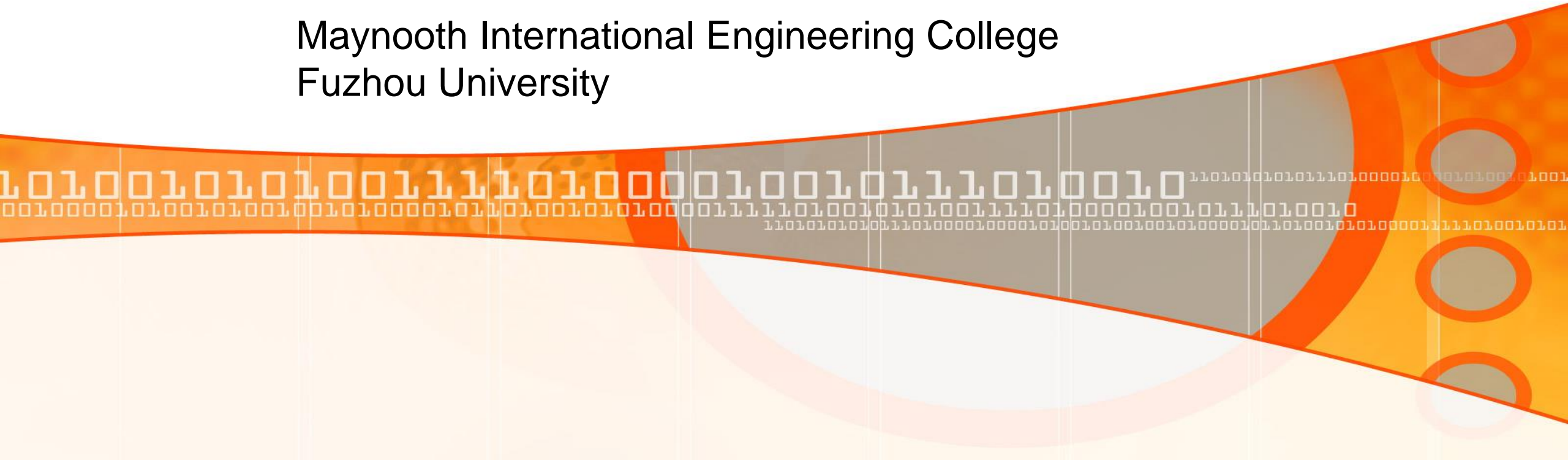


EE103 Digital Systems 1

Wong Chin Hong

106

Maynooth International Engineering College
Fuzhou University



So far ... !

- We've used Karnaugh Maps to minimise logic ...
- We've implemented circuits using NAND only or NOR only gates ...
- We've looked in detail at the SR, D, JK and T flipflops ...
- We've analysed a counter ...



***TODAY, we are going
to look at designing a
counter ...***




Designing a Counter

- **Ex. 7.2 Design a MOD 6 counter with a repeating sequence 0 1 3 7 6 4, using T flipflops. Check for possible lockout.**


Designing a Counter

 - **STEP I** - We **need to determine the number of flipflops** required.
- Since the sequence does not contain a number greater than 7 (i.e. 111 in binary), we only need to use 3 flipflops.
- We will label these A, B and C and, arbitrarily, choose A to represent the **MSB**. Hence:



Designing a Counter

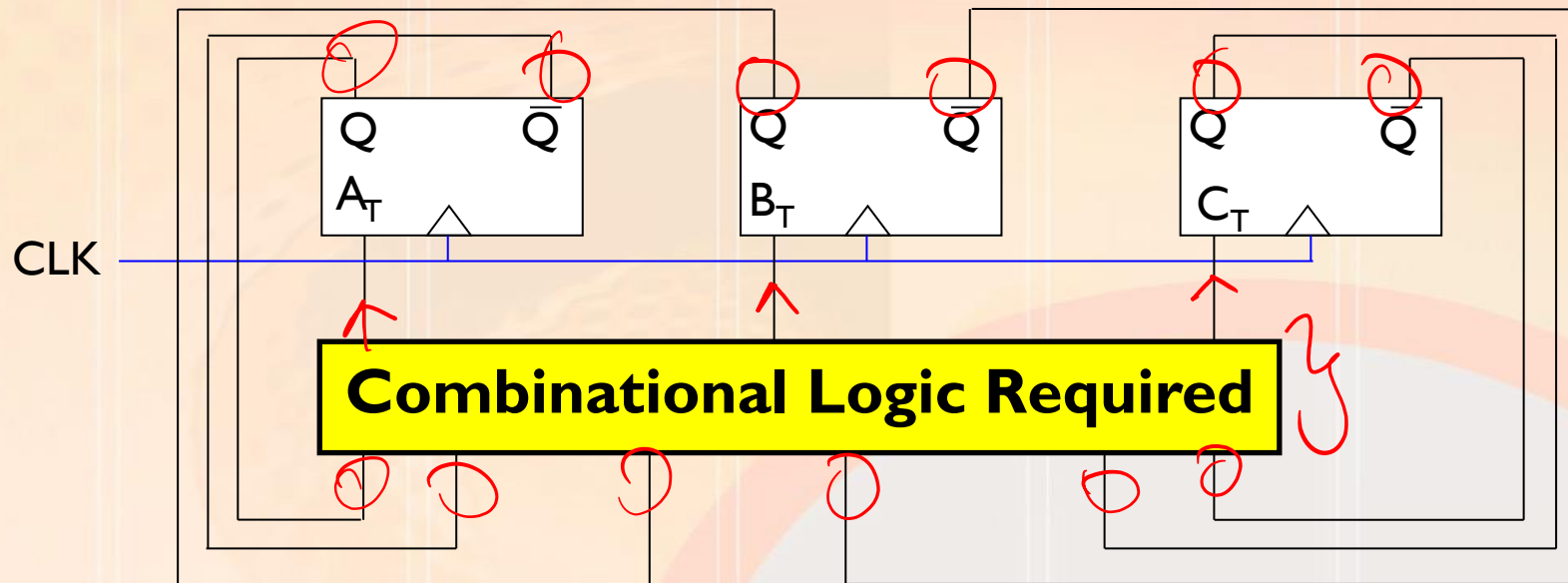- The design is reduced to determining the logic necessary to generate A_T , B_T and C_T from the states of A, B and C to produce the new values for A, B and C, i.e.:



Designing a Counter

- **STEP 2** – We know the sequence of states required (given in question), so we now **need to determine the sequence of inputs to each of the flipflops** in order to produce the required output.
- Hence, for example, let's take the first two states which are 0 and 1 or in binary **ABC = 000** and **001**.
- *Recall the requirements table for the T flipflop ...*

Operation	T
Stay at 0	0
Stay at 1	0
Go to 0	1
Go to 1	1

$$\begin{aligned} Q(t) &= Q \\ Q(t) &= \overline{Q} \end{aligned}$$

Designing a Counter

- So, taking each bit in turn:

A goes from 0 to 0 \Rightarrow no change $\Rightarrow A_T = 0$ ✓
 B goes from 0 to 0 \Rightarrow no change $\Rightarrow B_T = 0$ ✓
 C goes from 0 to 1 \Rightarrow output needs to be toggled
 $\Rightarrow C_T = 1$ ✓

- Hence, the flipflop inputs required to transition from state 000 to state 001 is given by:

$$A_T B_T C_T = 0 0 1$$

- Repeating this process for the remaining sequence of states (i.e. from, 1 to 3, 3 to 7, etc.), we obtain the following table:

T	Q(n)
0	Q
1	\bar{Q}

T	Q
0 \rightarrow 0	0
1 \rightarrow 1	1
1 \rightarrow 0	1
0 \rightarrow 1	1

000
001

State	A	B	C	A _T	B _T	C _T
0	0	0	0	0	0	1
1	0	0	1	0	1	0
2	0	1	1	1	0	0
3	1	1	1	0	0	0
4	1	0	1	0	1	0
5	1	0	0	1	0	0
6	0	0	0	1	1	0
7	0	1	0	0	1	0

Designing a Counter

T	Q(T)
0	Q
1	\bar{Q}

given.

3

State	A	B	C	Flipflop Inputs A_T B_T C_T
0	0	0	0	0 0 1
1	0	0	1	0 1 0
3	0	1	1	1 0 0
7	1	1	1	0 0 1
6	1	1	0	0 1 0
4	1	0	0	1 0 0
0	0	0	0	

State	A	B	C	A_T	B_T	C_T
0	0	0	0	0	0	1
1	0	0	1	0	1	0
3	0	1	1	1	0	0
7	1	1	1	0	0	1
6	1	1	0	0	1	0
4	1	0	0	1	0	0
0	0	0	0			

Designing a Counter

state	ABC	A _T B _T C _T
<u>2</u>	0 1 0	0 0 1
5	1 0 0	0 1 0
1	0 0 1	1 0 0
3	1 1 1	0 0 1
<u>2</u>	0 1 0	0 0 1

State	A	B	C	Flipflop Inputs A _T B _T C _T
<u>0</u>	0	0	0	0 0 1
1	0	0	1	0 1 0
3	0	1	1	1 0 0
7	1	1	1	0 0 1
6	1	1	0	0 1 0
4	1	0	0	1 0 0
0	0	0	0	0 0 0

mod 4 =

~~2 5 1 3~~

x 2 x 5


Since the sequence repeats, we need to ensure that we transition from state 4 back to the first state, i.e. state 0.

Designing a Counter

- **STEP 3** – Once we know the sequence of inputs to each of the flipflops, we then need to **generate a Karnaugh Map (KM) for each of the flipflop inputs** and obtain a minimal combinational logic circuit for implementing this sequence.
- A quick glance at the previous table shows that:

$$A_T = \Sigma(3,4), B_T = \Sigma(1,6), C_T = \Sigma(0,7)$$

 - Generate a KM for each of A_T , B_T , and C_T .
- We will treat the unused states **2** and **5** as **don't care terms** for now, as they are not part of the required sequence.




K-Map.

25 \Rightarrow X
A_T = 3, 4
B_T = 1, 6
C_T = 0, 7




Designing a Counter

State	A	B	C	Flipflop Inputs		
				A _T	B _T	C _T
0	0	0	0	0	0	1
1	0	0	1	1	1	0
3	0	1	1	3	0	0
7	1	1	1	7	0	1
6	1	1	0	6	1	0
4	1	0	0	4	0	0
0	0	0	0			

 

Designing a Counter

State	A	B	C	Flipflop Inputs		
				A _T	B _T	C _T
0	0	0	0	0	0	1
1	0	0	1	0	1	0
3	0	1	1		0	0
7	1	1	1	0	0	1
6	1	1	0	0	1	0
4	1	0	0	1	0	0
0	0	0	0			

 

Designing a Counter

State	A B C			Flipflop Inputs		
	A	B	C	A _T	B _T	C _T
0	0	0	0	0	0	1
1	0	0	1	0	1	0
3	0	1	1	1	0	0
7	1	1	1	0	0	1
6	1	1	0	0	1	0
4	1	0	0	1	0	0
0	0	0	0			

C_T

A

C

B

$$C_T = \bar{A}\bar{C} + AC$$

$$= \overline{A \oplus C}$$

Designing a Counter

- In engineering design, it is always good practice to self check a design to make sure that the design process has been carried out correctly.
- In this case, it provides a check to ensure that the minimisation was done correctly.
- We self check the design by effectively analysing our circuit to see if it produces the required sequence.

Designing a Counter

- Consider the first output of the sequence $ABC = 000$. Passing this through our circuit design gives:

$$\mathbf{A_T = A \oplus B = 0 \oplus 0 = 0}$$

$$\mathbf{B_T = B \oplus C = 0 \oplus 0 = 0}$$

Designing a Counter

- Consider the first output of the sequence $ABC = 000$. Passing this through our circuit design gives:

$$A_T = A \oplus B = 0 \oplus 0 = 0$$

$$B_T = B \oplus C = 0 \oplus 0 = 0$$

$$C_T = A \oplus C = 0 \oplus 0 = 1$$

$$A_T B_T C_T = 0 0 1$$

- Hence, if the current state is $ABC = 000$ and the flipflop inputs are $A_T B_T C_T = 0 0 1$ then the next state will be:

$$A(\tau) B(\tau) C(\tau) = 0 0 1$$

Designing a Counter

- We now repeat the process by passing this state through our circuit, by generating the new flipflop inputs and by determining the next state.

Designing a Counter

- Continuing in this manner we obtain the following self check table:

State	A	B	C	A_T	B_T	C_T
				$A \oplus B$	$B \oplus C$	$A \oplus C$
0	0	0	0	0	0	1
1	0	0	1	0	1	0
3	0	1	1	1	0	0
7	1	1	1	0	0	1
6	1	1	0	0	1	0
4	1	0	0	1	0	0
0	0	0	0			

\Rightarrow are correct

Designing a Counter

- We also need to **check the unused states**.
- Although they are not part of the main cycle, they may, nevertheless, cause problems with our counter design in certain circumstances.
- The unused states are 2 and 5. Passing these through our circuit design gives:

2 2 5 X



Designing a Counter

- We also need to **check the unused states**.
- Although they are not part of the main cycle, they may, nevertheless, cause problems with our counter design in certain circumstances.
- The unused states are 2 and 5. Passing these through our circuit design gives:




State	A	B	C	A_T B_T C_T		
				$A \oplus B$	$B \oplus C$	$A \oplus C$
2	0	1	0	1	1	1
5	1	0	1	1	1	1
2	0	1	0	1	1	1
5	1	0	1	1	1	1

→ X 0 1 3 7 6 4


Designing a Counter

- This self check shows that if the counter should enter one of the unused states 2 and 5, it will oscillate between these two states on successive clock cycles.
- It will be locked out of the *main* cycle. Hence **lockout** occurs.
- In this condition, the counter is said to be in a **parasitic cycle**.
- The counter can go into unused states by a pulse of noise (external spurious electrical intrusion) or at power up. 2 or 5 → randomly.

 

Designing a Counter

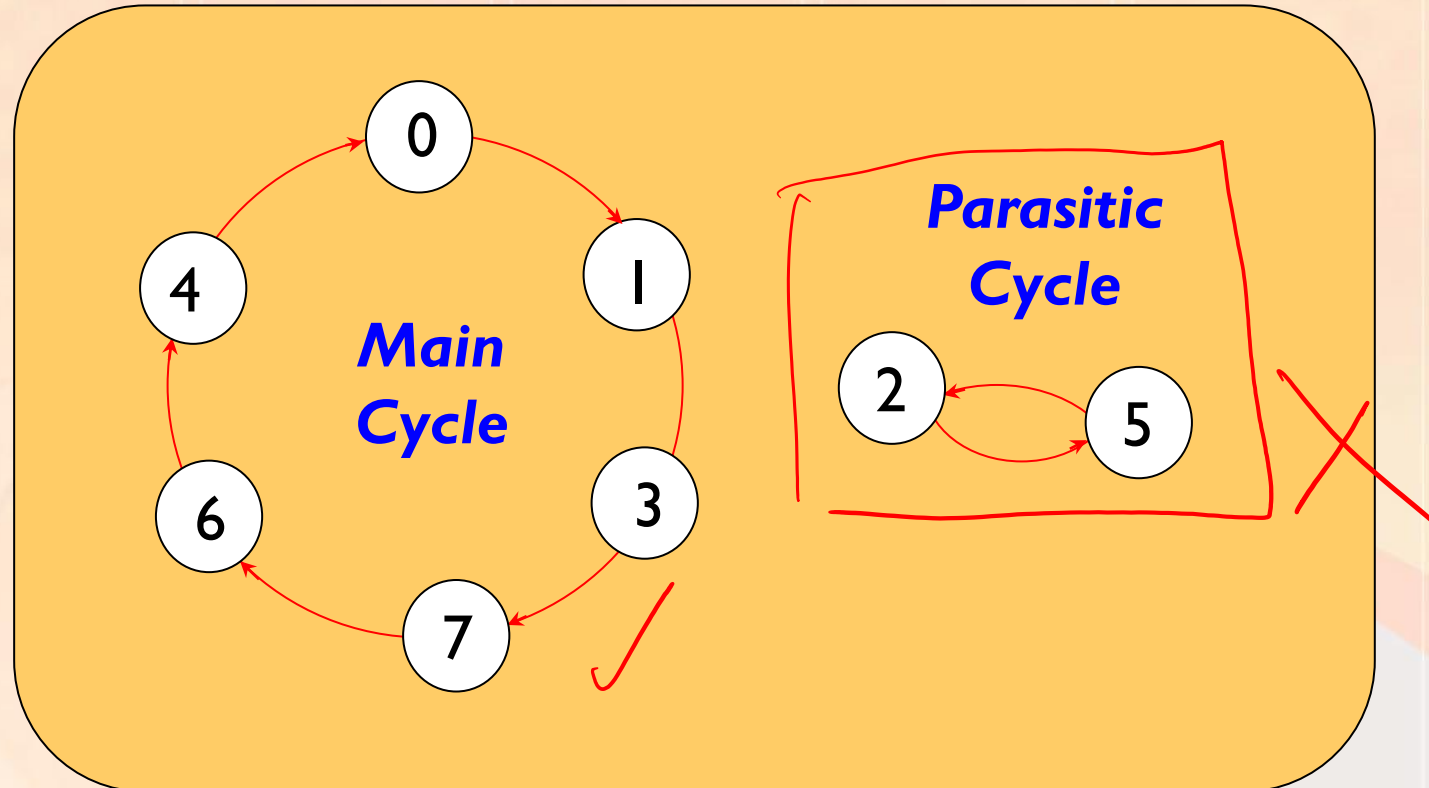- Thus, the state diagram for our current counter design is as follows:



Designing a Counter

- We can correct this problem in one of two ways.
- The first way is to use appropriate hardware – i.e. **flipflops that have asynchronous inputs** such as preset and clear.
- These inputs can be used to initialise the counter to the first state of $ABC = 000$ before normal operation begins.
- Our second option is to solve the problem by redesigning our circuit to prevent lockout occurring.
- One way to prevent lockout is to make a simple change to the existing design.

5/2

we need
best
choice




Designing a Counter

- Thus for example, we can make state 2 return to state 4 in the main cycle by forcing $C_T = 0$ for this state as follows:

State	A	B	C	A_T	B_T	C_T
2	0	1	0	1	1	0
4	1	0	0			

- We haven't modified the sequence of inputs to the Toggle flipflops representing A & B, so the input circuitry for these remain the same.
- However, we have modified the input sequences for the 'C' Toggle flipflop and so we need to revisit its KM as follows ...

Designing a Counter

 


Designing a Counter

- Alternatively, the counter could be redesigned from the outset so that lockout can never occur by ensuring that **all unused states return to a pre-defined state**, such as $ABC = 000$.

2 5 X don't care

 - This would give the following state diagram:



ABC	State	A _T	B _T	C _T
	0			
	1			
	2			
	3			
	4			
	5			
	6			
	7			

Designing a Counter


- This design yields a synchronous reset to 000 on receipt of the first clock pulse.
- We could implement the full design from scratch by repeating what we have done already and including the transition of states **2 to 0** and **5 to 0**.
- However, as we have already carried out the design of the main sequence, we only need to consider, in this case, the transition of states **2 to 0** and **5 to 0**.
- Hence, repeating step 2 for the unused states, we **need to determine the inputs that allows the transition of states 2 to 0 and 5 to 0, as follows ...**

change all the
don't care
to


Designing a Counter

- We no longer have don't care terms for the unused states as we do actually care what happens these states. 2, 1, 5
- Thus all the don't care terms in the previous KMs have now been assigned either a 1 or a 0.
- The new Karnaugh Maps are as follows ...


Designing a Counter

 

Designing a Counter

 

Designing a Counter

 

Designing a Counter

- In relation to both redesigns, it's worth noting the following:
- The first redesign is based on the principle of designing the counter circuit to satisfy the main cycle and only then checking to see if there's a problem with lockout. *X by X any don't care term*
- If there is, this problem can be resolved with the minimum of changes.
- Thus, this approach ensures **an overall minimal design** in terms of the combinational logic required.



Designing a Counter



- The second approach of ensuring that all unused states return to a prescribed state is a decision that is taken at the outset of the design.
- This approach **ensures that *lockout cannot occur***, i.e. the problem should never arise.
- It also ensures that **all *unused states return to the main cycle on one clock pulse***.
- These added benefits usually come at the expense of additional gates and, hence, **a *non-minimal solution*** (in comparison with the first design approach).



BCD 8 4 2 1
3 2 1 0

- $$2^1 2^2 2^1 2^0$$

De Morgan

- 1
- 2
- 3
- 4

Designing a Counter

- Note, here we are given a BCD 2421 weighted counter, as opposed to the conventional BCD 8421 standard weighting.
- When working with Karnaugh Maps and minterms, we use the latter weighting.
- **So the first thing we need to do here is to obtain the minterm (or 8421) equivalent of the 2421 weighting.**
- This is shown in the following table ...

Designing a Counter

0 000
↓
7 111

Decimal Value	BCD <u>2421</u>	Minterm Value (8421)
0	0000	0
1	0001	1
2	0010	2
3	0011	3
4	0100	4
5	1011	11
6	1100	12
7	1101	13
8	1110	14
9	1111	15

Given Count

2 4 2 1

	2	4	2	1
5	1	0	1	1
6	1	1	0	0

Designing a Counter

- So the sequence we are actually generating is in fact

0, 1, 2, 3, 4, 11, 12, 13, 14 and 15.

- The unused minterms (or states) are therefore **$m_5, m_6, m_7, m_8, m_9, m_{10}$** .
- Recall the requirements table for JK flipflops:

Operation	J	K
Stay at 0	0	X
Stay at 1	X	0
Go to 0	X	1
Go to 1	1	X

Designing a Counter

- **Step 1** – We need to **determine the number of flipflops required**.
- Since the sequence does not contain a number greater than 15 (i.e. 1111 in binary), we need to use **four** flipflops.
- We will label these A, B, C and D and, arbitrarily, choose A to represent the MSB.
- **Step 2** – Now, we need to **determine the sequence of inputs to the JK flipflops** in order to produce the required output.
- Hence, we obtain the following table ...

0
↓
15
4 ff



Designing a Counter

Minterm (8421)	Count (2421)	ABCD	Flipflop Inputs							
			<u>A_J</u>	<u>A_K</u>	<u>B_J</u>	<u>B_K</u>	<u>C_J</u>	<u>C_K</u>	<u>D_J</u>	<u>D_K</u>
0	0	0000	0	X	0	X	0	X	1	X
1	1	0001	0	X	0	X	1	X	X	1
2	2	0010	0	X	0	X	X	0	1	X
3	3	0011								
4	4	0100								
11	5	1011								
12	6	1100								
13	7	1101								
14	8	1110								
15	9	1111								


Operation	J	K
Stay at 0	0	X
Stay at 1	X	0
Go to 0	X	1
Go to 1	1	X

고 고 고 고


Designing a Counter

- Remember – we know the sequence of outputs, we are generating the sequence of inputs to go from one output to the next for each consecutive pair of outputs.
- Also, as the sequence repeats, the last state (1111) must return to the first state (0000).
- **Step 3** – Next, we need to put the sequence of values for each flipflop input (there are 8 inputs in total) into a Karnaugh Map in order to **obtain a minimal circuit implementation**.
- Noting that the unused states are treated as don't care terms, the Karnaugh Maps for each of the eight inputs are as follows ...

Designing a Counter

 


$$A_j = B$$

 


$$A_k = BCD$$

Designing a Counter

 


$$B_J = CD$$

 


$$B_K = \overline{A} + CD$$

Designing a Counter

 


$$C_j = D + \overline{A}B$$

 


$$C_k = D$$

Designing a Counter

 

$$D_j = 1$$

 

$$D_k = 1$$