

EE114


Intro to Systems & Control

Dr. Lachman Tarachand

Dr. Chen Zhicong

Prepared by Dr. Séamus McLoone

Dept. of Electronic Engineering

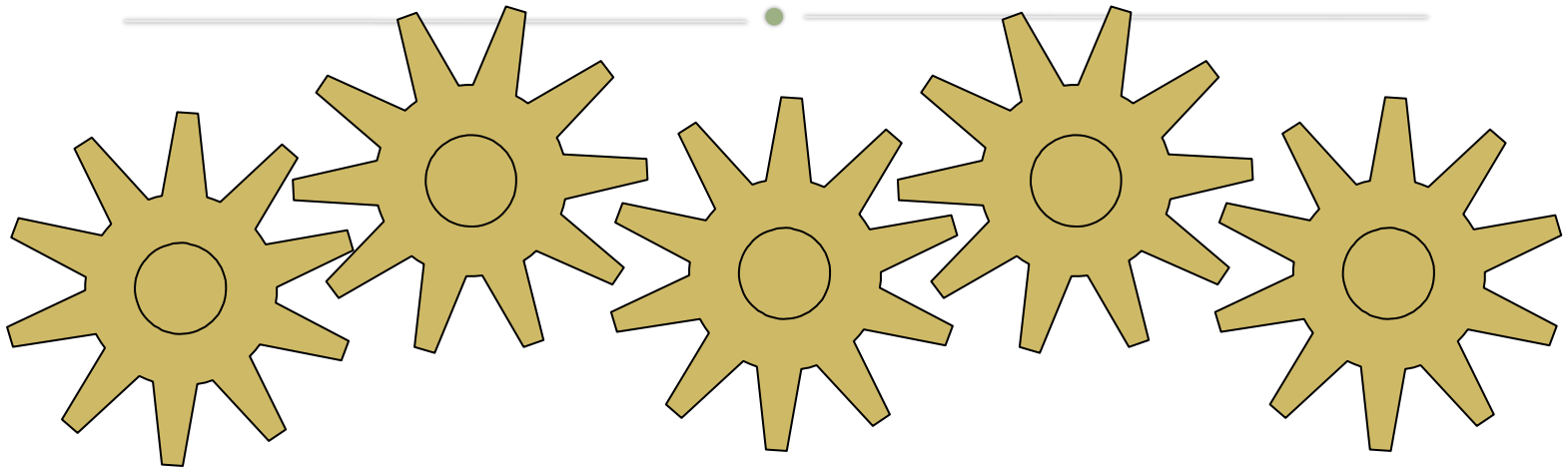


So far ...

- We've introduced the concept of control and, in particular, feedback control ...
- We've looked at what a system is, how systems can be categorized and illustrated the need for mathematical modelling ...



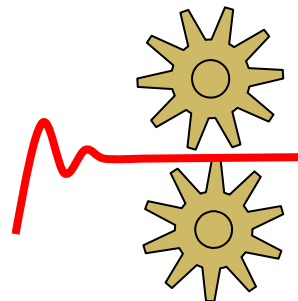'WELL, HIGGINS, I SEE EVERYTHING'S UNDER CONTROL.'




So far ...

- We've introduced the concept of control and, in particular, feedback control ...
- We've looked at what a system is, how systems can be categorized and illustrated the need for mathematical modelling ...




'WELL, HIGGINS, I SEE EVERYTHING'S UNDER CONTROL.'

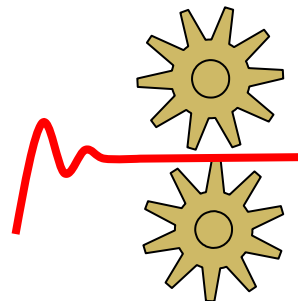- **Now, we are going to look at the mathematical modelling of a few simple systems.**




Modelling of Basic Systems

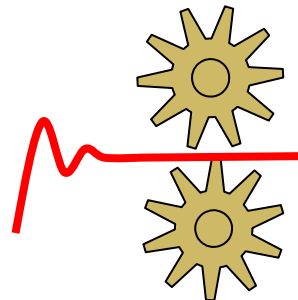- As mentioned already, obtaining a mathematical representation of a system allows us to:
 - Understand the characteristics of the system (useful for design purposes).
 - Simulate the system (useful for scenario testing, forecasting, etc.).
 - Provide a basis for control system design (for stability, optimising performance, etc.).




Modelling of Basic Systems

- As mentioned already, obtaining a mathematical representation of a system allows us to:
 - Understand the characteristics of the system (useful for design purposes).
 - Simulate the system (useful for scenario testing, forecasting, etc.).
 - Provide a basis for control system design (for stability, optimising performance, etc.).
- In essence, a mathematical model of a system will increase our understanding of it.

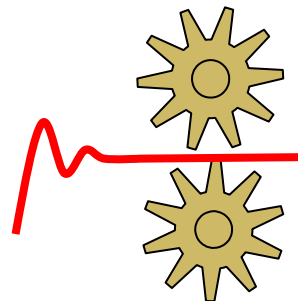


Modelling of Basic Systems

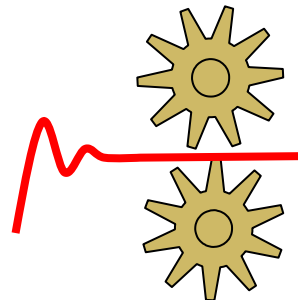- The basic modelling procedure is as follows:
 - 1 – Draw a schematic diagram of the system and define the variables.
 - 2 – Using physical laws, write equations for each component.
 - 3 – Parameterise the model (using experiment design and/or system identification techniques).
 - 4 – Validate the model.




Modelling of Basic Systems

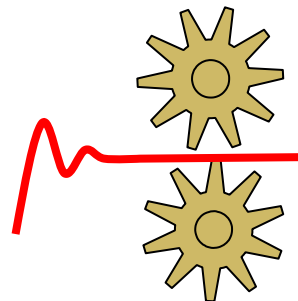- Other factors that need to be considered when modelling include:
 - **Complexity/accuracy trade-off** – the more accurate the model, the more complex it becomes (and hence more complex mathematical analysis required).




Modelling of Basic Systems

- Other factors that need to be considered when modelling include:
 - **Complexity/accuracy trade-off** – the more accurate the model, the more complex it becomes (and hence more complex mathematical analysis required).
 - **Objective of modelling** – what is the purpose of the model? This dictates the level of accuracy (and hence complexity) required. Different modelling objectives include design/synthesis, analysis and control.

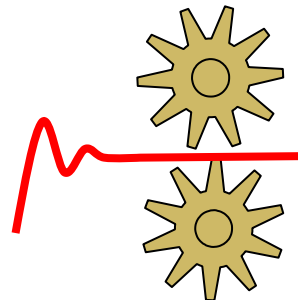



Modelling of Static Systems

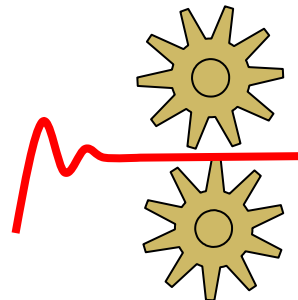- Before we consider dynamical systems, let us first look at some model representations of **basic static systems**. Here, we are only going to consider electrical systems.



Modelling of Static Systems

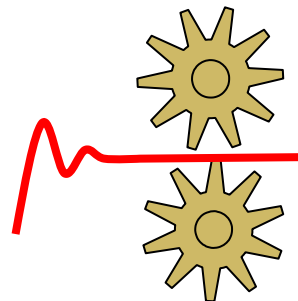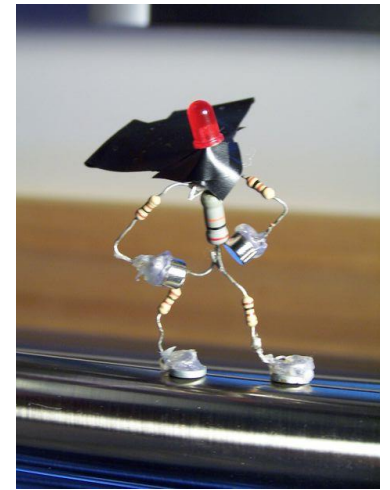- Before we consider dynamical systems, let us first look at some model representations of **basic static systems**. Here, we are only going to consider electrical systems.
- For static electrical systems, such as resistor networks, we use Ohm's law, which states that the voltage across a resistor is directly proportional to the current flowing through it:





Modelling of Static Systems

- Before we consider dynamical systems, let us first look at some model representations of **basic static systems**. Here, we are only going to consider electrical systems.
- For static electrical systems, such as resistor networks, we use Ohm's law, which states that the voltage across a resistor is directly proportional to the current flowing through it:


$$v = iR$$

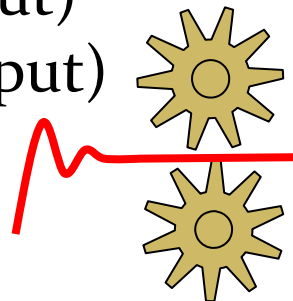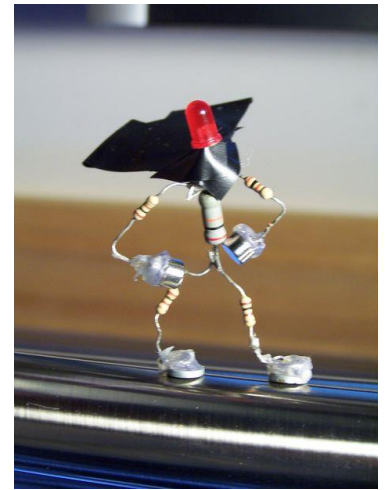v is the voltage across the resistor in volts (system output)
 i is the current through the resistor in amps (system input)
 R is the resistance in ohms (system model)





Modelling of Static Systems

- Note that there are no dynamics in this system. Here, a step change in the input will result in a step change in the output.
- The model is given by a resistor value with a tolerance specification.
- Different resistor networks will involve parallel and series configurations.
- Furthermore, you may need to apply Kirchoff's current and voltage laws (KCL and KVL) in order to obtain a suitable model representation.


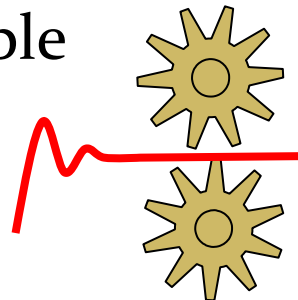


Modelling of Static Systems

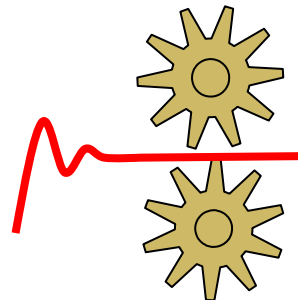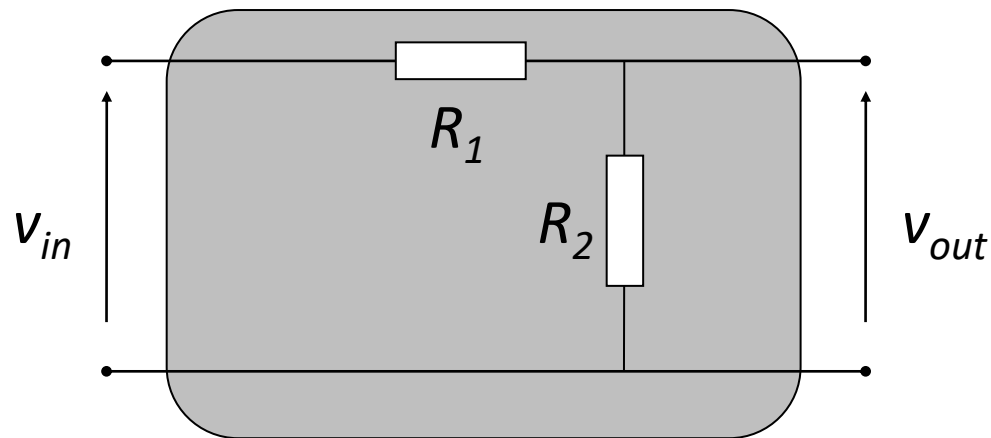
- *Ex. 3.1 Derive, from first principles, the input-output relationship for the voltage divider circuit below:*




Solution:

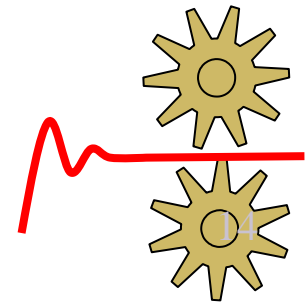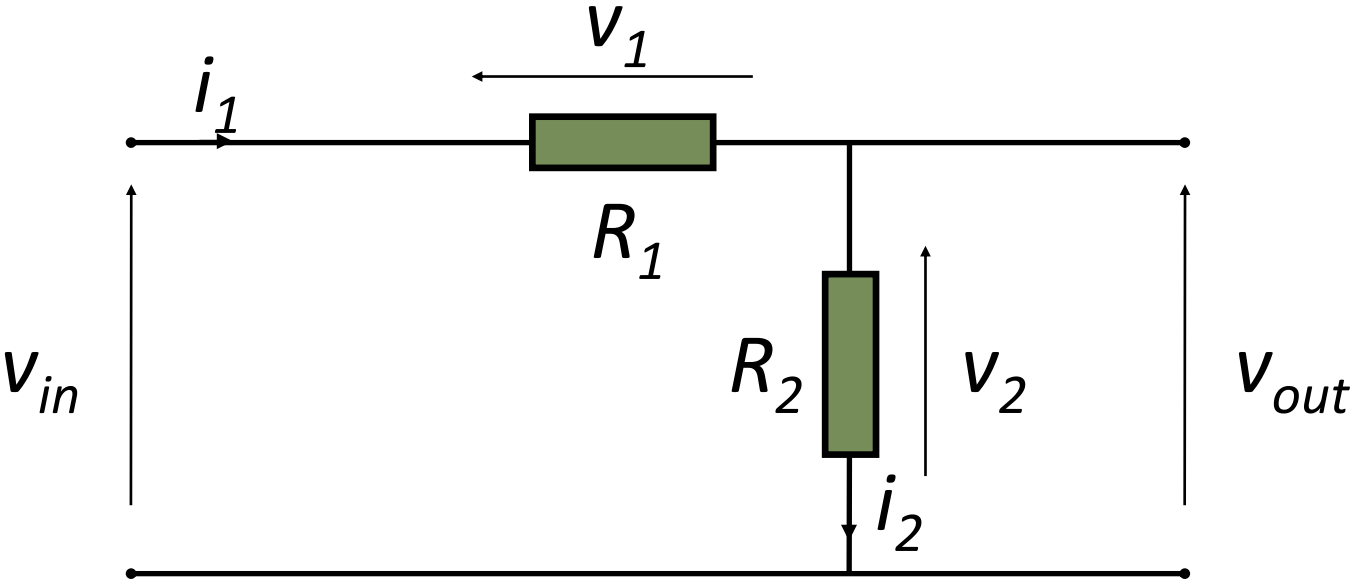


Solution:

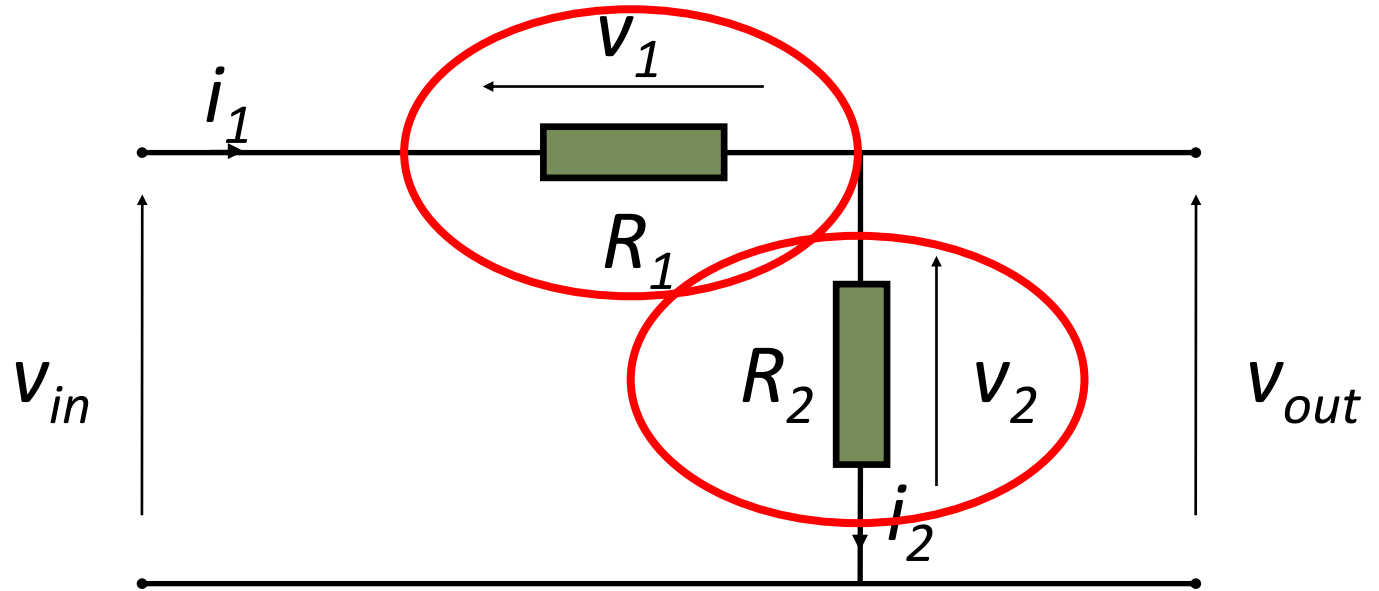


Ohm's Law ...

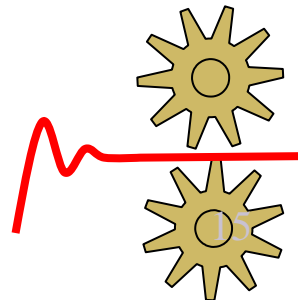


Solution:

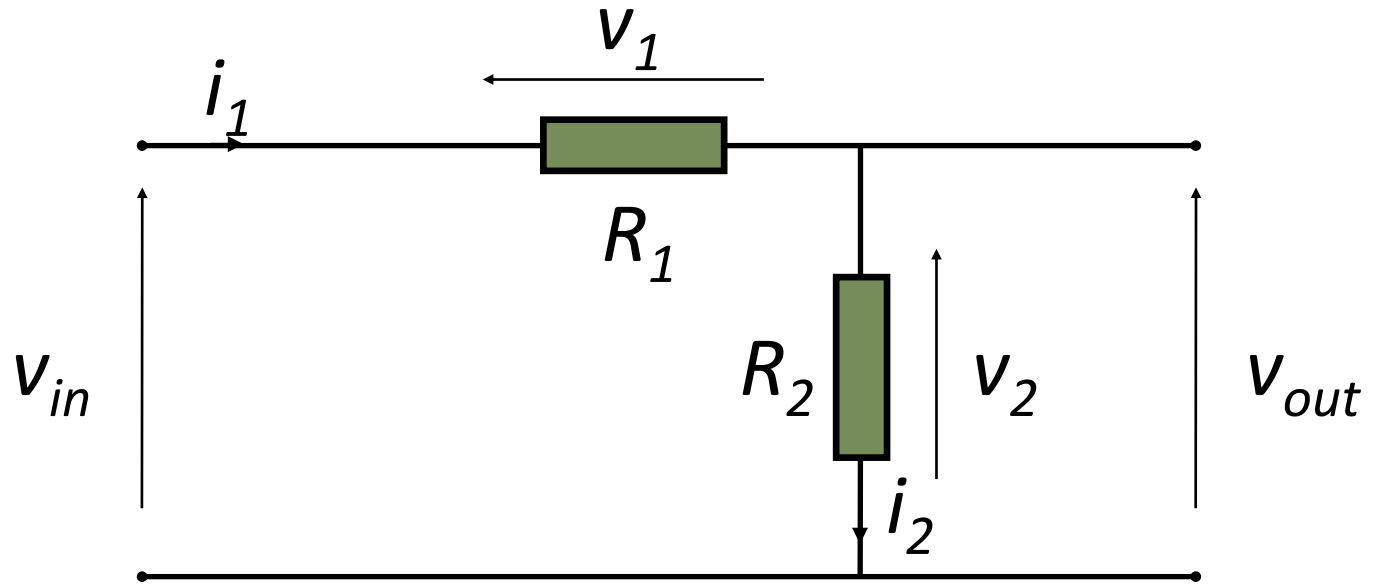

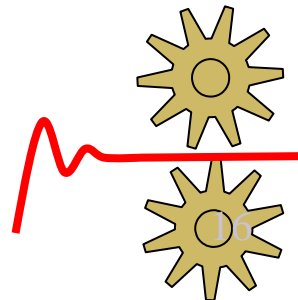Ohm's Law ... $v_1 = i_1 R_1$ and $v_2 = i_2 R_2$




Solution:

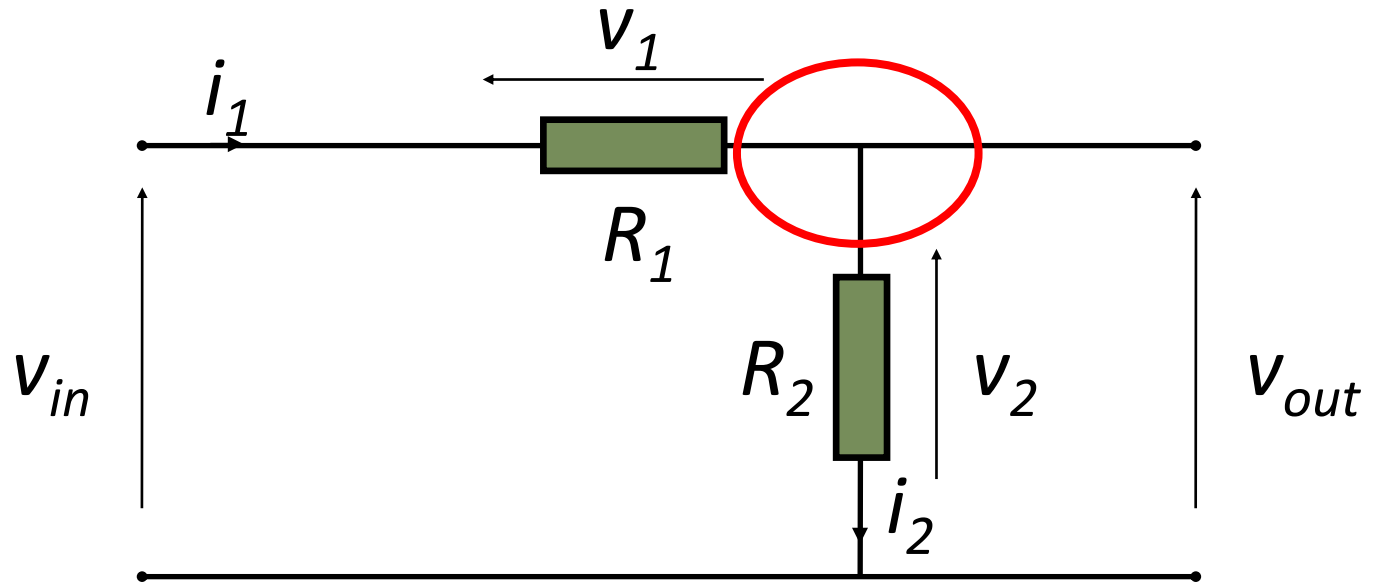


Ohm's Law ... $v_1 = i_1 R_1$ and $v_2 = i_2 R_2$

KCL ...

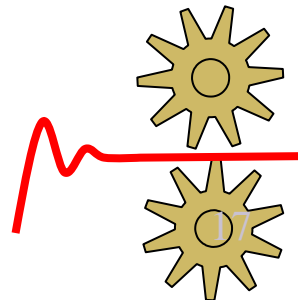


Solution:

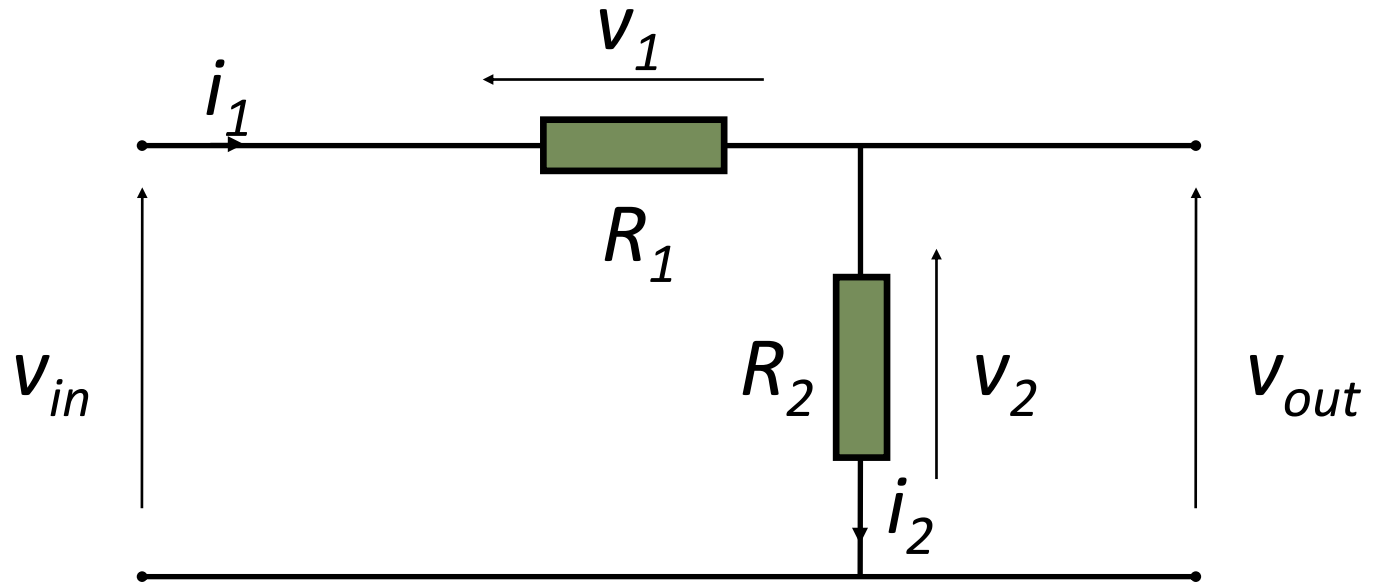


Ohm's Law ... $v_1 = i_1 R_1$ and $v_2 = i_2 R_2$

KCL ... $i_1 = i_2$

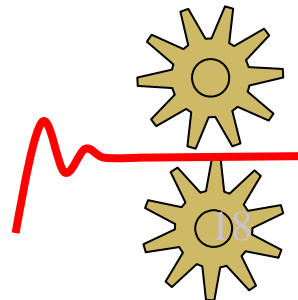


Solution:

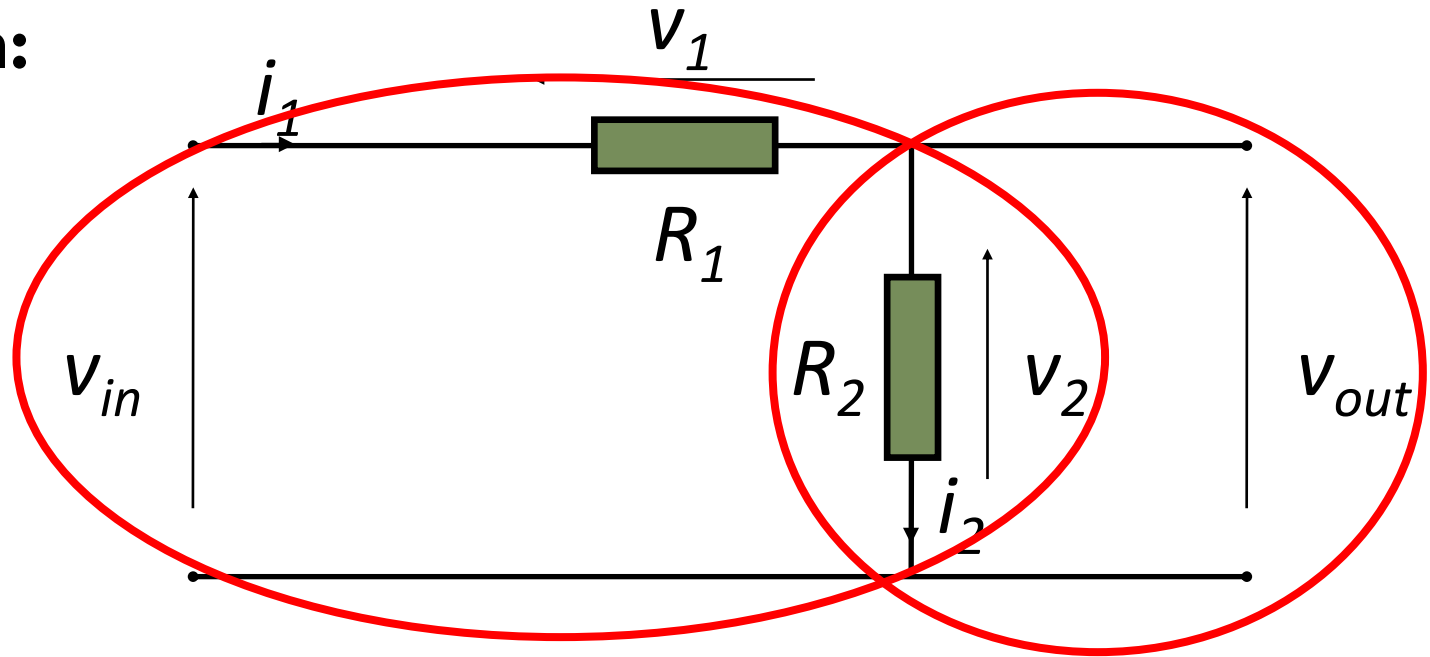


Ohm's Law ... $v_1 = i_1 R_1$ and $v_2 = i_2 R_2$

KCL ... $i_1 = i_2$

KVL ...

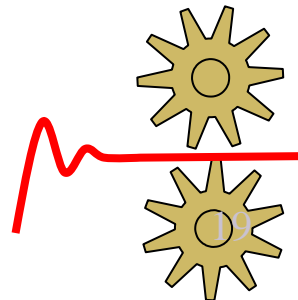

Solution:

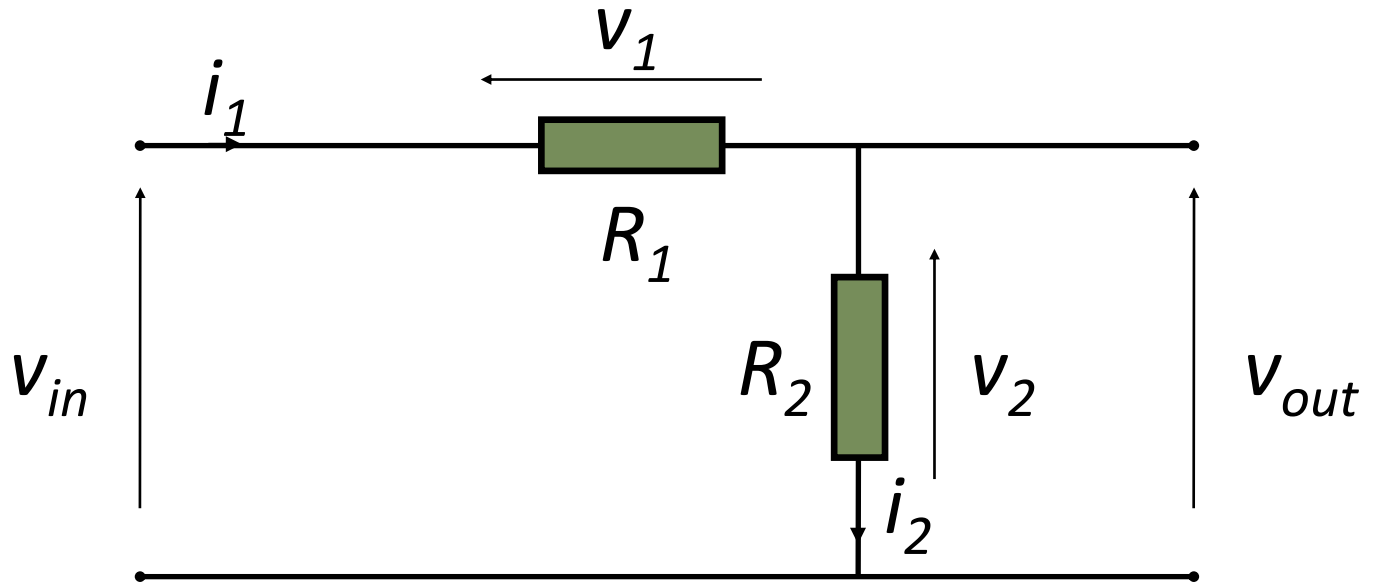


Ohm's Law ... $v_1 = i_1 R_1$ and $v_2 = i_2 R_2$

KCL ... $i_1 = i_2$

KVL ... $v_{in} = v_1 + v_2$ and $v_{out} = v_2$

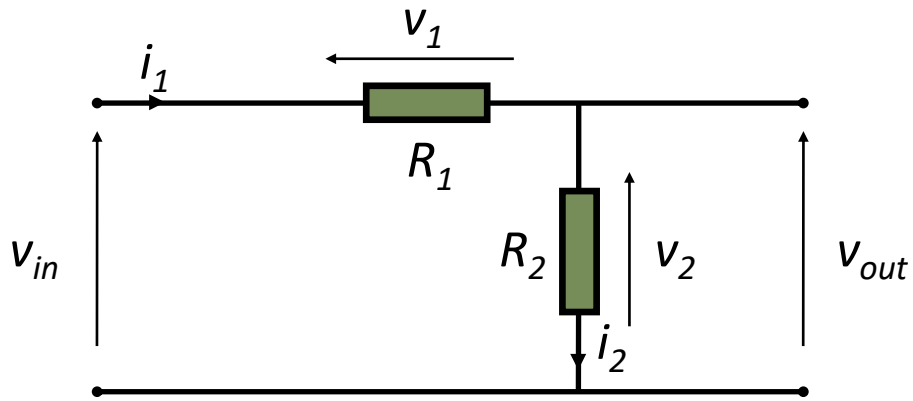A decorative graphic at the bottom right of the slide, featuring two interlocking gears (one yellow and one grey) and a red squiggly line.





$$v_1 = i_1 R_1 \text{ and } v_2 = i_2 R_2$$

$$i_1 = i_2$$

$$v_{in} = v_1 + v_2 \text{ and } v_{out} = v_2$$

Hence ...

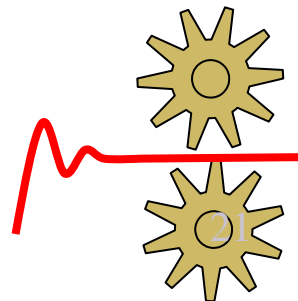

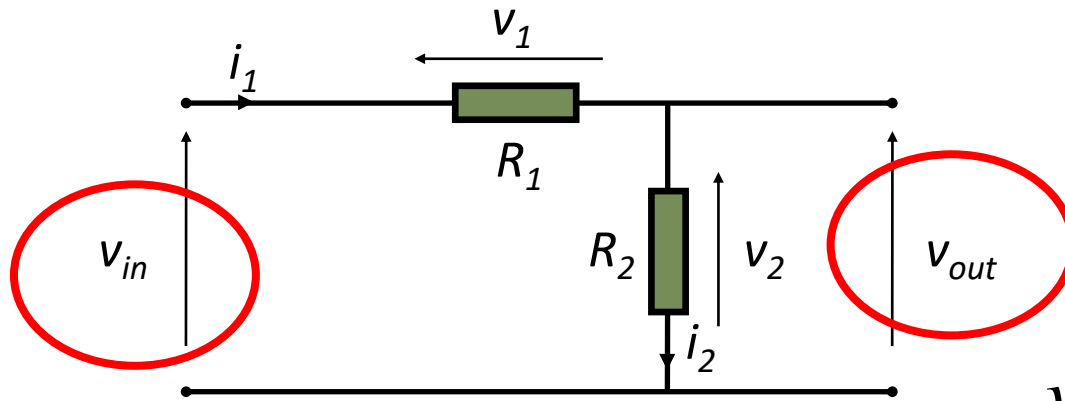


$$v_1 = i_1 R_1 \text{ and } v_2 = i_2 R_2$$


$$i_1 = i_2$$

$$v_{in} = v_1 + v_2 \text{ and } v_{out} = v_2$$

Hence ...
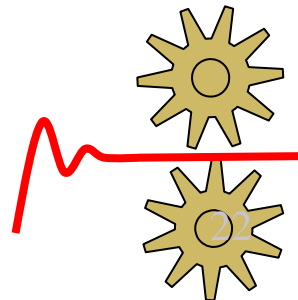
$$\frac{v_{out}}{v_{in}} = \frac{v_2}{v_1 + v_2}$$



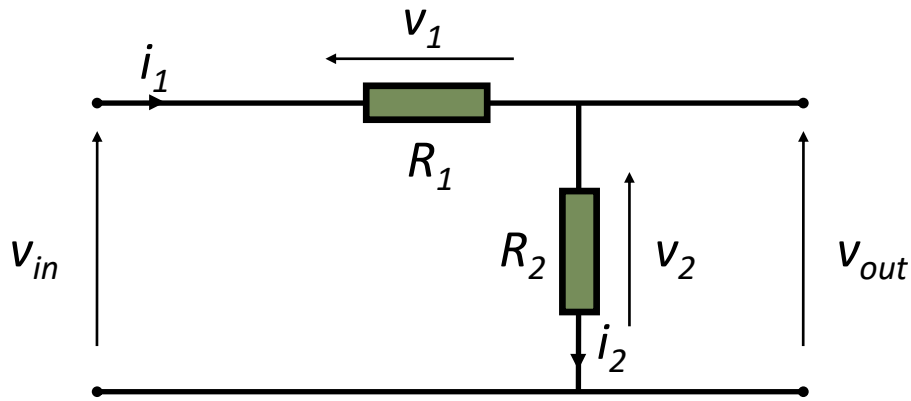


$$v_1 = i_1 R_1 \text{ and } v_2 = i_2 R_2$$


$$i_1 = i_2$$

$$v_{in} = v_1 + v_2 \text{ and } v_{out} = v_2$$

Hence ...
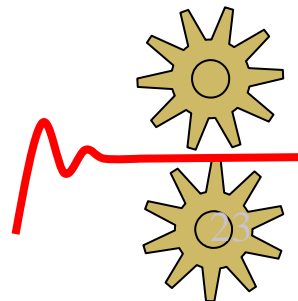
$$\frac{v_{out}}{v_{in}} = \frac{v_2}{v_1 + v_2} = \frac{i_2 R_2}{i_1 R_1 + i_2 R_2}$$



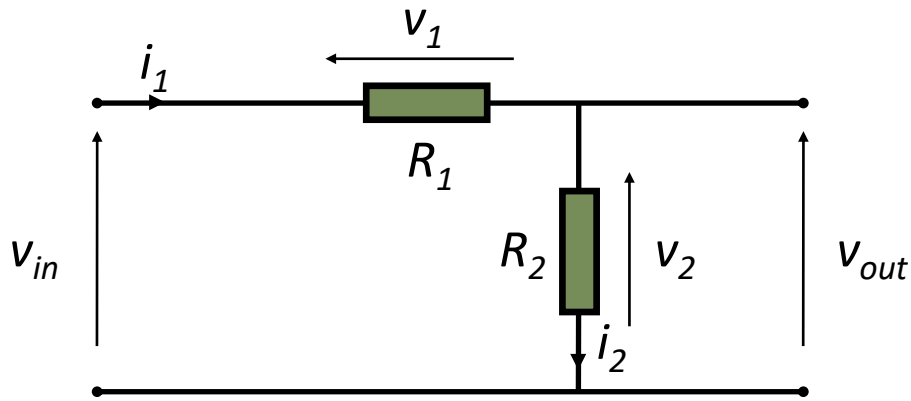


$$v_1 = i_1 R_1 \text{ and } v_2 = i_2 R_2$$


$$i_1 = i_2$$

$$v_{in} = v_1 + v_2 \text{ and } v_{out} = v_2$$

Hence ...
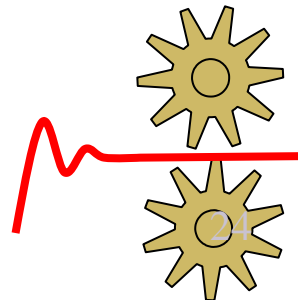
$$\frac{v_{out}}{v_{in}} = \frac{v_2}{v_1 + v_2} = \frac{i_2 R_2}{i_1 R_1 + i_2 R_2} = \frac{i_2 R_2}{i_2 R_1 + i_2 R_2}$$



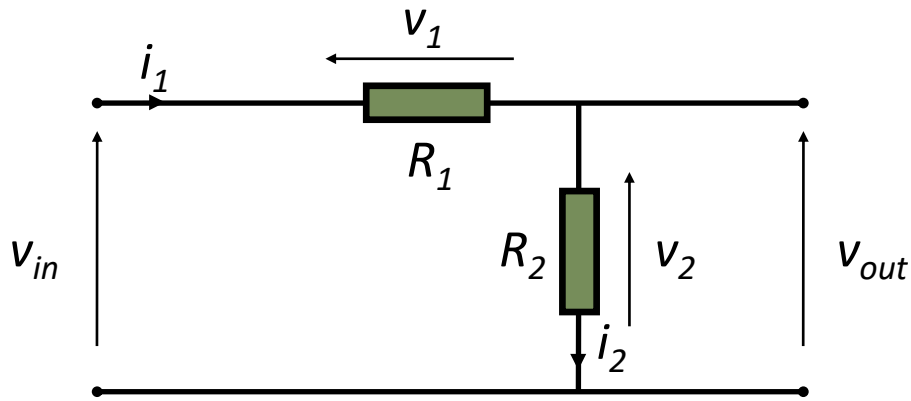

$$v_1 = i_1 R_1 \text{ and } v_2 = i_2 R_2$$


$$i_1 = i_2$$


$$v_{in} = v_1 + v_2 \text{ and } v_{out} = v_2$$

Hence ...

$$\frac{v_{out}}{v_{in}} = \frac{v_2}{v_1 + v_2} = \frac{i_2 R_2}{i_1 R_1 + i_2 R_2} = \frac{i_2 R_2}{i_2 R_1 + i_2 R_2}$$

$$= \frac{R_2}{R_1 + R_2}$$

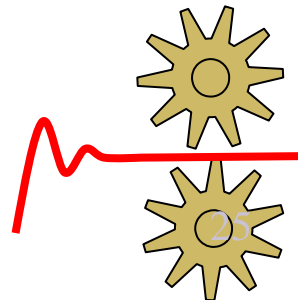

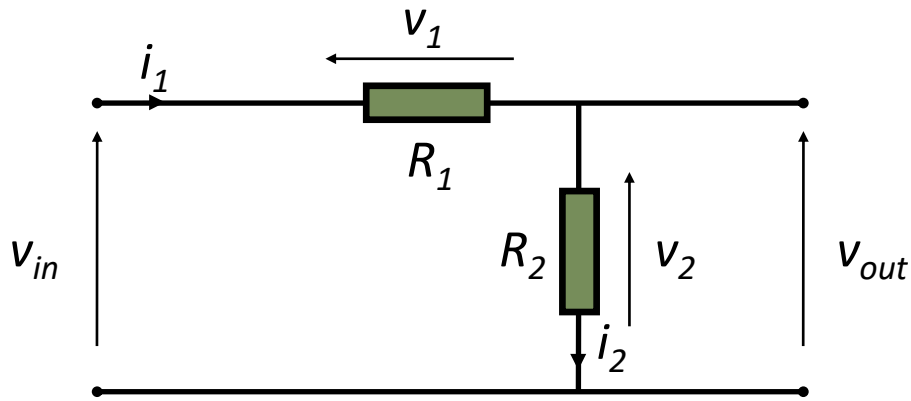

$$v_1 = i_1 R_1 \text{ and } v_2 = i_2 R_2$$


$$i_1 = i_2$$

$$v_{in} = v_1 + v_2 \text{ and } v_{out} = v_2$$

Hence ...



$$\frac{v_{out}}{v_{in}} = \frac{v_2}{v_1 + v_2} = \frac{i_2 R_2}{i_1 R_1 + i_2 R_2} = \frac{i_2 R_2}{i_2 R_1 + i_2 R_2}$$
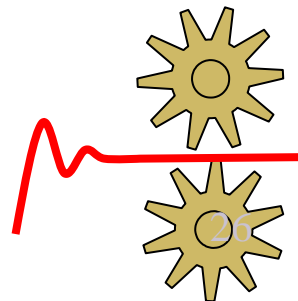
$$= \frac{R_2}{R_1 + R_2} \quad \dots \text{ voltage divider rule}$$





Modelling of Static Systems

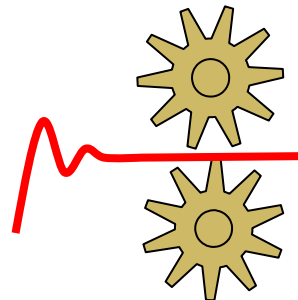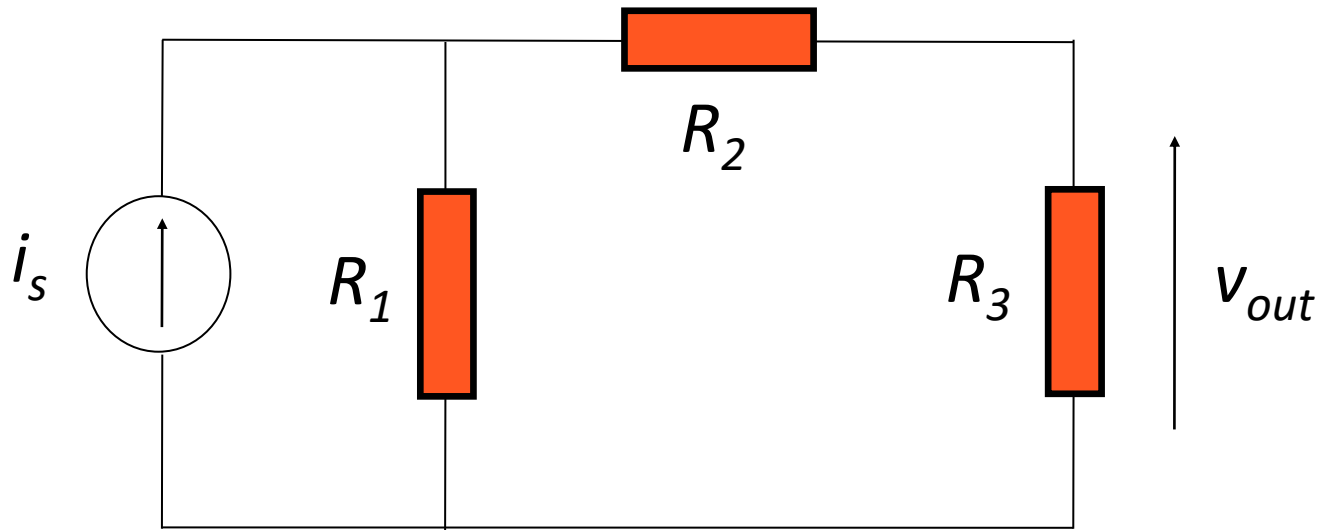
- *Ex. 3.2(a) Derive the input-output relationship for the following circuit given that the input is the current source i_s and the output is the voltage v_{out} (across resistor R_3 as shown):*



Solution:

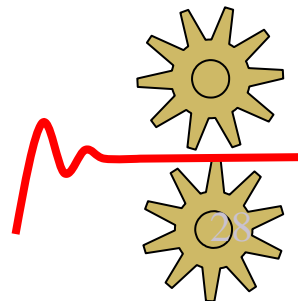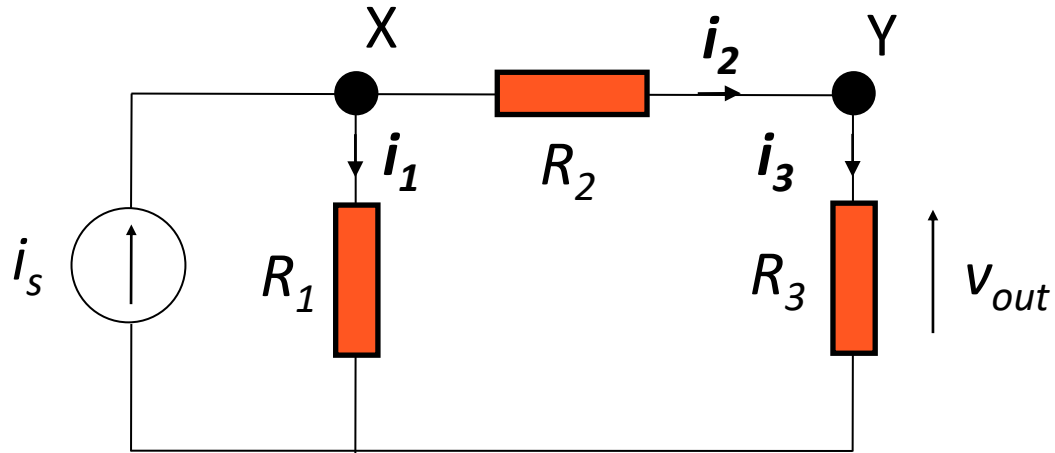


Solution:

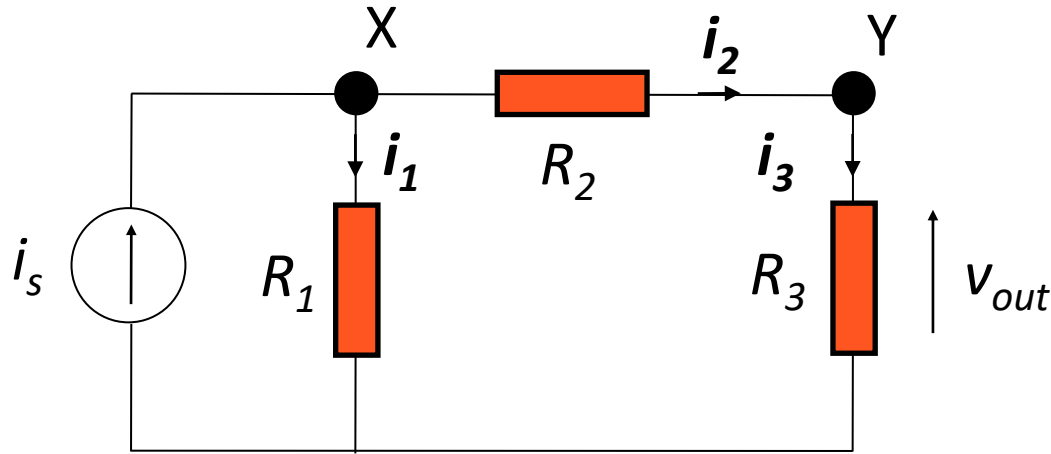


Using nodal analysis, we apply KCL to each of the nodes X and Y, as shown.

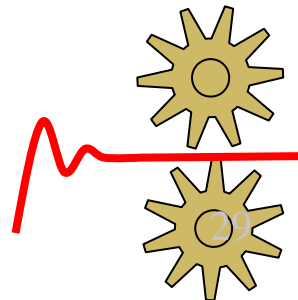
The voltage at node X is given by v_X while the voltage at node Y is v_{out} in this case.




Solution:

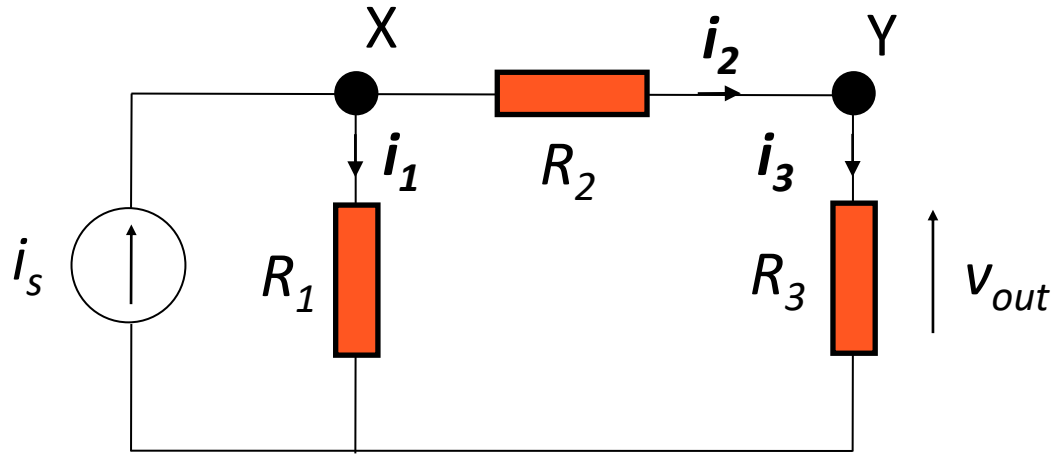

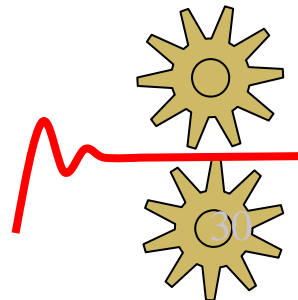KCL @ node X:
$$i_s = i_1 + i_2 \Rightarrow i_s = \frac{v_X}{R_1} + \frac{v_X - v_{out}}{R_2}$$




Solution:

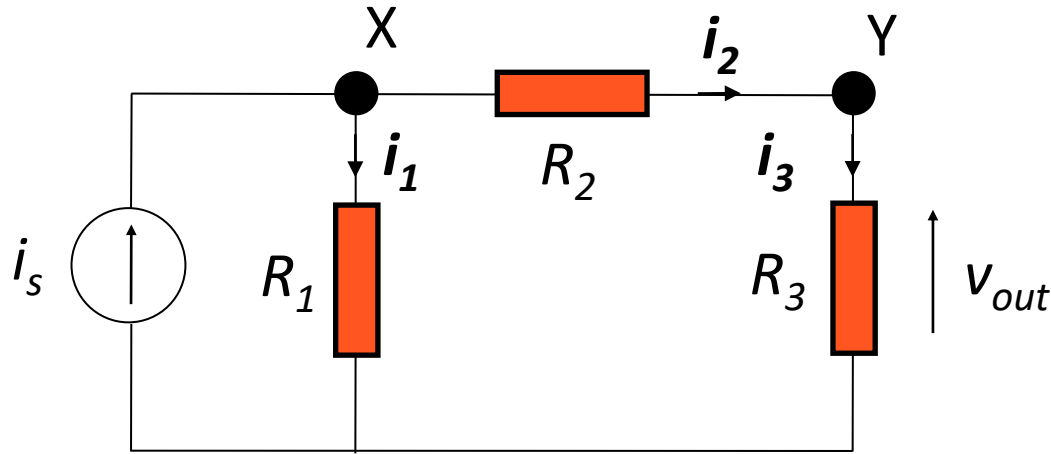


KCL @ node X:
$$i_s = i_1 + i_2 \Rightarrow i_s = \frac{v_X}{R_1} + \frac{v_X - v_{out}}{R_2}$$

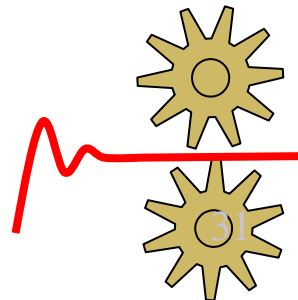KCL @ node Y:
$$i_2 = i_3 \Rightarrow \frac{v_X - v_{out}}{R_2} = \frac{v_{out}}{R_3}$$





Solution:

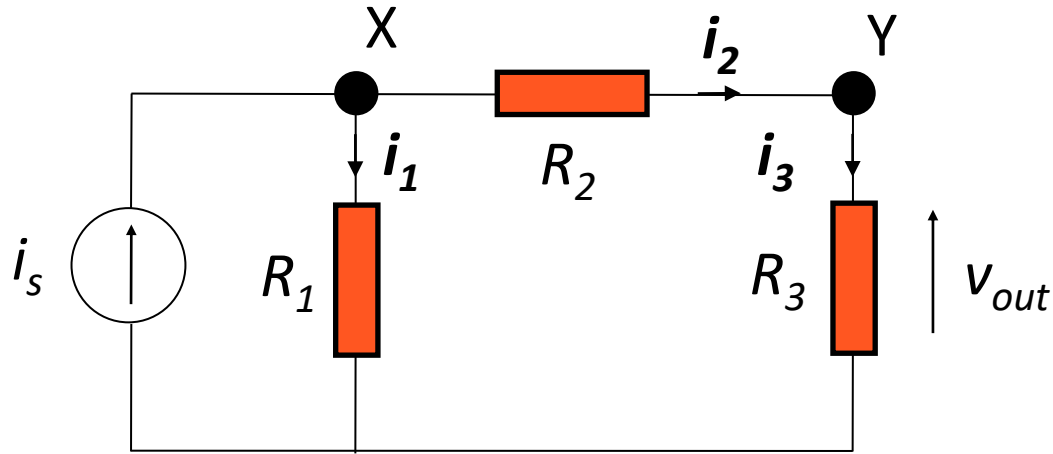


$$i_s = \frac{v_X}{R_1} + \frac{v_X - v_{out}}{R_2}$$

$$\frac{v_X - v_{out}}{R_2} = \frac{v_{out}}{R_3}$$

Rearranging gives:

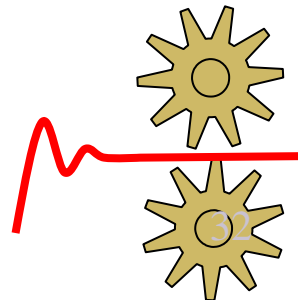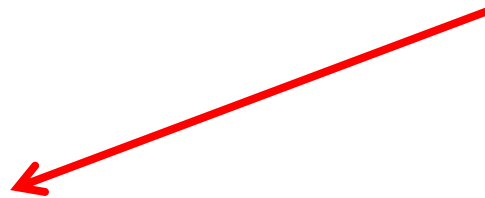

Solution:

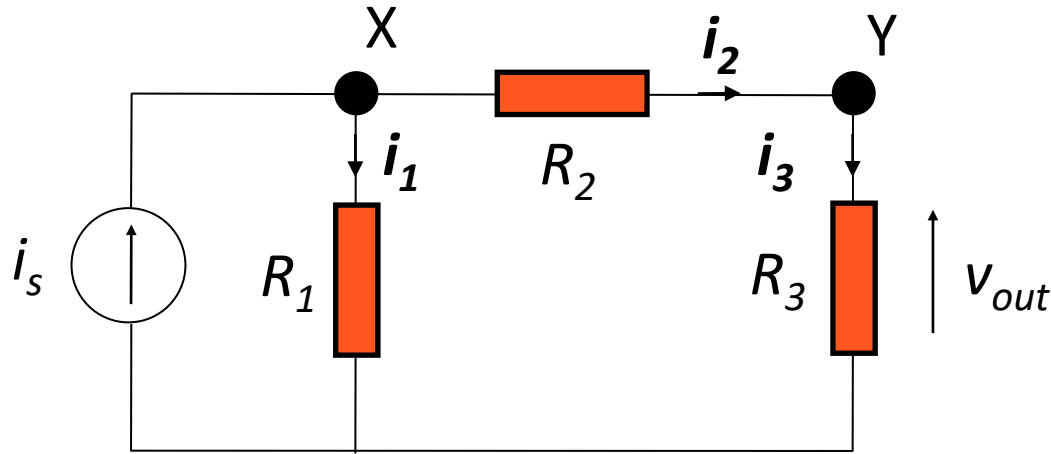


$$i_s = \frac{v_X}{R_1} + \frac{v_X - v_{out}}{R_2}$$


$$\frac{v_X - v_{out}}{R_2} = \frac{v_{out}}{R_3}$$

Rearranging gives:
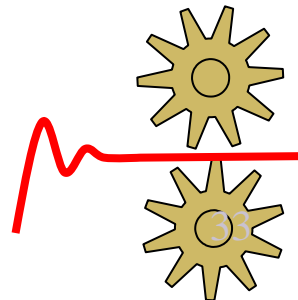
$$v_X - v_{out} = \frac{R_2}{R_3} v_{out}$$



Solution:

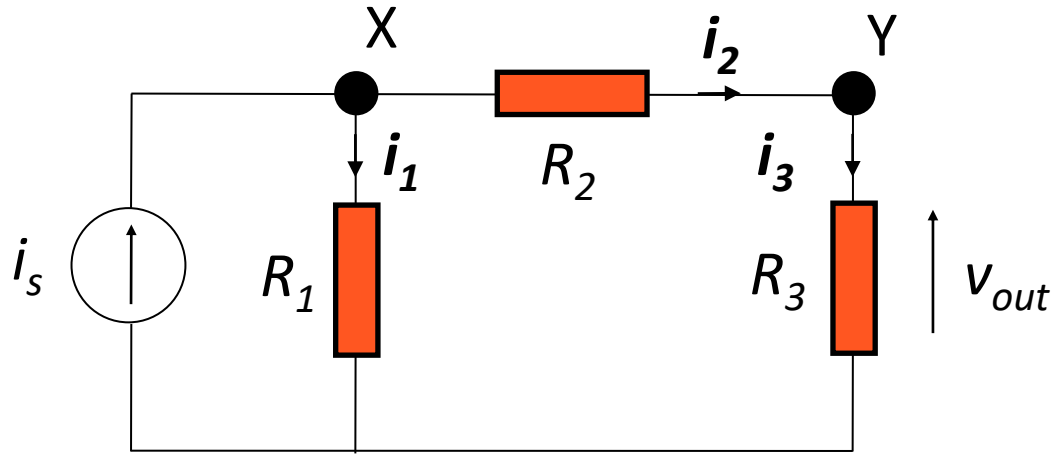


$$i_s = \frac{v_X}{R_1} + \frac{v_X - v_{out}}{R_2}$$


$$\frac{v_X - v_{out}}{R_2} = \frac{v_{out}}{R_3}$$

Rearranging gives:
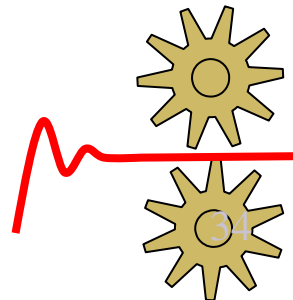
$$v_X - v_{out} = \frac{R_2}{R_3} v_{out} \quad \Rightarrow \quad v_X = v_{out} \left(1 + \frac{R_2}{R_3} \right)$$



Solution:

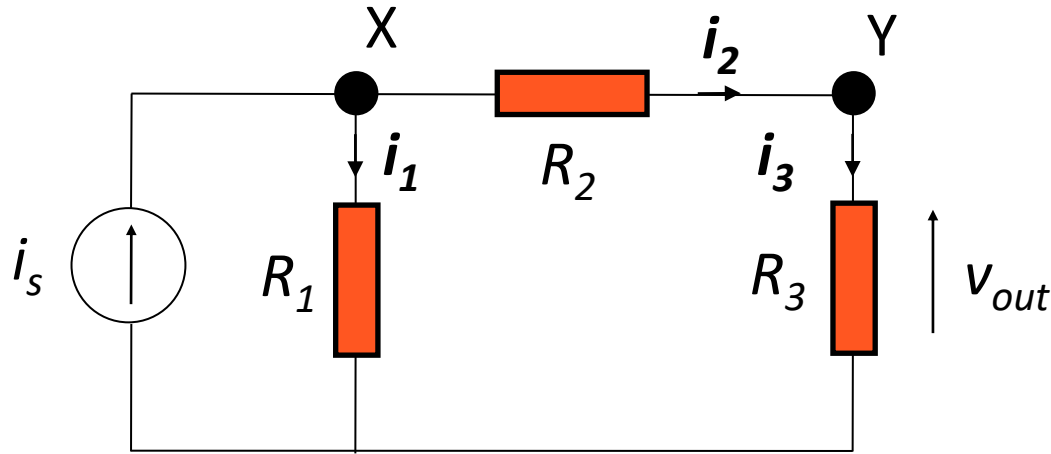


$$i_s = \frac{v_X}{R_1} + \frac{v_X - v_{out}}{R_2}$$


$$\frac{v_X - v_{out}}{R_2} = \frac{v_{out}}{R_3}$$

Rearranging gives:

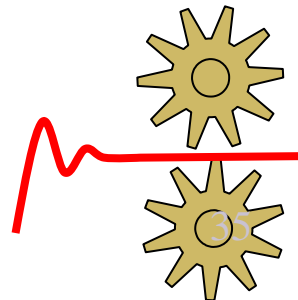
$$v_X - v_{out} = \frac{R_2}{R_3} v_{out} \quad \Rightarrow \quad v_X = v_{out} \left(1 + \frac{R_2}{R_3} \right)$$




Solution:

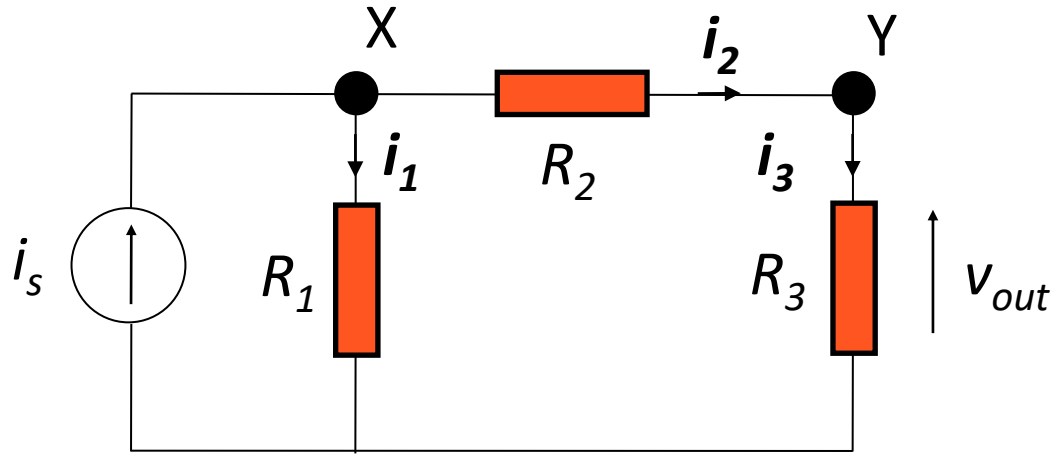

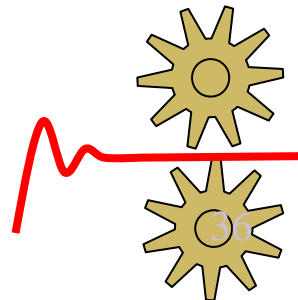
$$i_s = \frac{v_{out} \left(1 + \frac{R_2}{R_3} \right)}{R_1} + \frac{v_{out}}{R_3}$$




Solution:

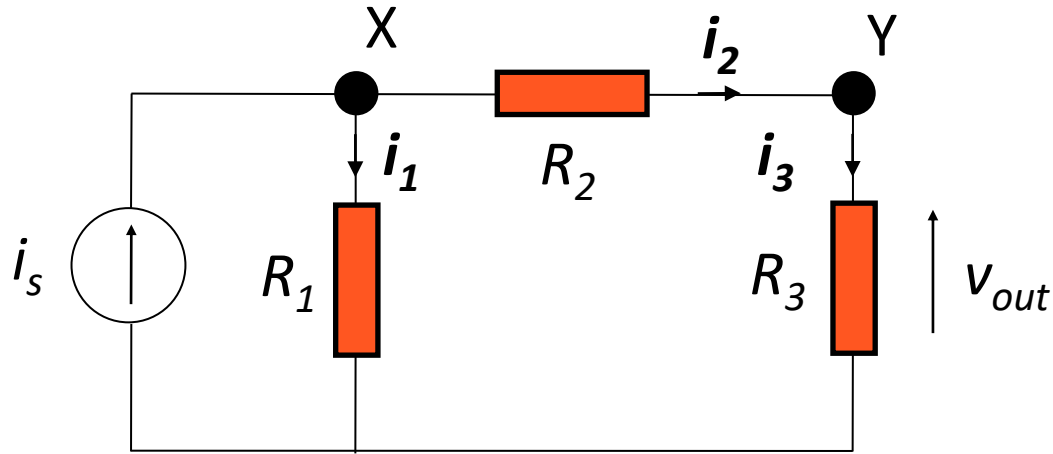
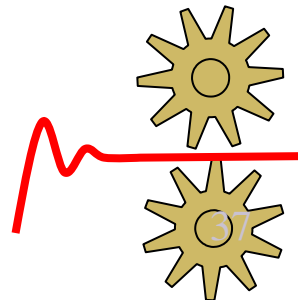
$$i_s = \frac{v_{out} \left(1 + \frac{R_2}{R_3} \right)}{R_1} + \frac{v_{out}}{R_3} \Rightarrow i_s = \left(\frac{\left(1 + \frac{R_2}{R_3} \right)}{R_1} + \frac{1}{R_3} \right) v_{out}$$




Solution:

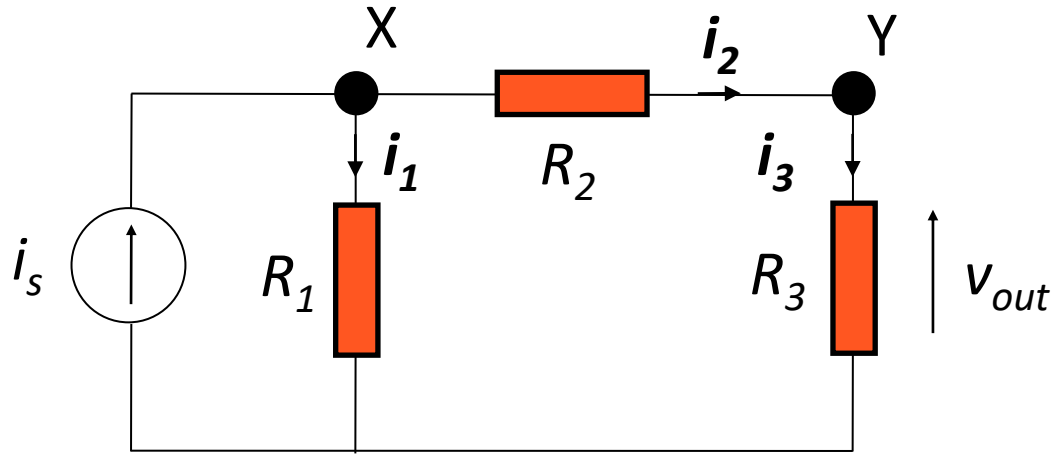


$$i_s = \frac{v_{out} \left(1 + \frac{R_2}{R_3} \right)}{R_1} + \frac{v_{out}}{R_3} \Rightarrow i_s = \left(\frac{\left(1 + \frac{R_2}{R_3} \right)}{R_1} + \frac{1}{R_3} \right) v_{out}$$

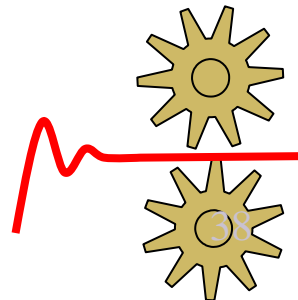
$$\Rightarrow \frac{i_s}{v_{out}} = \left(\frac{(R_3 + R_2) + R_1}{R_1 R_3} \right)$$



Solution:


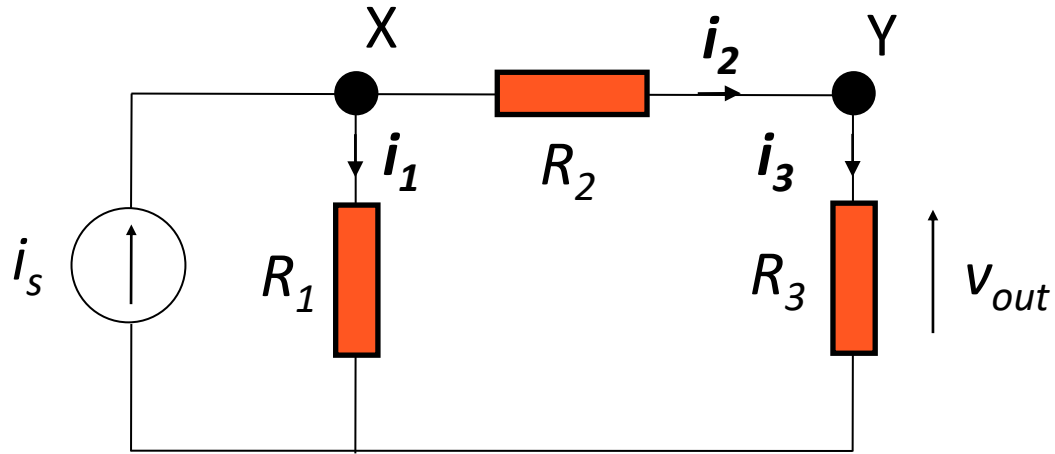

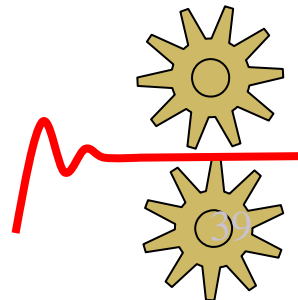
$$\Rightarrow \frac{v_{out}}{i_s} = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$




Modelling of Static Systems

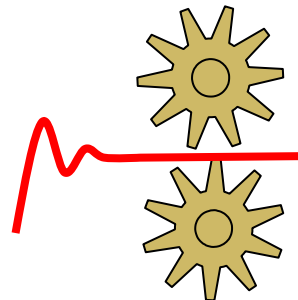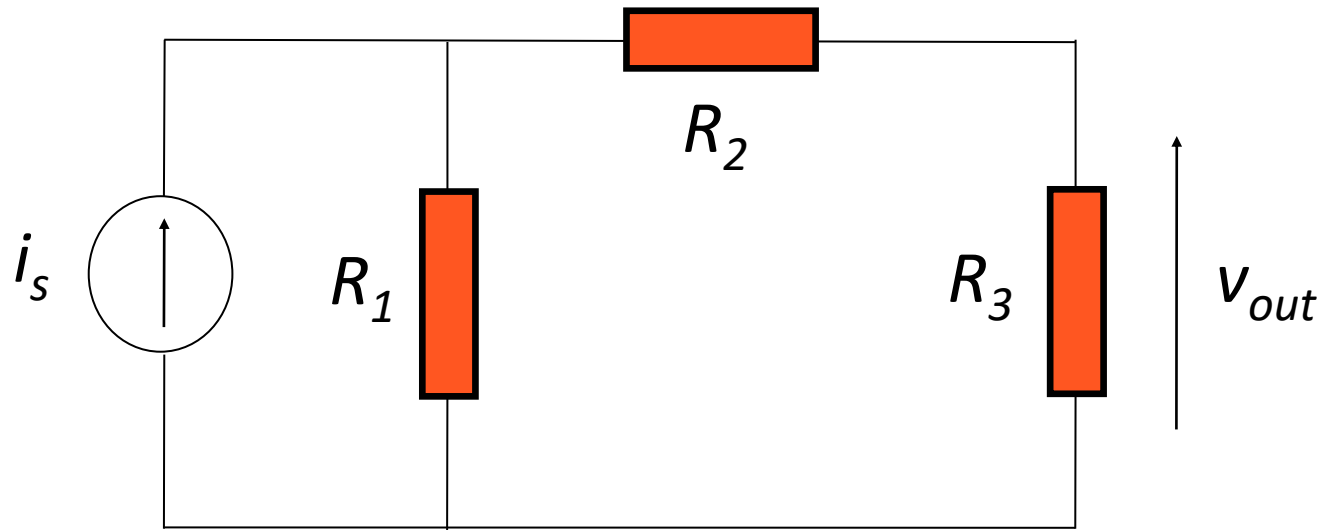
- *Ex. 3.2(b) Given that $R_1 = R_3 = 0.5\Omega$, $R_2 = 1\Omega$ and $i_s = 8A$, determine the voltage v_{out} for the circuit.*




Solution:

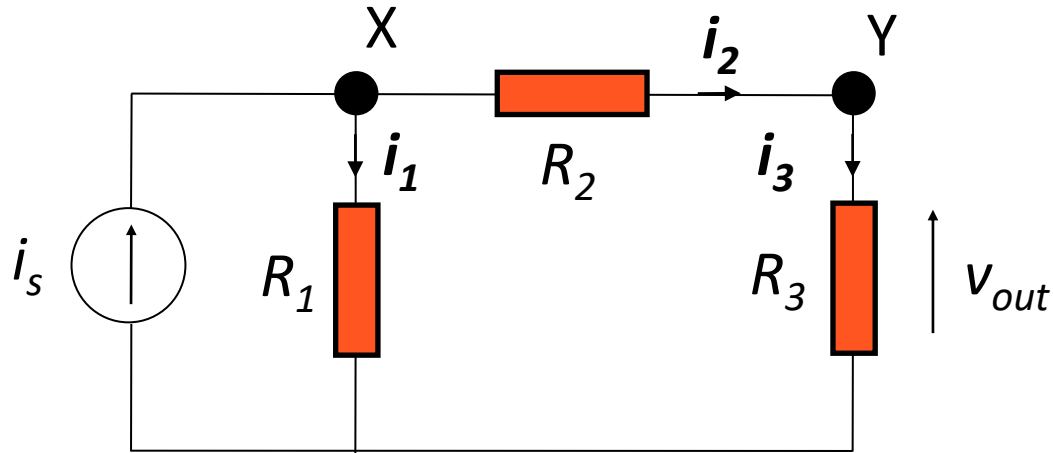
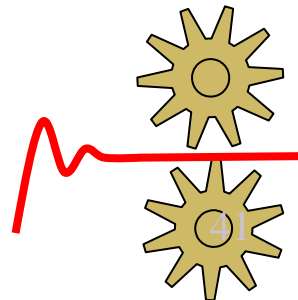
$$v_{out} = \frac{R_1 R_3}{R_1 + R_2 + R_3} i_s = \frac{(0.5)(0.5)}{0.5 + 1 + 0.5} (8)$$




Solution:

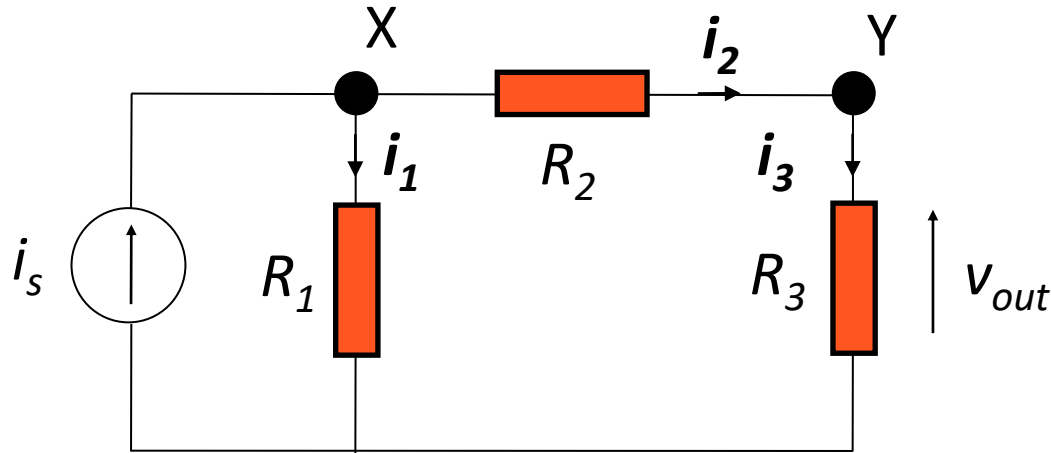


$$v_{out} = \frac{R_1 R_3}{R_1 + R_2 + R_3} i_s = \frac{(0.5)(0.5)}{0.5 + 1 + 0.5} (8) \quad (8)$$

$$= \frac{0.25}{2} (8) = 1V$$

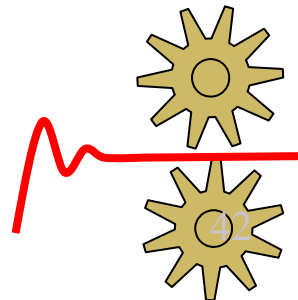

Modelling of Static Systems

- Overall, in the case of modelling of static systems, we can say:
 - A static relationship exists between input and output.
 - Static = memoryless = instantaneous.
 - We start with some basic laws for given system type - for example, Ohm's law for an electrical circuit.
 - Model parameters may be subject to error (e.g. resistance tolerance values).
 - We should also state any assumptions made in deriving model.

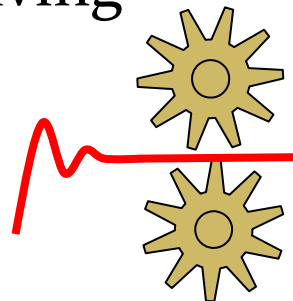


Modelling of Static Systems




more awesome pictures at THEMETAPICTURE.COM

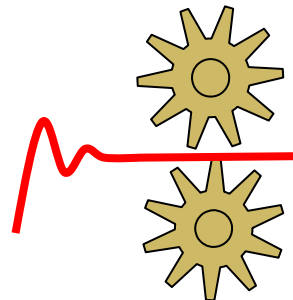- In general, all models are subject to assumptions and all models have errors.
- In the case of the previous examples, the wire in the circuit has resistance along its entire length – we can argue that this is negligible in relation to the value of the resistor itself.
- We also assume that the components are ideal.



Modelling of Static Systems

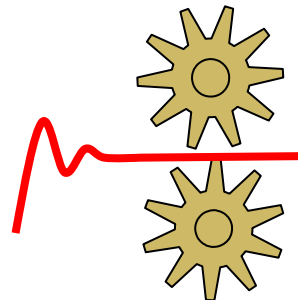- Ideally, the complete model description should give:
 - the model structure,
 - the parameters of the model,
 - modelling assumptions, including range of model validity, and
 - some measure of the error in the model.



Modelling of Static Systems

- Ideally, the complete model description should give:
 - the model structure,
 - the parameters of the model,
 - modelling assumptions, including range of model validity, and
 - some measure of the error in the model.
- In practice, most real systems have dynamics associated with them – even resistors!
- Sometimes these dynamics have a negligible effect on the system behaviour that we are interested in studying allowing us to assume steady state (or static) conditions.

